
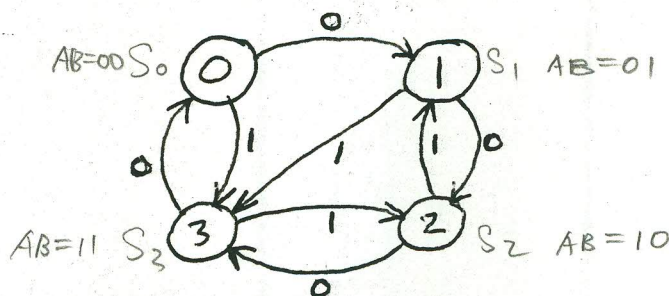


(One sheet of notes permitted -- attach to exam paper)

 1. Write J-K flip-flop input equations for this sequential machine:




2. Redraw this state graph with all redundant states removed (if any):



 3. Design a typical cell for a space iterative network to detect a legal 2-out-of-5 code.

(A 2-out-of-5 code contains two ones and three zeros)

Five of these cells are to be used, each with a one bit input plus a necessary number of lines to propagate state information between cells.



A termination cell is also required which will produce $Z=1$ for a legal code and $Z=0$ for an illegal code.

Show a typical iterative cell, the termination cell, and how to connect the complete system.

1. FLIP-FLOPS:

(1) J-K FLIP-FLOP:

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = JQ' + K'Q$$

Q	Q ⁺	J	K
0	0	0	X
0	1	0	1
1	0	1	X
1	1	1	0

(2) D FLIP-FLOP

D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

$$Q^+ = D$$

(3) T FLIP-FLOP

T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^+ = T \oplus Q$$

(4) S-R FLIP-FLOP

S	R	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-


$$Q^+ = S + R'Q$$

} not allowed

2. EXAMPLE FOR DRAWING THE TIMING CHART:

FROM STATE GRAPH, ASSIGN FF #, AND TO EACH STATE, CREATE STATE TABLE. E.g.

X	A	B	A ⁺	B ⁺	J _A	K _A	J _B	K _B	Z
0	0	0	0	1	0	X	1	X	1
0	0	1	1	0	1	X	X	1	1
0	1	0	1	1	X	0	1	X	0
0	1	1	0	0	X	1	X	1	0
1	0	0	1	0	1	X	0	X	1
1	0	1	0	0	0	X	X	1	0
1	1	0	1	1	X	0	1	X	1
1	1	1	0	0	X	1	X	1	0

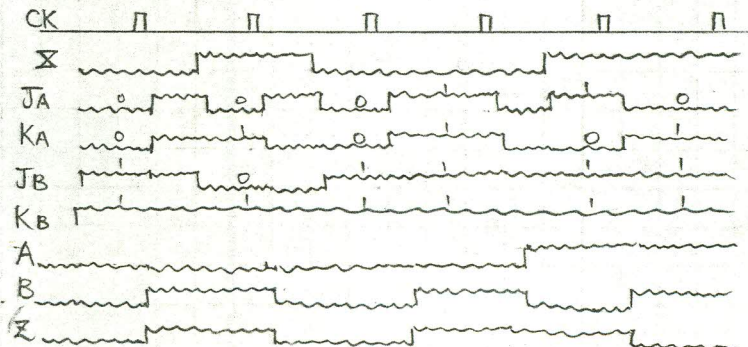⇒ KARNAUGH MAP: $J_A = X'B + XB'$, $K_A = B$, $J_B = X' + A$, $K_B = 1$, $Z = (A')B' + A'(B')$ 


* MOORE NO FALSE OUTPUT, MEALY MAY HAVE.

3. DIFFERENCES BETWEEN MOORE & MEALY STATE GRAPH & TABLE:

MOORE:



MEALY

 

PRE. S.	NEXT X=0, Z=1	Z	P. STATE	NEXT X=0, Z=1	OUTPUT X=0, Z=1
---------	------------------	---	----------	------------------	--------------------

4. Guideline for STATE ASSIGNMENT: (BY EXAMPLE)


	X=0	1	0	1
S ₀	S ₁	S ₂	0	0
S ₁	S ₃	S ₂	0	0
S ₂	S ₁	S ₄	0	0
S ₃	S ₅	S ₂	0	0
S ₄	S ₁	S ₆	0	0
S ₅	S ₅	S ₂	1	0
S ₆	S ₁	S ₆	0	1

G.1. (S₀, S₁, S₃, S₅) (S₃, S₅) (S₄, S₆) (S₀, S₂, S₄, S₆)2. (S₁, S₂) (S₂, S₃) (S₁, S₄) (S₂, S₅) 2x (S₁, S₆) 2x

A	0	1
S ₀		
S ₂	S ₅	
S ₄	S ₃	
S ₆	S ₁	

STATE MAP

A	0	1
S ₁	X	X
S ₃	S ₅	S ₄
S ₅	S ₃	S ₆
S ₆	S ₁	S ₂

 

5. LOGIC ELEMENTS

"AND"

"OR"

"INVERSE"

NATIONAL

 42-381 50 SHEETS 5 SQUARE
 42-382 100 SHEETS 5 SQUARE
 42-389 200 SHEETS 5 SQUARE
 Made in U. S. A.

	$\bar{A}$	A
$\bar{B}$	1	0
B	0	1

$$K_R = \bar{X} + A$$

STATE	NEXT		OUTPUT	
	$X=0$	$X=1$	$X=0$	$X=1$
✓ S_0	S_0	S_4	0	0
S_1	S_0	S_4	0	0
✓ S_2	S_1 S_0	S_5 S_4	0	1
S_3	S_1 S_0	S_5	0	1
✓ S_4	S_2	S_6 S_4	0	1
S_5	S_2	S_6	0	1
S_6	S_3 S_2	S_7 S_6	0	1
S_7	S_3	S_7	0	1

$$S_7 = S_6$$

3. I THINK WE HAVE TO USE FOUR STATES TO "REMEMBER"

INPUTS FROM LEFT-HAND SIDE HAVE

$S_0 \Rightarrow$ ZERO 1's , $S_1 =$ one 1 , $S_2 =$ Two 1's $S_3 >$ TWO 1's
 $AB = 00$ $AB = 01$ $AB = 10$ $AB = 11$

FOR TYPICAL CELL i (~~WE ARE GOING TO USE TWO D-F.F.~~)

S_i	S_{i+1}		Z
	$X_i=0$	$X_i=1$	
S_0	S_0	S_1	0
S_1	S_1	S_2	0
S_2	S_2	S_3	1
S_3	S_3	S_3	0

$A_i B_i$		$A_{i+1} B_{i+1}$		Z
		$X_i=0$	$X_i=1$	
0 0		0 0	0 1	0
0 1		0 1	1 0	0
1 0		1 0	1 1	1
1 1		1 1	1 1	0

$A_i B_i$		X_i	
		0	1
0 0		0	0
0 1		0	1
1 1		1	1
1 0		1	1

A_{i+1}

$A_i B_i$		X_i	
		0	1
0 0		0	1
0 1		1	0
1 1		1	1
1 0		0	1

B_{i+1}

$A_i B_i$		X_i	
		0	1
0 0		0	1
0 1		0	1
1 0		0	0
1 1		0	0


Z

$$A_{i+1} = A_i + B_i X_i$$


$$B_{i+1} = B_i \bar{X}_i + A_i X_i + \bar{B}_i X_i$$

$$Z = A_i \bar{B}_i$$


THE TYPICAL CELL CIRCUIT:

 

TERMINATION CELL

 

③ CONNECTION

 

$$\begin{aligned} a_i &= A_i \\ b_i &= B_i \end{aligned}$$

Good


C

H

E

N

 1. Use a PAL16R6 to design a "2-out-of-5" code up-counter (see page 13 for code sequence). Show your design on the PAL diagram sheet attached. Take into account the fact that the PAL outputs are inverted.
2. Use a 74163 counter to build this state machine. Show a complete circuit



Logic Diagram PAL16R6

INPUTS (0-31)

PRODUCT TERMS (0-63)

CK 1

SR 2

D0 3

D1 4

D2 5

D3 6

D4 7

D5 8

SL 9

18 LIRD

19 Q0

17 Q1

18 Q2

15 Q3

14 Q4

13 Q5

12 RILO

11 E=0

Q1, Q2, Q3, Q4, Q5

OK

Invert on

PROBLEM 1: USE PAL16 R6 TO BUILD A UP-COUNTER FOR "2-out-of-5" code

INPUT					OUTPUT									
Q ₁	Q ₂	Q ₃	Q ₄	Q ₅	Q ₁ ⁺	Q ₂ ⁺	Q ₃ ⁺	Q ₄ ⁺	Q ₅ ⁺	D ₁	D ₂	D ₃	D ₄	D ₅
0	0	0	1	1	0	0	1	0	1	1	1	0	1	0
0	0	1	0	1	0	0	1	1	0	1	1	0	0	1
0	0	1	1	0	0	1	0	0	1	1	0	1	1	0
0	1	0	0	1	0	1	0	1	0	1	0	1	0	1
0	1	0	1	0	0	1	1	0	0	1	0	0	1	1
0	1	1	0	0	1	0	0	0	1	0	1	1	1	0
1	0	0	0	1	1	0	0	1	0	0	1	1	0	1
1	0	0	1	0	1	0	1	0	0	0	1	0	1	1
1	0	1	0	0	1	1	0	0	0	0	0	1	1	1
1	1	0	0	0	0	0	0	1	1	1	1	1	0	0

$$D_1 = \overline{Q_1} \overline{Q_2} \overline{Q_3} Q_4 Q_5$$

+ ...

DONE IN CIRCUIT attached !

1. Eliminate all redundant rows in the following primitive flow table, then convert to Mealy and merge all possible rows.

	AB				Z
	00	01	11	10	
1	①	4	2	3	1
2	1	8	②	3	1
3	9	8	7	③	0
4	1	④	7	6	0
5	⑤	4	7	6	1
6	5	4	2	⑥	0
7	9	8	⑦	3	1
8	5	⑧	2	10	0
9	⑨	4	2	3	1
10	1	8	7	⑩	1
11	5	4	⑪	10	1


15.
A.
美.

2. Problem 27D on page 590 has the following primitive flow table

	X1 X2				Z
	00	01	11	10	
1	①	5	-	2	1
2	8	-	3	②	1
3	-	4	③	7	1
4	1	④	6	-	1
5	1	⑤	6	-	0
6	-	4	⑥	7	0
7	8	-	3	⑦	0
8	⑧	5	-	2	0

There are no redundant states, and none merge.
Find a set of race-free state assignments for this problem.
Show the binary bits assigned to each state.

 3. Identify all static hazards in the following circuit, and draw an equivalent circuit which is free of static hazards.



1. The following are all the potentially equivalent stable total states:

100

(1, 5), (1, 9), (5, 9), (4, 8), (2, 7), (7, 11), (2, 11), (3, 6)

1-5	2-7, 3-6	X
1-9	✓	✓
5-9	7-2, 6-3	X
4-8	1-5, 7-2, 6-10	X
2-7	1-9	✓
7-11	9-5, 8-4, 3-10	X
2-11	1-5, 8-4, 3-10	X
3-6	9-5, 8-4, 7-2	X

The equivalent s.t.s are (1, 9) and (2, 7)

Reduced

	AB					Z			
	00	01	11	10		00	01	11	10
1	①	4	2	3	}	1	-	-	-
2	1	8	②	3		-	-	1	-
3	1	8	2	③		-	-	-	0
4	1	④	2	6	}	-	0	-	-
5	⑤	4	2	6		1	-	-	-
6	5	4	2	⑥		-	-	-	0
8	5	⑧	2	10		-	0	-	-
10	1	8	2	⑩		-	-	-	1
11	5	4	⑪	10		-	-	1	-

Mealy merge

		AB					Z			
		00	01	11	10		00	01	11	10
a	1	①	4	2	3		1	-	-	-
b	2, 3	1	8	②	③		-	-	1	0
c	4	1	④	2	6		-	0	-	-
d	5, 6	⑤	4	2	⑥		-	-	-	0
e	8	5	⑧	2	10		-	0	-	-
f	10	1	8	2	⑩		-	-	-	1
g	11	5	4	⑪	10		-	-	1	-

OR :

		AB					Z			
		00	01	11	10		00	01	11	10
a		①	c	b	b		1	-	-	-
b		a	e	⑥	⑥		-	-	1	0
c		a	③	b	d		-	0	-	-
d		①	c	b	②		1	-	-	0
e		d	⑤	b	f		-	0	-	-
f		a	e	b	⑦		-	-	-	1
g		d	c	④	f		-	-	1	-


2. Required transition:

col: 00 : $2, 7 \rightarrow 8$, $4, 5 \rightarrow 1$

col: 01 : $1, 8 \rightarrow 5$, $3, 6 \rightarrow 4$

col: 11 : $2, 7 \rightarrow 3$, $4, 5 \rightarrow 6$

 col: 10 : $1, 8 \rightarrow 2$, $3, 6 \rightarrow 7$



OR


	0	1
00	1	5
01	2	8
11	3	7
10	4	6



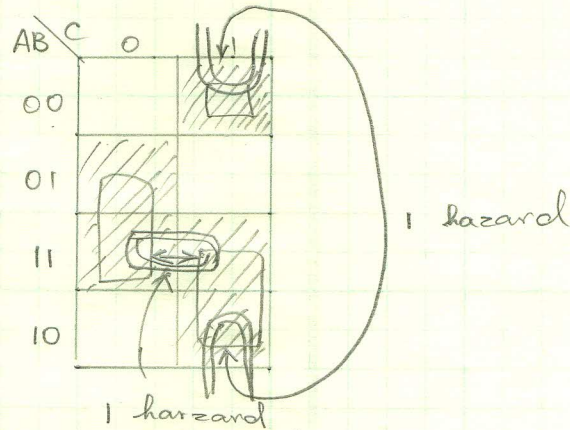3. From the circuit given in test sheet, we have

$$F^t = (\bar{A}\bar{B} + A)C + (\bar{B} + \bar{C}) \cdot B$$

$$= \bar{A}\bar{B}C + AC + B\bar{B} + B\bar{C}$$



One-hazards occur at $ABC = 001 \leftrightarrow 101$

and $ABC = 110 \leftrightarrow 111$

To eliminate the one-hazards, we have add two terms to F^t : AB and $\bar{B}\bar{C}$ ✓

$$(F^t)' = \overline{(\bar{A}\bar{B} + A)C + (\bar{B} + \bar{C})B}$$

$$= \overline{(\bar{A}\bar{B} + A)C} \cdot \overline{(\bar{B} + \bar{C})B}$$

$$= [\overline{(\bar{A}\bar{B} + A)} + \bar{C}] \cdot [\overline{(\bar{B} + \bar{C})} + \bar{B}]$$

$$= [(A+B) \cdot \bar{A} + \bar{C}] \cdot [BC + \bar{B}]$$


$$= (A\bar{A} + \bar{A}B + \bar{C})(BC + \bar{B})$$

$$= A\bar{A}B\bar{C} + \bar{A}B\bar{B}C + B\bar{C}\bar{C} + A\bar{A}\bar{B} + \bar{A}\bar{B}\bar{B} + \bar{B}\bar{C}$$

AB \ C	0	1
00	0	
01		0
11		
10	0	

no zero-hazard

 The equivalent static hazard free circuit =




What are the outstanding characteristics of :

TTL ECL
CMOS I²L

2. What are three sources of noise in a circuit board layout containing integrated circuits, and what could be done to help eliminate each ?
3. Consider this synchronous machine containing two D-flip-flops and combinational logic.
 - a) Is it a Mealy or Moore ?
 - b) Draw a state graph.
 - c) Draw a timing diagram showing the clock, X, A, B, Z. Assume A=B=0 initially, and the input changes midway between clock pulses. Use the input sequence X = 10011

X	A	B	Da	Db	Z
0	0	0	0	0	0
0	0	1	0	1	1
0	1	x	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	0	0

 

A door lock operates as follows: Inputs XY must be pressed in this sequence to unlock the door: 00, 01, 11, 10, 00. After inputting this sequence, the electric door latch will operate every time X is pressed. If Y is pressed, however, the system resets, and the unlock sequence must be entered to open the door again. Derive a minimum row flow table for this asynchronous system.

5. Make a set of race-free state assignments for the machine depicted by this flow table. Also, complete the output part of the table.

Present State	Next State				Outputs				<-- X1, X2
	00	01	11	10	00	01	11	10	
a	(a)	c	(a)	b	01		10		
b	(b)	d	a	(b)	01			00	
c	(c)	(c)	e	b	11	10			
d	a	(d)	a	-		11			
e	-	d	(e)	b			00		
f	b	-	e	(f)				11	
g	-	c	(g)	f		01			

PROBLEM 1:

1. FOR TTL, more capable of driving more gate inputs and faster than diode. And lower power consumption. ✓
2. ECL = fast ✓
3. Compared with TTL, CMOS has the advantage of much lower power dissipation. ✓
4. I²L, use currents instead of voltages. ✓

PROBLEM 2: THREE NOISE SOURCES:

1. Power and ground distribution problems ✓
 2. Signal crosstalk. ✓
 3. Transmission-line effects. ✓
1. For the first noise source, it can be minimized by keeping the power and ground lines as short and as direct as possible. such as to use a grid of conductors that approximates a plane. And the noise problem is solved by the use of capacitors called decoupling. ✓
2. Crosstalk can be reduced by physically separating crosstalk-prone conductors. It also can be reduced by the use of a good ground plane or grid. ✓
3. To match the characteristic impedance of the transmission line. like themselves. ✓

3.


X	A	B	A ⁺	B ⁺	Z
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	0	1	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	0	0

OR

	A	B	A ⁺ B ⁺		Z	
			X=0	X=1	X=0	X=1
S ₀	0	0	00	01	0	1
S ₁	0	1	01	10	1	0
S ₂	1	0	10	00	0	1
S ₃	1	1	10	00	0	0

a) It is a Mealy network.

b)

 

c)

AB \ X	0	1
00	0	0
01	0	1
11	1	0
10	1	0

D_a

AB \ X	0	1
00	0	1
01	1	0
11	0	0
10	0	0

D_b


AB \ X	0	1
00	0	1
01	1	0
11	0	0
10	0	1

Z


$$D_a = A\bar{X} + \bar{A}BX$$

$$D_b = \bar{A}B\bar{X} + A\bar{B}X$$

$$Z = \bar{A}B\bar{X} + \bar{B}X$$

 

4.

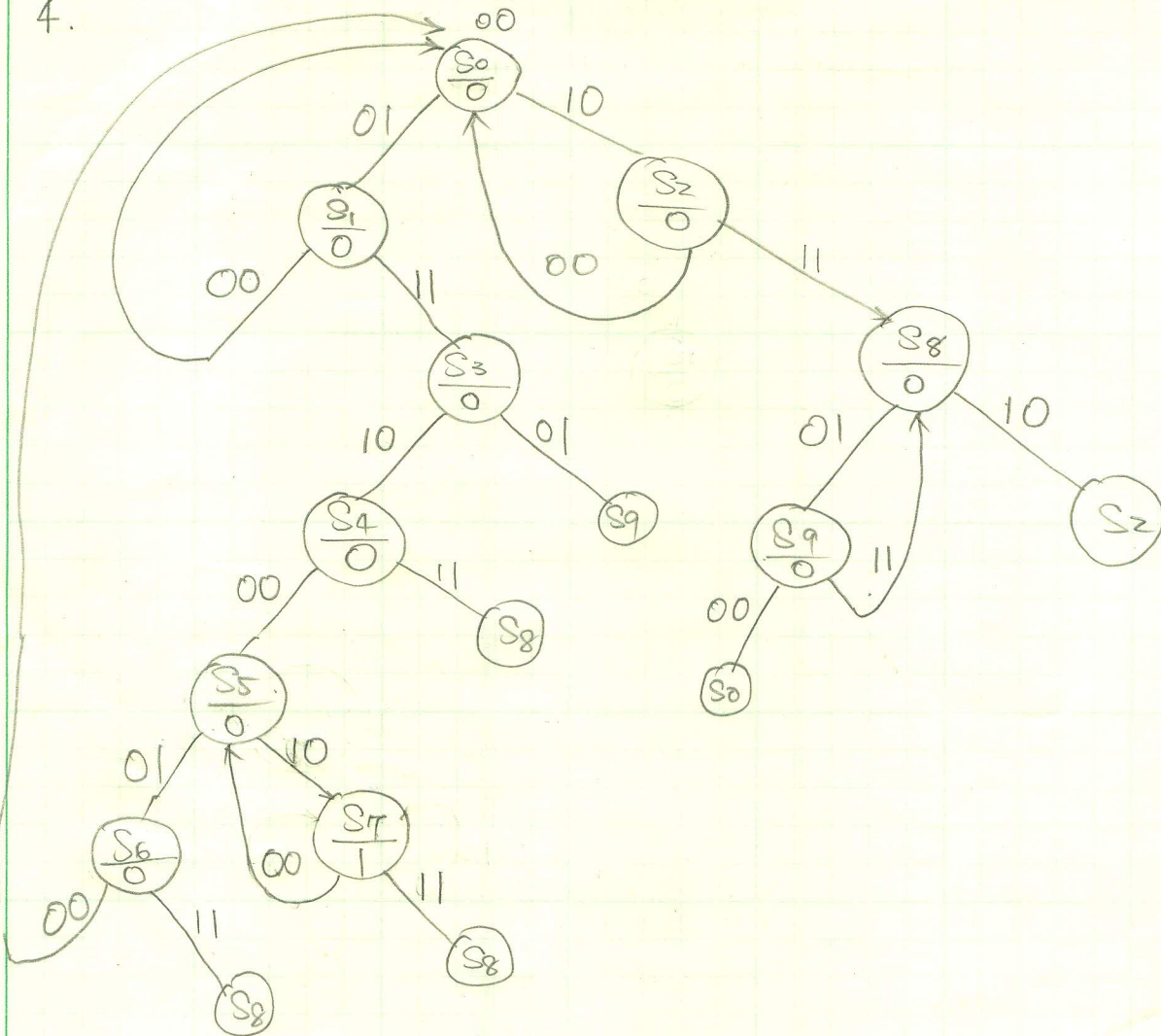

	00	01	11	10	Z
S0	S0	S1	-	S2	0
S1	S0	S1	S3	-	0
S2	S0	-	S8	S2	0
S3	-	S9	S3	S4	0
S4	S5	-	S8	S4	0
S5	S5	S6	-	S7	0
S6	S0	S6	S8	-	0
S7	S5	-	S8	S7	1
S8	-	S9	S8	S2	0
S9	S0	S9	S8	-	0

Six states
are sufficient

Reducing :

$$S_0 \leftrightarrow S_5$$

$$S_1 \leftrightarrow S_6 \leftrightarrow S_9$$

$$S_3 \leftrightarrow S_8$$

$$S_2 \leftrightarrow S_4$$

S_0, S_5	S_1-S_6, S_2-S_7	X
S_1, S_6	S_3-S_8	X
S_1, S_9	S_3-S_8	X
S_6, S_9	✓	
S_3, S_8	S_4-S_2	X
S_2, S_4	S_0-S_5	X

Reduced table

		00	01	11	10	Z			
		00	01	11	10	00	01	11	10
x S_0	(S ₀)	S ₁	—	S ₂	—	0	—	—	—
x S_1	S ₀	(S ₁)	S ₃	—	—	—	0	—	—
x S_2	S ₀	—	S ₈	(S ₂)	—	—	—	—	0
S_3	—	S ₆	(S ₃)	S ₄	—	—	—	0	—
S_4	S ₅	—	S ₈	(S ₄)	—	—	—	—	0
x S_5	(S ₅)	S ₆	—	S ₇	—	0	—	—	—
x S_6	S ₀	(S ₆)	S ₈	—	—	—	0	—	—
x S_7	S ₅	—	S ₈	(S ₇)	—	—	—	—	1
S_8	—	S ₆	(S ₈)	S ₂	—	—	—	0	—

Mealy merged :

		00	01	11	10	Z			
		00	01	11	10	00	01	11	10
(S_0, S_1)	(S ₀)	(S ₁)	S ₃	S ₂	—	0	0	—	—
(S_2, S_6)	S ₀	(S ₆)	S ₈	(S ₂)	—	—	0	—	0
S_3	—	S ₆	(S ₃)	S ₄	—	—	—	0	—
S_4	S ₅	—	S ₈	(S ₄)	—	—	—	—	0
(S_5, S_7)	(S ₅)	S ₆	S ₈	(S ₇)	—	0	—	—	1
S_8	—	S ₆	(S ₈)	S ₂	—	—	—	0	—

5. $001000 = d \rightarrow a, f \rightarrow b$

$01 = ag \rightarrow c, b, e \rightarrow d$

$11 = b \rightarrow a, f, c \rightarrow e, d \rightarrow g$

$10 = a, c, e \rightarrow b, g \rightarrow f$

$(a, d)_x, (b, f)_x, (a, g, c)_x, (b, d, e)_x$

$(a, b)_x, (f, c, e)_x, (d, g)_x, (a, b, c, e)_x, (f, g)_x$

a	d
b	e
f	c
x	g

Assignment :

$a = 000$

$b = 001$

$c = 111$

$d = 001$

$e = 011$

$f = 110$

$g = 101$

$x = 100$

	00	01	11	10	00	01	11	10
a	Ⓐ	Ⓐ	Ⓐ	b	01	10	10	00
b	Ⓑ	e	a	Ⓑ	01	11	10	00
c	Ⓒ	Ⓒ	e	e	11	10	00	00
d	a	Ⓓ	g	-	01	11	01	-
e	-	d	Ⓔ	b	-	11	00	00
f	b	-	c	Ⓕ	01	-	00	11
g	-	c	Ⓖ	x	-	10	01	11
x	-	g	-	f	-	10	-	11