

97
100

BENMEI CHEN

$$(20) \quad 1. \quad |H(j\omega)|^2 = \frac{1}{1+\omega^6}$$

Find the minimum phase function, $H(s)$.

- (60) 2. Realize the following DP functions by LC networks of the form indicated.
If the function is not realizable, clearly state the reasons.

a) Foster's 1st Form

$$(i) \quad Z(s) = \frac{s^3 + 10s^2}{s^2 + 4} \quad , \quad (ii) \quad Y(s) = \frac{s^2 + 2s + 1}{s^3 + s}$$

b) Cauer's 1st Form

$$(i) \quad Y(s) = \frac{s^3 + s}{s^4 + 5s^2 + 6} \quad , \quad (ii) \quad Z(s) = \frac{2s^2 + 16}{s^3 + 16s}$$

c) Cauer's 2nd Form

$$(i) \quad Z(s) = \frac{s^3 + 2s^2}{s^4 + 2s^2 + 1} \quad , \quad (ii) \quad Y(s) = \frac{s^2 + 1}{s^3 + 2s}$$

- (20) 3. Determine which of the following are realizable RC DP functions. If not, clearly state the reason.

a) $Z(s) = \frac{s^3 + 6s^2 + 8s}{s^2 + 4s + 3}$

b) $Z(s) = \frac{s^2 + 4s + 3}{s^2 + 6s + 8}$ not

c) $Y(s) = \frac{s^2 + 2s + 0.75}{s^2 + 3s + 2}$

d) $Y(s) = \frac{s^3 + 5s^2 + 6s}{s^2 + 5s + 4}$

$$1. \quad (1) \quad \frac{C(s)}{D(s)} \triangleq |H(j\omega)|^2 \Big|_{\omega=\frac{s}{j}} = \frac{1}{1+\omega^6} \Big|_{\omega=\frac{s}{j}} = \frac{1}{1-s^6} = \frac{-1}{s^6-1}$$

$$(2) \quad C(s) = -1 \quad \Rightarrow \quad A(s) = 1$$

$$(3) \quad D(s) = s^6 - 1 = (s-1)(s^5 + s^4 + s^3 + s^2 + s + 1) =$$

$$= (s-1)(s+1)(s-0.5-j\frac{\sqrt{3}}{2})(s-0.5+j\frac{\sqrt{3}}{2})(s+0.5-j\frac{\sqrt{3}}{2})(s+0.5+j\frac{\sqrt{3}}{2})$$

$$B(s) = (s+1)(s+0.5-j\frac{\sqrt{3}}{2})(s+0.5+j\frac{\sqrt{3}}{2})$$

$$= (s+1)(s^2 + s + 1) = (s^3 + 2s^2 + 2s + 1)$$

$$\therefore H(s) = \frac{1}{(s^3 + 2s^2 + 2s + 1)}$$




2. a) FOSTER'S 1st FORM

$$(i) Z(s) = (s^3 + 10s) / (2s^2 + 4)$$

$$\frac{Z(s)}{s} \Big|_{s^2=p} = \frac{p+10}{2p+4} = \frac{\frac{1}{2}(2p+4) + 8}{2p+4} = \frac{1}{2} + \frac{4}{p+2}$$
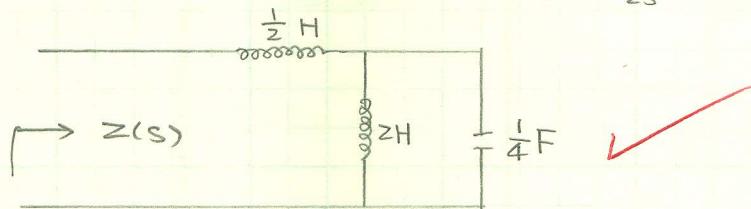
$$Z(s) = \frac{1}{2}s + \frac{4s}{s^2+2} = \frac{1}{2}s + \frac{1}{\frac{1}{4}s + \frac{1}{2s}}$$



$$(ii) Y(s) = (s^2 + 2s + 1) / (s^3 + s)$$

$$= (s+1)^2 / s(s^2 + 1)$$

$Y(s)$ is unrealizable, Because $Y(s)$ has two zeros at

$s = -1$. (not on $j\omega$ axis also)



b) Cauer's 1st FORM

$$(i) Y(s) = (s^3 + s) / (s^4 + 5s^2 + 6) = s(s+j)(s-j) / (s+j\sqrt{2})(s-j\sqrt{2})(s+j\sqrt{3})(s-j\sqrt{3})$$


$Y(s)$ is unrealizable because the zeros and poles are

$j\sqrt{3}$ (pole), $j\sqrt{2}$ (pole), j (zero), 0 (zero), $-j$ (zero), ...

doesn't satisfy the properties. ✓

$$(ii) Z(s) = (2s^2 + 16) / (s^3 + 16s), \quad Y(s) = (s^3 + 16s) / (2s^2 + 16)$$

$$\begin{array}{r} \frac{1}{2}s \\ \hline 2s^2 + 16 \end{array} \begin{array}{r} \frac{1}{2}s \\ \hline s^3 + 8s \end{array} \begin{array}{r} \frac{1}{4}s \\ \hline 8s \end{array} \begin{array}{r} \frac{1}{2}s \\ \hline 2s^2 + 16 \end{array} \begin{array}{r} \frac{1}{2}s \\ \hline 16 \end{array} \begin{array}{r} \frac{1}{2}s \\ \hline 8s \end{array} \begin{array}{r} \frac{1}{2}s \\ \hline 0 \end{array}$$

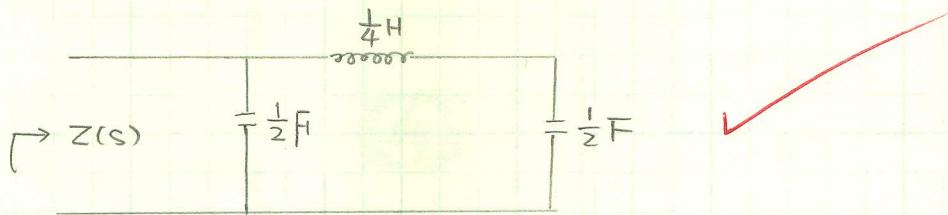

c) Cauer's 2nd FORM

$$(i) Z(s) = (s^3 + 2s) / (s^4 + 2s^2 + 1)$$

$$= s(s^2 + 2) / (s^2 + 1)(s^2 + 1)$$

$Z(s)$ is unrealizable because $Z(s)$ has two poles

at $s = \pm j$. ✓

$$(ii) Y(s) = (s^2 + 1)/(s^3 + 2s)$$

$$\begin{aligned} & \frac{\frac{1}{2s}}{s^3 + 2s} \rightarrow \frac{1}{2s} \\ & \frac{1 + \frac{1}{2}s^2}{\frac{1}{2}s} \quad \frac{\frac{4}{s}}{s^2 + 2s} \rightarrow \frac{1}{\frac{1}{4}s} \\ & \frac{2}{s} \quad \frac{\frac{1}{2s}}{\frac{1}{2}} \rightarrow \frac{1}{2s} \\ & \frac{1}{4F} \quad \text{---} \quad \frac{1}{2s} \end{aligned}$$

ZH 2H

$$3. a) Z(s) = (s^3 + 6s^2 + 8s) / (s^2 + 4s + 3) \stackrel{\Delta}{=} A(s) / B(s)$$

$Z(s)$ is unrealizable because the degree of $A(s) = 3$
 $>$ the degree of $B(s) = 2$. ✓

$$b) Z(s) = (s^2 + 4s + 3) / (s^2 + 6s + 8)$$

$$= (s+1)(s+3) / [(s+2)(s+4)]$$

$Z(s)$ is unrealizable because $2 > 1$ doesn't satisfy the properties of ZRC. ✓

$$c) Y(s) = (s^2 + 2s + 0.75) / (s^2 + 3s + 2)$$

$$= (s+0.5)(s+1.5) / [(s+1)(s+2)]$$

$$Y(s) = (s^2 + 3s + 2) - (s + 1.25) / [s^2 + 3s + 2]$$

$$= 1 - (s + 1.25) / [(s+1)(s+2)]$$

$$= 1 + \frac{-0.25}{s+1} + \frac{-0.75}{s+2} \quad (1 > 0, -0.25 \text{ and } -0.75 < 0)$$

$$Y(s) = 1 + \frac{-0.25}{s+1} + \frac{-0.75}{s+2}$$

$$\frac{dY(s)}{ds} = \frac{0.25}{(s+1)^2} + \frac{0.75}{(s+2)^2} > 0 \quad (\text{except at the poles})$$

so, $Y(s)$ is realizable.

what about poles
and zeros?

$$\begin{aligned}
 3. d) \quad Y(s) &= (s^3 + 5s^2 + 6s) / (s^2 + 5s + 4) \\
 &= s(s^2 + 5s + 6) / (s^2 + 5s + 4) \\
 &= s(s+2)(s+3) / [(s+1)(s+4)]
 \end{aligned}$$

$Y(s)$ is unrealizable because the poles and zeros of $Y(s)$ are like =

-4 (pole), -3 (zero), -2 (zero), -1 (pole), 0 (zero) ✓

doesn't satisfy the properties of YRC.

100

EE 448 ANALOG FILTER DESIGN

Benmei Chen

1 HR. EXAMINATION
DR. R. A. BIRGENHEIER

25 pts each

One Sheet of Notes

(Clearly draw and label a circuit diagram for each problem.)

1. Realize $Y(s)$ by (a) Foster 1st Form, (b) Foster 2nd Form.

$$Y(s) = \frac{s^2 + 4s + 3}{s + 2}$$

2. Realize $H(s)$ by an R-C ladder network.

$$H(s) = \frac{ks}{s^2 + 7s + 10}$$

3. Realize $H(s)$ with a loss-less 2-port network terminated in a 1 ohm load resistance

$$H(s) = \frac{ks^3}{(s + 1)^3}$$

4. Realize $H(s)$ as a loss-less 2-port network terminated at both ends with $R_s = 1\Omega$, $R_L = 2\Omega$. (Carry at least 4 digits.)

$$H(s) = \frac{k}{s^2 + 5s + 4}$$

$$1. \quad Y(s) = \frac{s^2 + 4s + 3}{s + 2}$$


(a) FOSTER'S 1st FORM.

$$\begin{aligned} Z(s) &= \frac{s+2}{s^2 + 4s + 3} = \frac{(s+2)}{(s+1)(s+3)} \\ &= \frac{\frac{1}{s+1}}{\frac{1}{s+3}} + \frac{\frac{1}{s+3}}{\frac{1}{s+1}} \\ &= \frac{1}{2s+2} + \frac{1}{zs+6} \end{aligned}$$

→ $Z(s)$

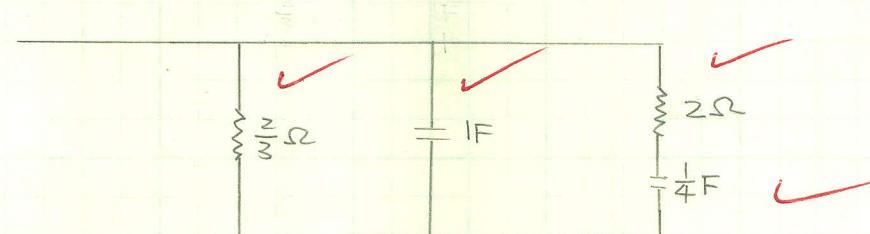(b) FOSTER'S 2nd FORM:

$$\begin{aligned} Y(s) &= \frac{s^2 + 4s + 3}{s + 2} \\ \frac{Y(s)}{s} &= \frac{s^2 + 4s + 3}{s(s+2)} = \frac{s^2 + 4s + 3}{s^2 + 2s} = \frac{(s^2 + 2s) + (2s + 3)}{s^2 + 2s} \\ &= 1 + \frac{2s + 3}{s^2 + 2s} = 1 + \frac{2s + 3}{s(s+2)} = 1 + \frac{\frac{2}{s}}{s} + \frac{\frac{3}{s}}{s+2} \\ Y(s) &= s + \frac{3}{2} + \frac{\frac{2}{s}}{s+2} = s + \frac{3}{2} + \frac{1}{z + \frac{1}{4}s} \end{aligned}$$



$$2. \quad H(s) = \frac{ks}{(s^2 + 7s + 10)}$$

$$\text{LET } Z_{11}(s) = \frac{(s+2)(s+5)}{(s+1)(s+4)}, \quad Z_{12} = \frac{ks}{s^2 + 7s + 10}$$


$$= \frac{s^2 + 7s + 10}{s^2 + 5s + 4}$$

$$\begin{array}{r} 1 \\ s^2 + 5s + 4 \sqrt{s^2 + 7s + 10} \\ \hline s^2 + 5s + 4 \\ \hline 2s + 6 \end{array} \quad \begin{array}{r} \frac{1}{2}s \\ s^2 + 5s + 4 \sqrt{s^2 + 3s} \\ \hline s^2 + 3s \\ \hline 2s + 4 \end{array}$$

$$Z_{11}(s) = 1 + \frac{1}{\frac{1}{2}s + \frac{2s+4}{2s+6}}$$

$$Y'(s) = \frac{2s+4}{2s+6}$$
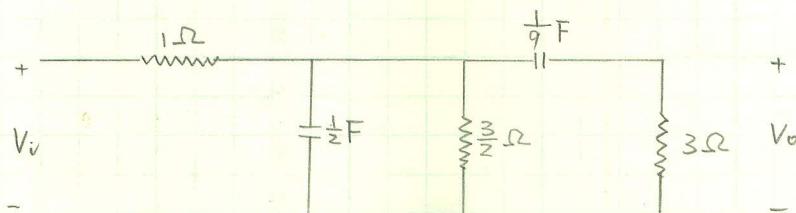
$$\begin{array}{r} \frac{2}{3} \\ 6 + 2s \sqrt{4 + 2s} \\ \hline 4 + \frac{4}{3}s \\ \hline \frac{2}{3}s \end{array} \quad \begin{array}{r} 9/s \\ \sqrt{6 + 2s} \\ \hline 6 \\ \hline 2 \end{array} \quad \begin{array}{r} \frac{1}{3} \\ \sqrt{\frac{2}{3}} \\ \hline \frac{2}{3} \\ \hline 0 \end{array}$$




$$3. \quad H(s) = \frac{ks^3}{(s+1)^3} = \frac{ks^3}{(s^3 + 3s^2 + 3s + 1)}$$

$$= \frac{\frac{ks^3}{(3s^2 + 1)}}{1 + \frac{(s^3 + 3s^2 + 3s + 1)}{(3s^2 + 1)}}$$

$$\text{LET } Y_{22}(s) = \frac{s^3 + 3s}{3s^2 + 1} \quad Y_{12} = -\frac{ks^3}{3s^2 + 1}$$

$$\text{LET } Z(s) = \frac{1}{Y_{22}(s)} = \frac{3s^2 + 1}{s^3 + 3s}$$
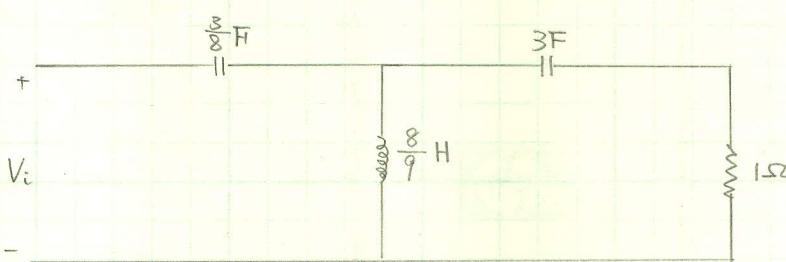
$$\begin{array}{c} \frac{1}{3s} \\ 3s + s^3 \sqrt{1 + 3s^2} \\ \hline 1 + \frac{1}{3}s^2 \\ \hline \frac{1}{3}s \\ \hline \end{array} \quad \begin{array}{c} \frac{9}{8s} \\ \hline 3 + s^2 \\ \hline 3 \\ \hline s \\ \hline \frac{8}{3s} \\ \hline \frac{8}{3s} \\ \hline 0 \end{array}$$



$$4. H(s) = \frac{k}{(s^2 + 5s + 4)} , R_s = 1\Omega , R_L = 2\Omega$$

$$H(0) = \frac{R_L}{R_L + R_s} = \frac{2}{3} = \frac{k}{4} , k = \frac{8}{3}$$

$$(1) P(s) P(-s) = 1 - \frac{4}{R_s} H(s) H(-s)$$

$$= 1 - 2 \cdot \frac{k^2}{(s^2 + 5s + 4)(s^2 - 5s + 4)}$$

$$= \frac{s^4 - 17s^2 + 16 - 2 \times \frac{64}{9}}{(s^2 + 5s + 4)(s^2 - 5s + 4)}$$

$$= \frac{s^4 - 17s^2 + 1.77778}{(s^2 + 5s + 4)(s^2 - 5s + 4)}$$

$$= \frac{(s+4.11033)(s+0.32439)(s-4.11033)(s-0.32439)}{(s^2 + 5s + 4)(s^2 - 5s + 4)}$$

$$= \frac{(s^2 + 4.43472s + 1.33335)(s^2 - 4.43472s + 1.33335)}{(s^2 + 5s + 4)(s^2 - 5s + 4)}$$

$$\text{LET } P(s) = \frac{s^2 + 4.43472s + 1.33335}{s^2 + 5s + 4}$$

$$(2) Z_{in1}(s) = \frac{1 + P(s)}{1 - P(s)} = \frac{zs^2 + 9.43472s + 5.33335}{0.56528s + 2.66665}$$

$$Z_{in2}(s) = \frac{1 - P(s)}{1 + P(s)} = \frac{0.56528s + 2.66665}{2s^2 + 9.43472s + 5.33335}$$

$$Z_{in}(0) = R_s = 2 , Z_{in1}(0) = 2 , Z_{in2}(0) = 0.5$$


$$\therefore Z_{in}(s) = Z_{in1}(s)$$

$$= \frac{zs^2 + 9.43472s + 5.33335}{0.56528s + 2.66665}$$

$$\begin{array}{r} 3.538078 \\ 0.56528s + 2.66665 \sqrt{z^2 s^2 + 9.43472s + 5.33335} \\ \hline z^2 s^2 + 9.43472s \\ 5.33335 \end{array}$$

$$\begin{array}{r} 0.10599s \\ 0.56528s + 2.66665 \sqrt{0.56528s} \\ \hline 0.56528s \end{array}$$
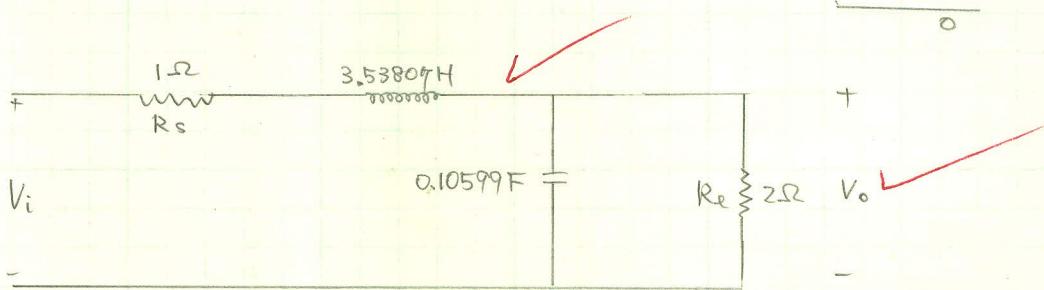
$$\begin{array}{r} 2 \\ 2.66665 \sqrt{\frac{5.33335}{5.33335}} \\ \hline 0 \end{array}$$



One Sheet of Notes

Points

- 30 1. Determine the (a) order, (b) pole locations, (c) $H(s)$ (in factored form) for a Butterworth filter that satisfies the following specifications:
- $R_s = 1 \text{ ohm}$, $R_L = .5 \text{ ohms}$.
 - Passband attenuation
 $<0.5 \text{ dB}, |\omega| < 0.8 \text{ rps}$
 - Stopband attenuation
 $> 40 \text{ dB}, |\omega| > 3.0 \text{ rps}$
- 30 2. Determine the (a) order, (b) pole locations, (c) $H(s)$ (in factored form) for a Chebyshev filter that satisfies the following specifications:
- $R_s = 1 \text{ ohm}$, $R_L = 1.5 \text{ ohms}$
 - Passband attenuation
 $<0.5 \text{ dB}, |\omega| < 1.0 \text{ rps}$
 - Stopband attenuation
 $> 40 \text{ dB}, |\omega| > 3.0 \text{ rps}$
- 30 3. Realize a 2nd order Bessel low-pass filter for which $\tau(0) = 0.5$ seconds, $R_s = 1 \text{ ohm}$ and $R_L = 2 \text{ ohms}$. i.e., find (a) $H(s)$, (b) $\rho(s)$, (c) $Z_{in}(s)$, (d) realization (clearly draw circuit diagram - use 5 significant figures).
- 10 4. Find the transfer function, $H(s)$, for a transitional filter obtained from Butterworth and Bessel filters with the following pole locations:
- Butterworth pole locations: $-.7071 \pm j.7071$
- Bessel pole locations: $-1.5 \pm j0.866$
- (be sure to normalize the Bessel poles so that they are on the unit circle).

CHAPTER 8

$$\text{BUTTERWORTH: } |H(j\omega)|^2 = B_n(\omega) = \frac{1}{1 + \omega^{2n}}$$

$$\text{POLES: } S_k = -\sin\theta_k + j\cos\theta_k \quad ; \quad \theta_k = \frac{2k-1}{2n} \pi, \quad k=1, 2, 3, \dots, n$$



$$\begin{aligned} H(s) &= H(s) = \prod_{k=1}^{n/2} \frac{1}{s^2 + (2\sin\theta_k)s + 1} \quad n \text{ is even} \\ H(s) &= \left[\prod_{k=1}^{(n-1)/2} \frac{1}{s^2 + (2\sin\theta_k)s + 1} \right] \cdot \frac{1}{(s+1)} \end{aligned}$$

$$\text{CIR. REALIZ.: } \lambda = \left(\frac{R_L - 1}{R_L + 1} \right)^{1/n} \quad \text{or} \quad \lambda = \left(\frac{1 - R_L}{R_L + 1} \right)^{1/n}$$

$$\alpha_i = 2\sin \frac{\pi i}{2n}, \quad \beta_i = 2\cos \frac{\pi i}{2n}, \quad \tilde{C}_1 = \frac{\alpha_1}{R_L(1-\lambda)}, \quad \hat{L}_1 = \frac{\alpha_1 R_L}{1-\lambda}$$

$$\tilde{C}_{2m-1} \tilde{L}_{2m} \{ \hat{L}_{2m-1} \hat{C}_{2m} \} = \frac{\alpha_{4m-3} \alpha_{4m-1}}{1 - \lambda \beta_{4m-2} + \lambda^2}$$
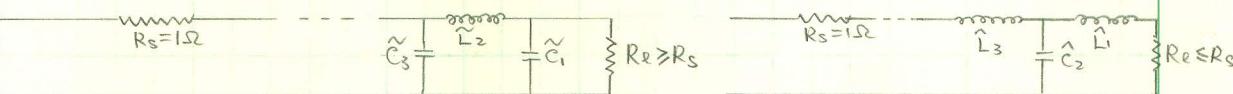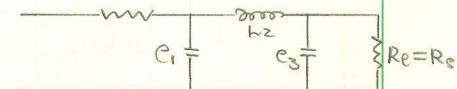
$$\tilde{C}_{2m+1} \tilde{L}_{2m} \{ \hat{L}_{2m+1} \hat{C}_{2m} \} = \frac{\alpha_{4m-1} \alpha_{4m+1}}{1 - \lambda \beta_{4m} + \lambda^2}$$




$$\text{CHEBYSHEV: } T_n(\omega) = \begin{cases} \cos(n \cos^{-1} \omega) & |\omega| \leq 1 \\ \cosh(n \cosh^{-1} \omega) & |\omega| \geq 1 \end{cases}$$

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)}, \quad \epsilon = \sqrt{10^{(A_{\max} \text{ dB}/10)} - 1}$$

$$\text{POLES: } S = -\sinh \left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right] \sin \frac{2k-1}{2n} \pi + \cosh \left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right] \cos \frac{2k-1}{2n} \pi, \quad k=1, 2, \dots, n$$
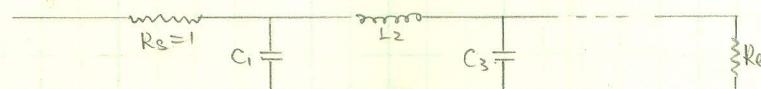
$$\text{CIR: } a = \frac{4R_L}{(R_L + 1)^2} \quad \text{WHEN } n \text{ is odd.} \quad a = \frac{4R_L}{(R_L + 1)^2} [1 + \epsilon^2] \leq 1 \quad \text{WHEN } n \text{ is even.}$$



$$\text{BESSEL: } H(s) = \frac{k}{B_n(\tau_0 s)}, \quad \tau_0 = \tau(0), \quad \hat{B}_n(s) = (2n-1) \hat{B}_{n-1}(s) + s^2 \hat{B}_{n-2}(s)$$

$$\hat{B}_1(s) = s+1, \quad \hat{B}_2(s) = s^2 + 3s + 3, \quad \hat{B}_3(s) = s^3 + 6s^2 + 15s + 15, \quad \hat{B}_4(s) = s^4 + 10s^3 + 45s^2 + 105s + 105$$


TRANSITIONAL: POLES = $\frac{1}{2}$ (POLES OF BUTT. + POLES OF BESSEL)

DARLINGTON REALIZATION:

$$(1) \quad p(s)p(-s) = 1 - \frac{4}{R_L} H(s)H(-s)$$

$$(2) \quad Z_{in}(s), \quad Z_{in}(0) = R_L$$

(3) LONG DIVISION GET

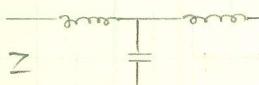

$$1. \quad |H(j\omega)|^2 = \frac{1}{1+\omega^{2n}}$$

$$|H(j\omega)|_{dB} = -10 \log(1 + \omega^{2n})$$

$$\text{ii)} \quad -10 \log(1 + 0.8^{2n}) < 0.5$$


$$0.8^{2n} < 0.1220 \quad \Rightarrow \quad n \geq 4.7135 \quad \therefore n \geq 5$$

$$\text{iii)} \quad -10 \log(1 + 3^{2n}) > 40$$

$$3^{2n} > 9999 \quad \Rightarrow \quad n \geq 4.1918 \quad \therefore n \geq 5$$

(a) THE MINIMUM ORDER = 5 ✓

(b)

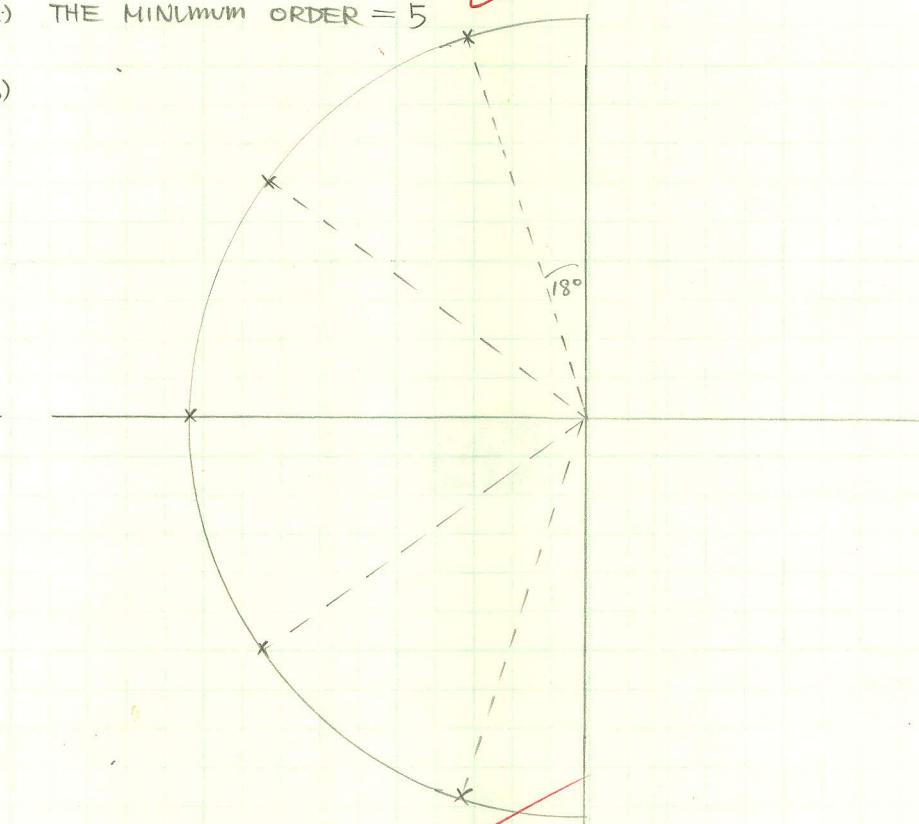

$$S_1, 2 = -0.3090 \pm j0.9511 \quad , \quad S_3, 4 = -0.8090 \pm j0.5878 \quad , \quad S_5 = -1$$

$$(c) \quad H(s) = \frac{1}{(s+1)(s^2 + 0.6180s + 1)(s^2 + 1.6180s + 1)}$$

2. $T_n(\omega) = \begin{cases} \cos(n \cos^{-1}\omega) & |\omega| \leq 1 \\ \cosh(n \cosh^{-1}\omega) & |\omega| \geq 1 \end{cases}$

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)}$$

$$|H(j\omega)|_{dB} = -10 \log(1 + \epsilon^2 T_n^2(\omega))$$

ii) Passband attenuation $< 0.5 \text{ dB}$ $|\omega| < 1.0 \text{ rad/s}$

FOR CHERYSHEV FILTER, THIS MEANS $A_{max} < 0.5 \text{ dB}$

$$\epsilon \leq \sqrt{10^{0.5/10} - 1} = 0.3493$$

iii) $10 \log(1 + 0.3493^2 T_n^2(3.0)) > 40$

$$T_n(3.0) > 286.2632$$

$$\cosh(n \cosh^{-1} 3.0) > 286.2632 \Rightarrow n > 3.6024 \Rightarrow n \geq 4$$

(a) MINIMUM ORDER = 4

$$(b) S_k = -\sinh\left[\frac{1}{4} \sin^{-1} \frac{1}{0.3493}\right] \sin \frac{zk-1}{2n} \pi + \cosh\left[\frac{1}{4} \sinh^{-1} \frac{1}{0.3493}\right] \cos \frac{zk-1}{2n} \pi$$

$$= -0.4582 \sin \frac{zk-1}{8} \pi + 1.1000 \cos \frac{zk-1}{8} \pi \quad k=1, 2, 3, 4$$

$$S_{1,4} = -0.1753 \pm j1.0163 \quad S_{2,3} = -0.4233 \pm j0.4210$$

(c)

$$H(s) = \frac{1}{(s + 0.1753 + j1.0163)(s + 0.1753 - j1.0163)(s + 0.4233 + j0.4210)(s + 0.4233 - j0.4210)}$$

$$= \frac{1}{(s^2 + 0.3506s + 1.0636)(s^2 + 0.8466s + 0.3564)}$$

3. FROM 'SHEET' : $\hat{B}_z(s) = s^2 + 3s + 3$

$$\begin{aligned}
 (a) \quad H(s) &= \frac{k}{B_z(\tau(0)s)} \\
 &= \frac{k}{(0.5s)^2 + 3(0.5s) + 3} \\
 &= \frac{k}{0.25s^2 + 1.5s + 3} \quad k=3 \\
 &= \frac{k'}{s^2 + 6s + 12}
 \end{aligned}$$

$$(b) \quad H(0) = \frac{R_e}{R_s + R_e} = \frac{z}{1+z} = \frac{k'}{12} \Rightarrow k' = 8$$


$$\begin{aligned}
 p(s)p(-s) &= 1 - \frac{4}{2} H(s)H(-s) \\
 &= 1 - \frac{128}{(s^2 + 6s + 12)(s^2 - 6s + 12)} \\
 &= \frac{s^4 - 12s^2 + 16}{(s^2 + 6s + 12)(s^2 - 6s + 12)} \\
 &= \frac{(s^2 + 4.47214s + 4)(s^2 - 4.47214s + 4)}{(s^2 + 6s + 12)(s^2 - 6s + 12)}
 \end{aligned}$$

$$\therefore p(s) = \frac{s^2 + 4.47214s + 4}{(s^2 + 6s + 12)}$$

$$(c) \quad Z_{in}(s) = \frac{1 + p(s)}{1 - p(s)} = \frac{2s^2 + 10.47214s + 16}{1.52786s + 8}$$

$$Z_{in}(0) = 2 = R_e$$

$$\begin{array}{r}
 (d) \quad \frac{1.30902s}{1.52786s + 8} \quad | \quad \frac{1.30902s}{2s^2 + 10.47214s + 16} \\
 \underline{-} \quad \frac{1.30902s}{2s^2 + 10.47216s} \\
 \hline
 16
 \end{array}
 \quad \begin{array}{r}
 0.09549s \\
 \sqrt{1.52786s + 8} \\
 \underline{-} \quad \frac{1.52786s}{1.52786s} \\
 \hline
 8
 \end{array}
 \quad \begin{array}{r}
 z \\
 \sqrt{\frac{16}{16}} \\
 \hline
 0
 \end{array}$$

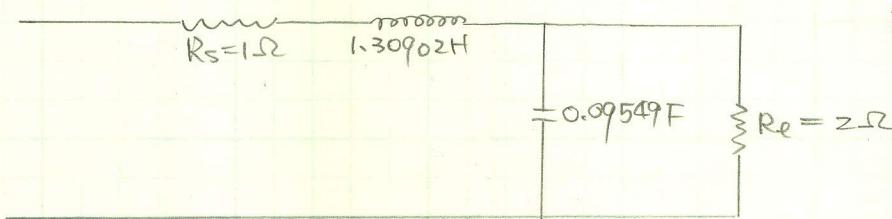

4.

X POLES OF TRANSITIONAL FILTER

$$s_{1,2} = -\frac{0.7071 + 1.5}{2} \pm j \frac{0.7071 + 0.866}{2}$$

$$= -1.10355 \pm j 0.78655$$

$$H(s) = \frac{k}{(s + 1.10355 + j 0.78655)(s + 1.10355 - j 0.78655)}$$

$$= \frac{k}{s^2 + 2.20710s + 1.83648}$$

(2) ✓ THE NORMALIZE BESSSEL POLES:

$$= -0.866 \pm 0.5$$

POLES OF TRAN. FILTER:

$$s_{1,2} = -\frac{0.866 + 0.7071}{2} \pm j \frac{0.7071 + 0.5}{2}$$

$$= -0.78657 \pm j 0.60355$$

SO,

$$H(s) = \frac{k}{(s + 0.78657 - j 0.60355)(s + 0.78657 + j 0.60355)}$$

$$= \frac{0.98176}{s^2 + 1.57314 + 0.98176}$$

172
200

Bennie Chen

OPEN NOTES

50 points each

1. Consider a LPF to meet the following specifications:

- (i) Maximally-flat passband response.
- (ii) 3dB cut-off frequency: $f_c = 15 \text{ KHz}$
- (iii) Stopband Attenuation: >20 dB for $f > 37.5 \text{ KHz}$
- (iv) $R_s = R_L = 1 \text{ K ohm}$

Determine (a) minimum order n; (b) $H(s)$; (c) realization (start with a normalized LP prototype).

2. Consider a HPF to meet the following specifications:

- (i) Maximum passband ripple: 0.25 dB for $f > 120 \text{ KHz}$
- (ii) Minimum stopband attenuation: >50 dB for $f < 30 \text{ KHz}$
- (iii) $R_s = R_L = 300 \text{ ohms}$

Determine (a) minimum order n; (b) $H(s)$; (c) realization (start with a normalized LPF prototype). *CHB*

3. Consider a Butterworth BPF to meeth the following specifications:

- (i) 3 dB bandwidth: 1 MHz
- (ii) Center frequency: 10 MHz
- (iii) Stopband attenuation at least 20 dB $|f| < 5 \text{ MHz}$ and $|f| > 15 \text{ MHz}$
- (iv) $R_s = R_L = 600 \text{ ohms}$,

Determine (a) Q_0 of filter; (b) minimum order n; (c) $H(s)$;
(d) realization (start with a normalized LPF prototype).

4. Consider a Bessel LPF to meet the following specifications:

(i) $\tau(0) = 10^{-6}$ seconds

(ii) $\tau(\omega)$ has less than 2% error for $\omega < 2.5$ Mrps

(iii) $R_s = R_L = 1K \text{ ohm}$

Determine (a) minimum order n; (b) $H(s)$; (c) realization (use filter structure and element values given below).

I. First, consider the condition (ii)

$$f_c = 15 \text{ kHz} , \quad \omega_c = 2\pi f_c = 30\pi \text{ rad/s}$$

Now, consider condition (iii), THIS means

Stopband Attenuation = > 20dB for $\omega > 2.5 \text{ rad/s}$

WE CAN USE A NORMALIZED LP BUTTERWORTH FILTER (FOR condition (ii))

$$|H(j\omega)|^2 = \frac{1}{1 + \omega^{2n}}$$

$$|H(j\omega)|_{\text{dB}} = -10 \log(1 + \omega^{2n})$$

$$\therefore -10 \log(1 + 2.5^{2n}) > 20 \Rightarrow n > 2.50746$$

SO, (a) minimum order $n = 3$ ✓

(b) TRANSF. FUN. OF THE NORMALIZED FILTER: $\theta_1 = \frac{\pi}{6}$

$$H_N(s) = \frac{1}{(s+1)(s^2 + 2s \sin \theta_1 s + 1)} = \frac{1}{(s+1)(s^2 + 8 + 1)} = \frac{1}{s^3 + 2s^2 + 8s + 1}$$


$$\text{SO, } H(s) = \frac{1}{(\frac{s}{\omega_c})^3 + 2(\frac{s}{\omega_c})^2 + 2(\frac{s}{\omega_c}) + 1}$$

$$= \frac{\omega_c^3}{s^3 + 2\omega_c s^2 + 2\omega_c^2 s + \omega_c^3}$$


$$= \frac{(30\pi \times 10^3)^3}{s^3 + 2 \times 30\pi \times 10^3 s^2 + 2 \times (30\pi \times 10^3)^2 s + (30\pi \times 10^3)^3}$$

$$= \frac{8.37169 \times 10^{14}}{s^3 + 188495.5592 s^2 + 1.79653 \times 10^{16} s + 8.37169 \times 10^{14}} \checkmark$$


(c) THE LP REALIZ. CIRCUIT:

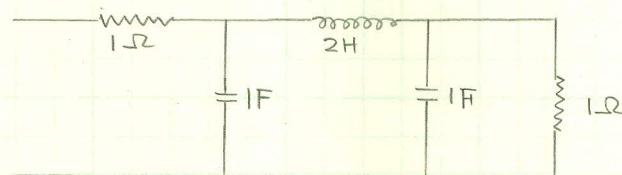

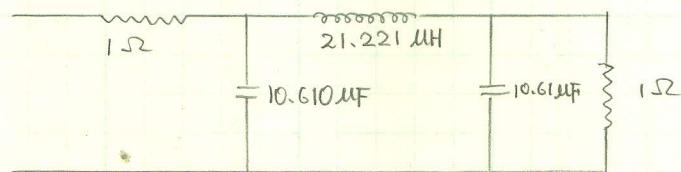NOW SCALING TO THE 3dB AT $\omega_c = 30\pi \text{ K rad/s}$



AND THEN, IMPEDANCE SCALING BY 1000

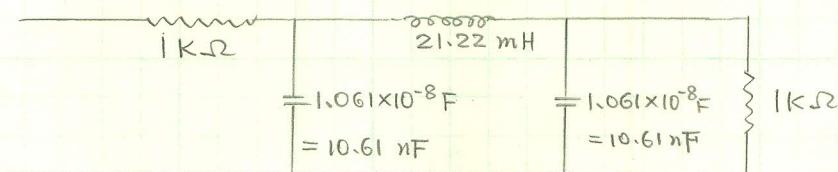

THIS IS THE REALIZATION WE NEED.

2. FIRST, LET US BUILD A HPF TO MEET THE FOLLOWING CONDITIONS:

- (i)' Maximum passband ripple = 0.25 dB FOR $\omega = 1 \text{ rad/s}$
- (ii)' Minimum Stopband atten. = > 50 dB FOR $\omega < 0.25 \text{ rad/s}$

USING FREQ. SCALING $K_f = 120 \times 2\pi \times 10^3 = 240\pi \times 10^3$, THE CONDITIONS

(i)' and (ii)' WILL BE THE SAME AS CON. (i),(ii)

THEN, WE CONSIDER. CHEBYSHEV. LPF WITH

- (i)'' Maximum passband ripple = 0.25 dB FOR $\omega = 1 \text{ rad/s}$
- (ii)'' Minimum Stopband atten. = > 50 dB FOR $\omega > 4 \text{ rad/s}$

$$\epsilon = \sqrt{10^{0.25} - 1} = 0.2434$$

$$|H(j\omega)|_{dB} = -10 \log(1 + \epsilon^2 T_n^2(\omega))$$

$$10 \log(1 + \epsilon^2 T_n^2(4)) > 50 \Rightarrow T_n(4) > 1299.0923$$

$$T_n(4) = \cosh(n \cosh^{-1} 4) > 1299.0923 \Rightarrow n > 3.8104$$

SO, (a) minimum order = 4

$$\text{POLES OF NOR. CHEB. LPF} = -0.5553 \sin \frac{\frac{2k-1}{8}\pi}{j} + j 1.1439 \cos \frac{\frac{2k-1}{8}\pi}{j}$$

$$S_{1,4} = -0.2125 \pm j 1.0568, \quad S_{2,3} = -0.5130 \pm j 0.4378$$

$$H_N(s) = \frac{1}{(s^2 + 0.4250s + 1.1620)(s^2 + 1.0260s + 0.4548)}$$


$$H_{HP,N}(s) = H_N(\frac{1}{s}) = \frac{s^4}{(1.1620s^2 + 0.4250s + 1)(0.4548s^2 + 1.0260s + 1)}$$

$$H(s) = H_{HP, \text{SCALED}} = H_{HP,N}(\frac{s}{\omega_p}) = \frac{(s/240\pi \times 10^3)^4}{(1.1620/(240\pi \times 10^3)s^2 + 0.4250/(240\pi \times 10^3)s + 1)}$$

$$\times \frac{1}{(0.4548/(240\pi \times 10^3)s^2 + 1.0260/(240\pi \times 10^3)s + 1)}$$


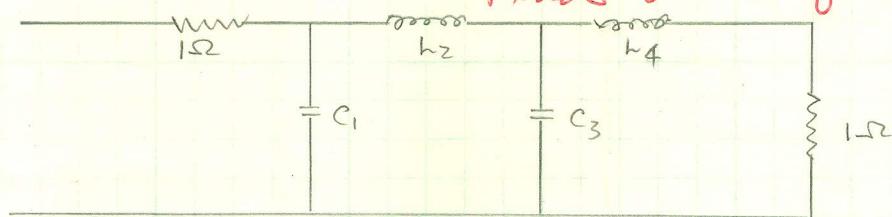
(c) NORMALIZED CHEB. LPF CIR. =

need 5th order
Find values of normalized
LPF



-15

THEN HP NOR. CHEB: CIR. =

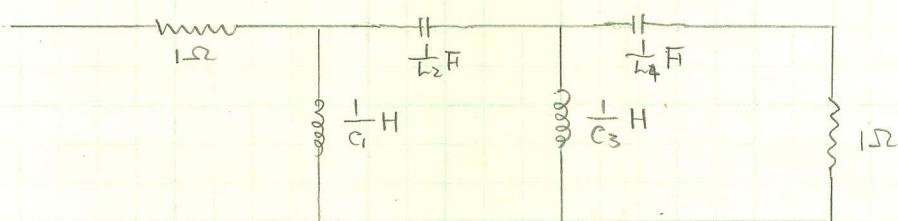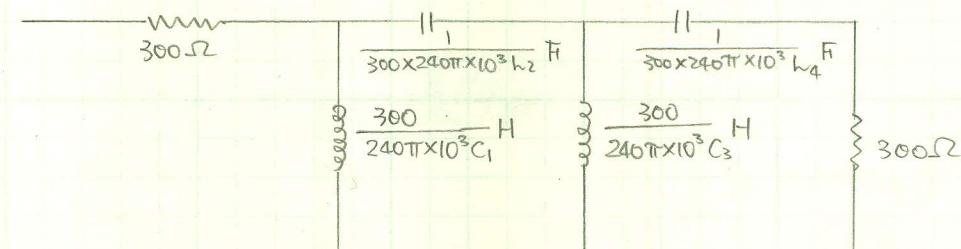SALING TO $k_f = 240\pi \times 10^3$, $A = 300$ 

$$3. \quad B = 1 \text{ MHz} \rightarrow 2\pi M \text{ rad/s} = 2\pi \times 10^6 \text{ rad/s}$$

$$\omega_0 = 10 \text{ MHz} \rightarrow \omega_0 = 2\pi \times 10 \times 10^6 = 2\pi \times 10^7 \text{ rad/s}$$

$$(a) \quad Q_0 = \frac{\omega_0}{B} = \frac{2\pi \times 10^7}{2\pi \times 10^6} = 10$$

$$(b) \quad \text{FROM LPF TO BPF, THE FREQ. } s \cdot 1 \longrightarrow \frac{s^2 + \omega_0^2}{BS}$$

SO, WE HAVE

$$\omega_{LP} = \frac{\omega_{BP}^2 - \omega_0^2}{B \omega_{BP}}$$

$$f_{1,BP} = 5 \text{ MHz}, \omega_{1,BP} = 2\pi \times 5 \times 10^6 \text{ rad/s} \Rightarrow \omega_{LP1} = -15 \text{ rad/s}$$

$$f_{2,BP} = 15 \text{ MHz}, \omega_{2,BP} = 2\pi \times 15 \times 10^6 \text{ rad/s} \Rightarrow \omega_{LP2} = 8.3333 \text{ rad/s}$$

Condition (iii) is same as

Slopband attnu. > 20dB WHEN $\omega > 8.3333 \text{ rad/s}$ FOR LP


$$10 \log (1 + (8.3333)^{2n}) > 20 \quad n > 1.0836$$

minimum order = 2

$$(c) \quad \text{NORMAL. BUTT. LP} \quad H(s) = \frac{1}{s^2 + \omega_0^2 s + 1}$$

$$BP = H(s) = \frac{1}{(\frac{s^2 + 2\pi \times 10^7}{2\pi \times 10^6 s})^2 + \sqrt{2}(\frac{s^2 + 2\pi \times 10^7}{2\pi \times 10^6 s}) + 1} \quad -5$$

(d) NORM. BUTT. LP = CIR. REAL. AS BELOW

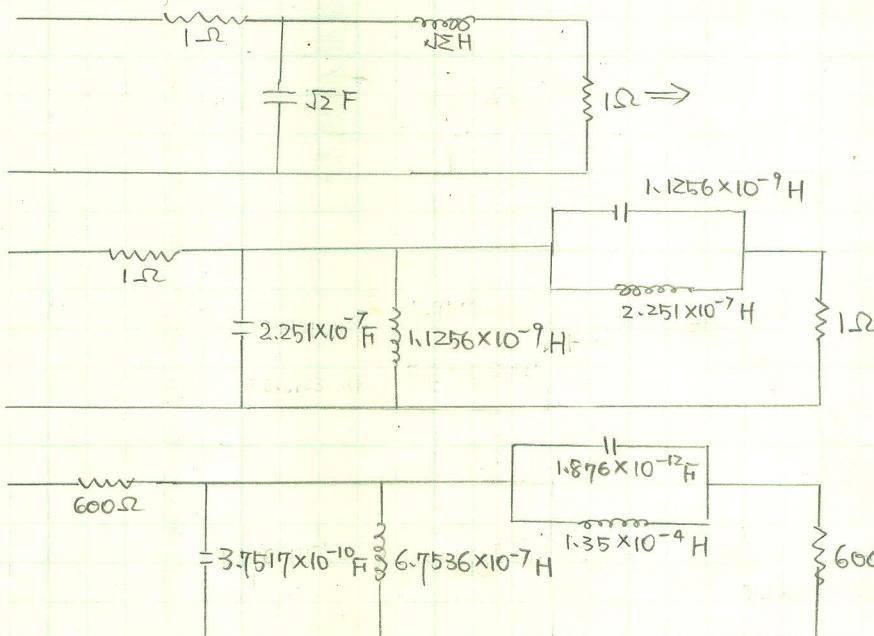

ANSWER!!

4. condition (ii) is same as

$T(\omega)$ has less than 2% error for $\omega < 2.5 \times 10^6 \times \tau(0) = 2.5 \text{ rps}$

LOOKING AT THE FIG 8-21, WE FIND THAT

(a) minimum order = 5

$$(b) \hat{B}_3(s) = s^3 + 6s^2 + 15s + 15$$

$$\hat{B}_4(s) = s^4 + 10s^3 + 45s^2 + 105s + 105$$

$$\hat{B}_5(s) = q\hat{B}_4(s) + s^2\hat{B}_3(s)$$


$$= q(s^4 + 10s^3 + 45s^2 + 105s + 105) + s^2(s^3 + 6s^2 + 15s + 15)$$

$$= s^5 + 15s^4 + 105s^3 + 420s^2 + 945s + 945$$


$$H(s) = \frac{k}{\hat{B}_5(10^{-6}s)}$$

$$= \frac{k}{(10^{-6}s)^5 + 15 \times (10^{-6}s)^4 + 105 \cdot (10^{-6}s)^3 + 420 \cdot (10^{-6}s)^2 + 945 \cdot (10^{-6}s) + 945}$$

(c) NORMAL CIR.:

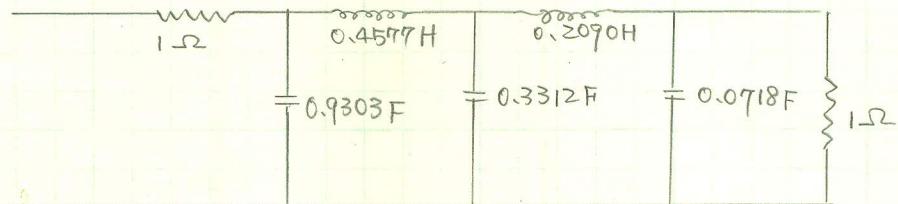

CIR. WITH $R_S = R_L = 1\text{ k}\Omega$

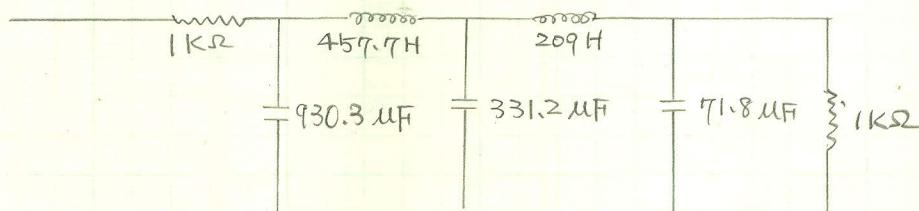

freq. scale

-8