

Analog and Digital Filter

E-E 448

Instructor:

Dr. R. A. Birgenheier

Fall 1986

Homework and Tests

Benmei Chen

42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-383 200 SHEETS 5 SQUARE
MADE IN U.S.A.



3-5C

$$R(\omega) = (4\omega^2 + 160) / (\omega^2 + 16)$$

$$M(s) = R(\omega) \Big|_{\omega = \frac{s}{j}} = (-4s^2 + 160) / (-s^2 + 16)$$

$$C(s) \triangleq -4s^2 + 160$$

$$D(s) \triangleq -s^2 + 16$$

40
50

$$1) D(s) = -s^2 + 16 = (s+4)(-s+4)$$

$$B(s) = s+4$$

$$M_2(s) = 4$$

$$N_2(s) = s$$

$$2) A(s) = a_0 + a_1s + a_2s^2 + a_3s^3$$

$$M_1(s) = a_0 + a_2s^2$$

$$N_1(s) = a_1s + a_3s^3$$

$$3) M_1(s)M_2(s) - N_1(s)N_2(s) = 4a_0 + 4a_2s^2 - a_1s^2 - a_3s^4 = C(s)$$

$$4a_0 + (4a_2 - a_1)s^2 - a_3s^4 = -4s^2 + 160$$

$$a_0 = 40, a_3 = 0, 4a_2 - a_1 = -4$$

In this problem, we are not able to determine the exact values of a_1 and a_2 . Assume $a_1 = 4, a_2 = 0$

$$F(s) = (4s + 40) / (s + 4) \quad (\text{minimum phase function})$$

$$\text{CHECK: } R(\omega) = \text{Re} \{ F(s) \Big|_{s=j\omega} \} = (4\omega^2 + 160) / (\omega^2 + 16)$$

Let $a_1 = 35.36, a_2 = 7.84$, we obtain

$$F(s) = (7.84s^2 + 35.36s + 40) / (s + 4) \quad (\text{mini-phase, also})$$

$$\text{CHECK: } F(\omega) = F(s) \Big|_{s=j\omega} = (-7.84\omega^2 + 40 + j35.36\omega) / (4 + j\omega)$$

$$= (-7.84\omega^2 + 40 + j35.36\omega)(4 - j\omega) / (\omega^2 + 16)$$

$$= [(4\omega^2 + 160) + j(141.44\omega + 7.84\omega^2 - 40\omega)] / (\omega^2 + 16)$$

CHECKED

3-6e

$$X(\omega) = (-3\omega^3 - \omega) / (\omega^6 + 2\omega^4 + \omega^2 + 36)$$

$$N(s) = jX(\omega) \Big|_{\omega = \frac{s}{j}} = (3s^3 - s) / (-s^6 + 2s^4 - s^2 + 36)$$

$$C(s) \triangleq 3s^3 - s$$

$$D(s) \triangleq -s^6 + 2s^4 - s^2 + 36$$

$$\begin{aligned} 1) \quad D(s) &= -s^6 + 2s^4 - s^2 + 36 = (-s+2)(s+2)(s^2-2s+3)(s^2+2s+3) \\ &= (-s+2)(s^2-2s+3)(s+2)(s^2+2s+3) \end{aligned}$$

$$B(s) = (s+2)(s^2+2s+3) = s^3 + 4s^2 + 7s + 6$$

$$M_2(s) = 4s^2 + 6$$

$$N_2(s) = s^3 + 7s$$

$$2) \quad A(s) = a_1s + a_0$$

$$M_1(s) = a_0, \quad N_1(s) = a_1s$$

$$\begin{aligned} N_1(s)M_2(s) - N_2(s)M_1(s) &= 4a_1s^3 + 6a_1s - a_0s^3 - 7a_0s \\ &= (4a_1 - a_0)s^3 + (6a_1 - 7a_0)s = C(s) = 3s^3 - s \end{aligned}$$

$$\begin{cases} 4a_1 - a_0 = 3 \\ 6a_1 - 7a_0 = -1 \end{cases} \Rightarrow \begin{cases} a_1 = 1 \\ a_0 = 1 \end{cases}$$

$$3) \quad F(s) = (s+1) / (s^3 + 4s^2 + 7s + 6) \quad \checkmark$$

$$\begin{aligned} \text{CHECK: } F(\omega) &= F(s) \Big|_{s=j\omega} = (j\omega+1) / (-j\omega^3 - 4\omega^2 + j7\omega + 6) \\ &= (j\omega+1) [-4\omega^2 + 6 + j(\omega^3 - 7\omega)] / (\omega^6 + 2\omega^4 + \omega^2 + 36) \\ &= [-\omega^4 + 3\omega^2 + 6 + j(-3\omega^3 - \omega)] / (\omega^6 + 2\omega^4 + \omega^2 + 36) \end{aligned}$$

$$X(\omega) = (-3\omega^3 - \omega) / (\omega^6 + 2\omega^4 + \omega^2 + 36) \quad \checkmark$$

CHECKED!

3-8d

$$\Phi(\omega) = -\tan^{-1}(-3\omega^3 - \omega) / (-\omega^4 + 3\omega^2 + 6)$$

$$\Phi(s) \triangleq \Phi(\omega) \Big|_{\omega = \frac{s}{j}} = -\tan^{-1}(3s^3 - s) / j(-s^4 - 3s^2 + 6)$$

$$\Phi_o(s) = 3s^3 - s$$

$$\Phi_e(s) = -s^4 - 3s^2 + 6$$

$$1) \quad p(s) = \Phi_o(s) + \Phi_e(s) = -s^4 + 3s^3 - 3s^2 - s + 6 = (-s+2)(s+1)(s^2 - 2s + 3)$$

$$2) \quad B(-s) = (-s+2)(s^2 - 2s + 3)$$

$$B(s) = (s+2)(s^2 + 2s + 3) = s^3 + 4s^2 + 7s + 6$$

$$A(s) = s+1$$

$$3) \quad F(s) = (s+1) / (s^3 + 4s^2 + 7s + 6)$$

$$\text{CHECK} = \quad F(\omega) = F(s) \Big|_{s=j\omega} \quad (\text{See } 3-6e)$$

$$= [(-\omega^4 + 3\omega^2 + 6) + j(-3\omega^3 - \omega)] / (\omega^6 + 2\omega^4 + \omega^2 + 36)$$

$$\Phi(\omega) = -\tan^{-1}(-3\omega^3 - \omega) / (-\omega^4 + 3\omega^2 + 6)$$

CHECKED!

you did wrong prob.

-5

3-9e

$$|H(j\omega)|^2 = (\omega^4 + 2\omega^2 + 1) / (\omega^8 - 5\omega^6 + 11\omega^4 - 11\omega^2 + 4)$$

$$1) \frac{C(s)}{D(s)} \stackrel{\Delta}{=} |H(j\omega)|^2 \Big|_{\omega = \frac{s}{j}} = (s^4 - 2s^2 + 1) / (s^8 + 5s^6 + 11s^4 + 11s^2 + 4)$$

$$C(s) = s^4 - 2s^2 + 1$$

$$D(s) = s^8 + 5s^6 + 11s^4 + 11s^2 + 4$$

$$2) C(s) = s^4 - 2s^2 + 1 = (s-1)^2 (s+1)^2 = (s^2 - 2s + 1)(s^2 + 2s + 1)$$

$$A(s) = s^2 + 2s + 1$$

$$3) D(s) = s^8 + 5s^6 + 11s^4 + 11s^2 + 4 = (s^4 + 2s^2 + 1)(s^4 + 3s^2 + 4)$$

$$= (s-j)(s+j)(s-j)(s+j)(s-0.5+j1.323)(s-0.5+j1.323)(s+0.5+j1.323) \cdot (s+0.5-j1.323)$$

$$B(s) = (s^2 + 1) \cdot (s + 0.5 + j1.323)(s + 0.5 - j1.323)$$

$$= (s^2 + 1)(s^2 + s + 2) = s^4 + s^3 + 3s^2 + s + 2$$

$$4) H(s) = (s^2 + 2s + 1) / (s^4 + s^3 + 3s^2 + s + 2)$$

$$\text{CHECK: } H(j\omega) = H(s) \Big|_{s=j\omega} = (-\omega^2 + 1 + j2\omega) / (2 + \omega^4 - 3\omega^2 + j\omega - j\omega^3)$$

$$\begin{aligned} |H(j\omega)|^2 &= (-\omega^2 + 1 + j2\omega)(-\omega^2 + 1 - j2\omega) / (2 + \omega^4 - 3\omega^2 + j\omega - j\omega^3)(2 + \omega^4 - 3\omega^2 - j\omega + j\omega^3) \\ &= (\omega^4 + 2\omega^2 + 1) / (\omega^8 - 5\omega^6 + 11\omega^4 - 11\omega^2 + 4) \end{aligned}$$

CHECKED!

Wrong problem

5

4.1

$$(d) \quad p(s) = 3s^4 + 2s^3 + 3s^2 + 2s + 3$$

$$M(s) = 3s^4 + 3s^2 + 3$$

$$N(s) = 2s^3 + 2s$$

$$\begin{array}{r} \frac{3}{2}s \\ 2s^3 + 2s \overline{) 3s^4 + 3s^2 + 3} \\ \underline{3s^4 + 3s^2} \\ 0 \end{array}$$

so, $p(s)$ is neither Hurwitz nor modified Hurwitz polynomial. ✓

* If $p(s)$ is a Hurwitz polynomial, $T(s) \triangleq \frac{M(s)}{N(s)}$ or $\frac{N(s)}{M(s)}$ could be written

as this form $T(s) = \xi_1 s + \frac{1}{\xi_2 s + \frac{1}{\xi_3 s + \frac{1}{\ddots \frac{1}{\xi_n s}}}}$. In this problem, $T(s)$ can't be

written in this form, so, $p(s)$ is not a Hurwitz or modified polynomial.

$$(e) \quad p(s) = s^4 + 2s^3 + 3s^2 + 4s + 2$$

$$M(s) = s^4 + 3s^2 + 2$$

$$N(s) = 2s^3 + 4s$$

$$\begin{array}{r} \frac{1}{2}s \\ 2s^3 + 4s \overline{) s^4 + 3s^2 + 2} \\ \underline{s^4 + 2s^2} \\ 0 \end{array}$$

$$k(s) = s^2 + 2$$

$$\hat{T}(s) = \frac{s^2 + 2}{2s} = \frac{1}{2}s + \frac{1}{s}$$

so, $p(s)$ is a modified Hurwitz polynomial. ✓

$$(f) \quad p(s) = s^4 + 5s^3 + 11s^2 + 11s + 4$$

$$M(s) = s^4 + 11s^2 + 4, \quad N(s) = 5s^3 + 11s$$

$$\begin{array}{r} \frac{1}{5}s \\ 5s^3 + 11s \overline{) s^4 + 11s^2 + 4} \\ \underline{s^4 + \frac{11}{5}s^2} \\ \frac{44}{5}s^2 + 4 \end{array}$$

$$\begin{array}{r} \frac{25}{44}s \\ \frac{44}{5}s^2 + 4 \overline{) 5s^3 + 11s} \\ \underline{5s^3 + 25/11s} \\ 96/11s \end{array}$$

$$\begin{array}{r} \frac{121}{120}s \\ \frac{96}{11}s \overline{) \frac{44}{5}s^2 + 4} \\ \underline{\frac{44}{5}s^2} \\ 4 \end{array}$$

$$\begin{array}{r} \frac{24}{11}s \\ 4 \overline{) \frac{96}{11}s} \\ \underline{\frac{96}{11}s} \\ 0 \end{array}$$

so, $p(s)$ is a Hurwitz polynomial. ✓

57
60

(i) $p(s) = s^5 + s^4 + 3s^3 + 2s^2 + 2s + 2$

$N(s) = s^5 + 3s^3 + 2s$

$M(s) = s^4 + 2s^2 + 2$

$$\begin{array}{r}
 s \\
 \hline
 s^4 + 2s^2 + 2 \sqrt{s^5 + 3s^3 + 2s} \\
 \hline
 s^5 + 2s^3 + 2s \\
 \hline
 s^3 \\
 \hline
 s \\
 \hline
 s^4 + 2s^2 + 2 \\
 \hline
 s^4 \\
 \hline
 2s^2 + 2 \\
 \hline
 \frac{1}{2}s \\
 \hline
 s^3 + 2 \\
 \hline
 -s \\
 \hline
 2s^2 + 2 \\
 \hline
 2s^2 \\
 \hline
 2
 \end{array}$$

So, $p(s)$ is neither Hurwitz nor modified Hurwitz polynomial.

(p) $p(s) = s^6 + 2s^4 + s^2 + 3$

$M(s) = s^6 + 2s^4 + s^2 + 3$

$N(s) = 0$

$k(s) = s^6 + 2s^4 + s^2 + 3$

($p(s)$ is not a Hurwitz.)

$\hat{f}(s) = \frac{s^6 + 2s^4 + s^2 + 3}{6s^5 + 8s^3 + 2s}$

$$\begin{array}{r}
 \frac{1}{6}s \\
 \hline
 6s^5 + 8s^3 + 2s \sqrt{s^6 + 2s^4 + s^2 + 3} \\
 \hline
 s^6 + \frac{4}{3}s^4 + \frac{1}{3}s^2 \\
 \hline
 \frac{2}{3}s^4 + \frac{2}{3}s^2 + 3 \\
 \hline
 9s \\
 \hline
 6s^5 + 8s^3 + 2s \\
 \hline
 6s^5 + 6s^3 + 27s \\
 \hline
 2s^3 - 25s \\
 \hline
 \frac{1}{3}s \\
 \hline
 \frac{2}{3}s^4 + \frac{2}{3}s^2 + 3 \\
 \hline
 \frac{2}{3}s^4 - \frac{25}{3}s^2 \\
 \hline
 \frac{27}{3}s^2 + 3 \\
 \hline
 \frac{6}{27}s \\
 \hline
 2s^3 - 25s \\
 \hline
 2s^3 + \frac{16}{27}s \\
 \hline
 -\frac{683}{27}s
 \end{array}$$

So, $p(s)$ is not a modified Hurwitz polynomial.

4-7

(b) $F(s) = \frac{1}{s}$

$F(s)$ is PR.

Let $s = \sigma + j\omega$, $F(s) = \frac{1}{s} = \frac{1}{\sigma + j\omega} = \frac{1}{\sigma^2 + \omega^2} (\sigma - j\omega)$

$\omega = 0 \rightarrow F(s) = \frac{\sigma}{\sigma^2 + \omega^2}$ real.

$\sigma \geq 0 \rightarrow \text{Re}\{F(s)\} = \sigma / (\sigma^2 + \omega^2) \geq 0$

$$(d) F(s) = \frac{s+4}{s^2+s+15}$$

$$(1) s = \sigma, F(s) = F(\sigma) = \frac{\sigma+4}{\sigma^2+\sigma+15} \text{ is real}$$

$$(2) B(s) = s^2+s+15 \text{ is Hurwitz polynomial.}$$

$$(3) F(s) = \frac{s+4}{s^2+s+15} = \frac{0.5-j0.456}{(s+0.5-j3.84)} + \frac{0.5+j0.456}{(s+0.5+j3.84)}$$

SO, $F(s)$ is not PR

Need to check $RG(j\omega)$!

$$(f) F(s) = \frac{s^2+9}{s^3+4s}$$

$$(1) F(\sigma) = (s^2+9)/(s^3+4s)|_{s=\sigma} = (\sigma^2+9)/(\sigma^3+4\sigma) \text{ real}$$

$$(2) B(s) = s^3+4s = s(s+jz)(s-jz) \text{ modified Hurwitz}$$

$$(3) F(s) = \frac{9/4}{s} + \frac{-5/8}{s+jz} + \frac{-5/8}{s-jz} \text{ negative residues}$$

SO, $F(s)$ is not PR.

$$(h) F(s) = \frac{s^3+6s^2+2s+1}{(s+1)^2}$$

(1) $F(s)$ is real when s is real

(2) $B(s) = (s+1)^2$ is Hurwitz

$$(3) A(s) = s^3+6s^2+2s+1 = (s+5.68)(s+0.16-j0.388)(s+0.16+j0.388)$$

$A(s)$ is Hurwitz.

$$G(s) \triangleq 1/F(s) = B(s)/A(s) = (s+1)^2 / (s+5.68)(s+0.16-j0.388)(s+0.16+j0.388)$$

$$= \frac{0.715}{s+5.68} + \frac{0.076-j0.201}{s+0.16-j0.388} + \frac{0.076+j0.201}{s+0.16+j0.388}$$

$\therefore G(s)$ is not a PR function

$F(s)$ is also not PR.

$$g) F(s) = (s^3 + 6s^2 + 2s + 1) / (s^3 + 3s + 1)$$

$$B(s) = s^3 + 3s + 1$$

$$N_B(s) = s^3 + 3s$$

$$M_B(s) = 1$$

$$1. \sqrt{s^3 + 3s}$$

So, $B(s)$ is neither Hurwitz nor modified Hurwitz polynomial.

$F(s)$ isn't PR. ✓

$$(1) F(s) = (s^4 + s^3 + 2s^2 + 5) / (4s^2 + 2s + 1)$$

$F(s)$ isn't PR. Because the difference between degrees $A(s)$ and $B(s)$ is 2. ✓

$$(n) F(s) = (10s^4 + 8s^2 + 1) / (4s^5 + 10s^3 + 4s)$$

(1) $F(s)$ is real when s is real

$$(2) B(s) = 4s^5 + 10s^3 + 4s$$

$$N_B(s) = 4s^5 + 10s^3 + 4s, \quad M_B(s) = 0$$

$$k(s) = 4s^5 + 10s^3 + 4s$$

$$\hat{T}(s) = \frac{4s^5 + 10s^3 + 4s}{20s^4 + 30s^2 + 4}$$

$$20s^4 + 30s^2 + 4 \begin{array}{l} \frac{1}{5}s \\ \hline 4s^5 + 10s^3 + 4s \\ 4s^5 + 6s^3 \\ \hline 4s^3 + 4s \end{array} \begin{array}{l} 5s \\ \hline 20s^4 + 30s^2 + 4 \\ 20s^4 + 20s^2 \\ \hline 10s^2 + 4 \end{array} \begin{array}{l} \frac{2}{5}s \\ \hline 4s^3 + 4s \\ 4s^3 + \frac{8}{5}s \\ \hline \frac{12}{5}s \end{array} \begin{array}{l} \frac{12}{5}s \\ \hline 10s^2 + 4 \\ 10s^2 \\ \hline 4 \end{array} \begin{array}{l} \frac{12}{5}s \\ \hline 4s^2 + \frac{12}{5}s \\ 4s^2 + \frac{12}{5}s \\ \hline 0 \end{array}$$

$B(s)$ is modified Hurwitz. ✓

$$\begin{aligned}
 (3) \quad F(s) &= (10s^4 + 8s^2 + 1) / (4s^5 + 10s^3 + 4s) \\
 &= (10s^4 + 8s^2 + 1) / 4s \cdot (s - j\frac{\sqrt{2}}{2})(s + j\frac{\sqrt{2}}{2})(s + j\sqrt{2})(s - j\sqrt{2}) \\
 &= \frac{2.5}{s} + \frac{25/24}{s - j\sqrt{2}} + \frac{25/24}{s + j\sqrt{2}} + \frac{1/12}{s + j\sqrt{2}/2} + \frac{1/12}{s - j\sqrt{2}/2}
 \end{aligned}$$

$$\begin{aligned}
 (4) \quad F(j\omega) &= (10\omega^4 - 8\omega^2 + 1) / (j4\omega^5 - j10\omega^3 + j4\omega) \\
 &= -j (10\omega^4 - 8\omega^2 + 1) / (4\omega^5 - 10\omega^3 + 4\omega)
 \end{aligned}$$

$$\therefore \operatorname{Re}\{F(j\omega)\} = 0$$

so, $F(s)$ is PR. ✓

5-1. DETERMINE which of the following $F(s)$ are realizable as lossless DP Functions. Justify your answers.

$$(a) F(s) = (s^4 + 5s^2 + 6) / (s^4 + 3s^2 + 2)$$

Answer: $F(s)$ is unrealizable.

Because the difference between the degrees of $(s^4 + 5s^2 + 6)$ and $(s^4 + 3s^2 + 2)$ is zero. This doesn't satisfy Property 3. ✓

109
120

Good job!

$$(c) F(s) = (s^3 + 5s) / (s^4 + 3s^2 + 2)$$

$$= s(s + j\sqrt{5})(s - j\sqrt{5}) / [(s - j)(s + j)(s - j\sqrt{2})(s + j\sqrt{2})]$$

Answer: $F(s)$ is unrealizable. X

Because, $F(s)$ does not satisfy Proper 6. The poles and zeros ^{are} along the imaginary axis like:

∞ (zero), $j\sqrt{5}$ (zero), $j\sqrt{2}$ (pole), j (pole), 0 (zero), ...

$$(e) F(s) = (s^3 + 1.5s) / (s^2 + 1)$$

Answer: $F(s)$ is realizable. ✓

It is easy to check that $F(s)$ satisfies Property 1, 2, 3, 4 and 6. And

$$F(j\omega)/j = (-j\omega^3 + j1.5\omega) / j(-\omega^2 + 1) = (-\omega^2 + 1.5\omega) / (-\omega^2 + 1)$$

$$\frac{d F(j\omega)/j}{d\omega} = [(-3\omega^2 + 1.5)(-\omega^2 + 1) - (-2\omega) \cdot (-\omega^3 + 1.5\omega)] / (1 - \omega^2)^2$$

$$= (\omega^4 - 1.5\omega^2 + 1.5) / (1 - \omega^2)^2$$

$$= [(\omega^2 - 0.75)^2 + 0.9375] / (1 - \omega^2)^2$$

> 0 (except the poles of $F(s)$). ✓

$$\begin{aligned} \text{c) } F(s) &= (s^5 + 3s^3 + 2s) / (s^4 + 5.5s^2 + 6) \\ &= s(s+j)(s-j)(s+j\sqrt{2})(s-j\sqrt{2}) / [(s-j1.225)(s+j1.225)(s+j2)(s-j2)] \end{aligned}$$

Answer: $F(s)$ is unrealizable. ✓

Because the poles and zeros of $F(s)$ don't alternate with each other along the imaginary axis. ✓

∞ (pole), $j2$ (pole), $j1.225$ (pole), $j\sqrt{2}$ (zero), j (zero), 0 (zero), $-j$ (zero), ...

$$\text{(i) } F(s) = (s^4 + 3s^2 + 2) / (s^5 + 5.5s^3 + 6)$$

Answer: $F(s)$ is unrealizable.

Because $F(-s) = (s^4 + 3s^2 + 2) / (-s^5 - 5.5s^3 + 6) \neq -F(s)$.

5-7 Realize the following DP admittance functions by two Foster's forms and two Cauer's forms. If a given $Y(s)$ is not realizable, state your reasons.


$$\text{(b) } Y(s) = (s^2 + 3) / [s(s^2 + 4)]$$

FIRST FOSTER'S FORM:

$$Z(s) = s(s^2 + 4) / (s^2 + 3)$$

$$\frac{Z(s)}{s} \Big|_{s^2=p} = (p+4) / (p+3) = 1 + \frac{1}{p+3}$$
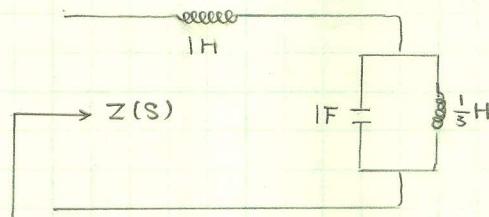
$$Z(s) = s + \frac{s}{s^2+3} = s + \frac{1}{s + \frac{1}{\frac{1}{3}s}}$$



$$\text{CHECK: } Z(s) = s + \frac{\frac{1}{3}s \cdot (\frac{1}{s})}{\frac{1}{3}s + \frac{1}{s}} = s + \frac{s}{s^2+3} = \frac{s(s^2+4)}{s^2+3}$$

CHECKED!


5-7(b) CONT.

SECOND FOSTER'S FORM:

$$Y(s) = (s^2 + 3) / [s(s^2 + 4)]$$

$$Y(s) \Big|_{s^2=p} = (p+3) / [p(p+4)] = \frac{3/4}{p} + \frac{1/4}{p+4}$$
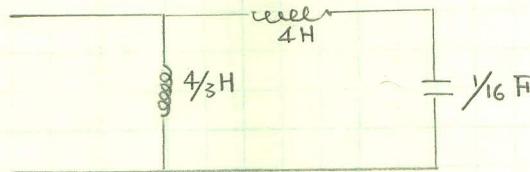
$$Y(s) = \frac{3/4}{s} + \frac{1/4 s}{s^2+4} = \frac{1}{4/3 s} + \frac{1}{4s + \frac{1}{16s}}$$




CHECK: $Y(s) = \frac{1}{4/3 s} + \frac{1}{4s + \frac{1}{16s}} = (s^2 + 3) / [s(s^2 + 4)]$

CHECKED!!

FIRST CAUER'S FORM:

$$Z(s) = s(s^2 + 4) / (s^2 + 3) = (s^3 + 4s) / (s^2 + 3)$$
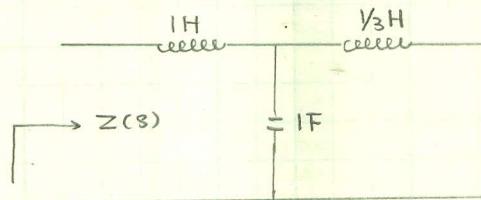
$$s^2 + 3 \overline{) \begin{array}{r} s \\ s^3 + 4s \\ \hline s^2 + 3s \\ \hline s \end{array}} \quad \begin{array}{r} s \\ s^2 + 3 \\ \hline s^2 \\ \hline 3 \end{array} \quad \begin{array}{r} 1/3 s \\ s \\ \hline s \\ \hline 0 \end{array}$$



CHECK: $Z(s) = s + \frac{1/3 s \cdot \frac{1}{s}}{1/3 s + \frac{1}{s}} = (s^3 + 4s) / (s^2 + 3)$ CHECKED!!


SECOND CAUER'S FORM:

$$Y(s) = (s^2 + 3) / (s^3 + 4s)$$

$$4s + s^3 \overline{) \begin{array}{r} 3/4 s \\ 3 + s^2 \\ \hline 3 + 3/4 s^2 \\ \hline 1/4 s \end{array}} \quad \begin{array}{r} 16/3 \\ 4 + s^2 \\ \hline 4 + 0 \\ \hline s \end{array} \quad \begin{array}{r} 1/4 s \\ 1/4 \\ \hline 1/4 \\ \hline 0 \end{array}$$



5-7(b) CONT.

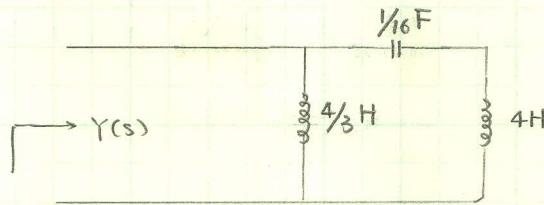

$$\text{CHECK: } Y(s) = \frac{3}{4s} + \frac{1}{4s + \frac{1}{16s}} = \frac{(s^2 + 3)}{(s^3 + 4s)} \quad \text{CHECKED!!}$$


$$(c) \quad Y(s) = \frac{(s^2 + 1)(s^2 + 3)}{[s(s^2 + 2)]}$$

FIRST FOSTER'S FORM

$$Z(s) = \frac{s(s^2 + 2)}{[(s^2 + 1)(s^2 + 3)]}$$

$$\frac{Z(s)}{s} \Big|_{s^2=p} = \frac{(p+2)}{[(p+1)(p+3)]} = \frac{0.5}{p+1} + \frac{0.5}{p+3}$$
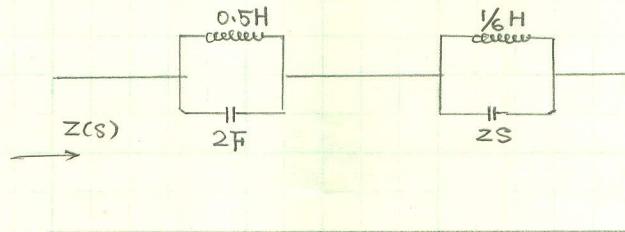
$$Z(s) = \frac{0.5s}{s^2+1} + \frac{0.5s}{s^2+3} = \frac{1}{2s + \frac{1}{0.5s}} + \frac{1}{2s + \frac{1}{1/6s}}$$




$$\text{CHECK: } Z(s) = \frac{1}{2s + \frac{1}{0.5s}} + \frac{1}{2s + \frac{1}{\frac{1}{6s}}} = \frac{s(s^2 + 2)}{[(s^2 + 1)(s^2 + 3)]} \quad \text{CHECKED}$$

SECOND FOSTER'S FORM

$$Y(s) = \frac{(s^2 + 1)(s^2 + 3)}{[s(s^2 + 2)]}$$

$$\frac{Y(s)}{s} \Big|_{s^2=p} = \frac{(p+1)(p+3)}{[p(p+2)]} = 1 + \frac{\frac{3}{2}}{p} + \frac{\frac{1}{2}}{p+2}$$
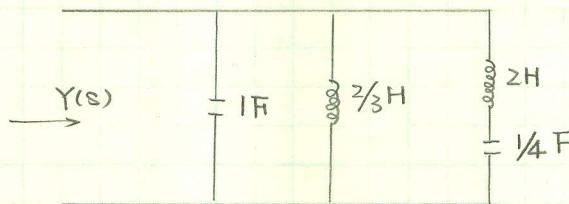
$$Y(s) = s + \frac{1}{\frac{2}{3}s} + \frac{1}{2s + \frac{1}{4s}}$$



$$\text{CHECK: } Y(s) = s + \frac{3}{2s} + \frac{1}{2s + \frac{1}{4s}} = \frac{(s^2 + 1)(s^2 + 3)}{[s(s^2 + 2)]}$$


CHECKED !!

5-7 (c) CONT.

FIRST CAUER'S FORM

$$Y(s) = (s^2+1)(s^2+3) / [s(s^2+2)] = (s^4+4s^2+3) / (s^3+2s)$$

$$\begin{array}{r} s^3+2s \overline{) s^4+4s^2+3} \\ \underline{s^4+2s^2} \\ 2s^2+3 \end{array} \quad \begin{array}{r} \frac{1}{2}s \overline{) s^3+2s} \\ \underline{s^3+\frac{1}{2}s} \\ \frac{3}{2}s \end{array} \quad \begin{array}{r} 4s \overline{) 2s^2+3} \\ \underline{2s^2} \\ 3 \end{array} \quad \begin{array}{r} \frac{1}{6}s \overline{) \frac{3}{2}s} \\ \underline{\frac{1}{2}s} \\ \frac{1}{2}s \\ 0 \end{array}$$

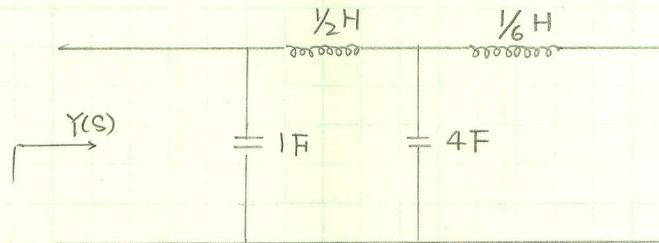


$$\text{CHECK: } Y(s) = s + \frac{1}{0.5s} + \frac{1}{4s + \frac{6}{s}} = \frac{(s^2+1)(s^2+3)}{s(s^2+2)}$$

CHECKED!!

SECOND CAUER'S FORM

$$Y(s) = (s^4+4s^2+3) / (s^3+2s)$$

$$\begin{array}{r} \frac{3}{2s} \overline{) 3+4s^2+s^4} \\ \underline{3+\frac{3}{2}s^2} \\ \frac{5}{2}s+s^3 \end{array} \quad \begin{array}{r} \frac{4}{5s} \overline{) 2+s^2} \\ \underline{2+\frac{4}{5}s^2} \\ \frac{1}{5}s \end{array} \quad \begin{array}{r} \frac{25}{2s} \overline{) \frac{5}{2}s+s^2} \\ \underline{\frac{5}{2}} \\ s \end{array} \quad \begin{array}{r} \frac{1}{5s} \overline{) \frac{1}{5}s} \\ \underline{\frac{1}{5}} \\ 0 \end{array}$$

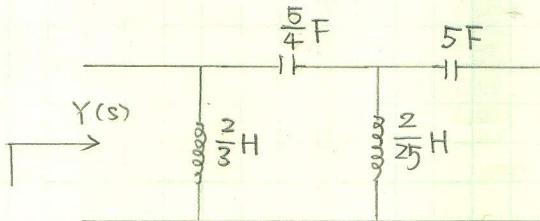

$$\text{CHECK: } Y(s) = \frac{3}{2s} + \frac{1}{\frac{4}{5s} + \frac{1}{\frac{25}{2s} + 5s}}$$

$$= \frac{3}{2s} + \frac{25s(2s^2+5)}{50s^2+100} = \frac{3}{2s} + \frac{s(2s^2+5)}{2s^2+4}$$

$$= \frac{s^4+4s^2+3}{s^3+2s} \quad \text{CHECKED!}$$


5-7 (d) $Y(s) = s(s^2+2)(s^2+4)/(s^2+1)(s^2+3)$

FOSTER'S FIRST FORM:

$$Z(s) = (s^2+1)(s^2+3)/s(s^2+2)(s^2+4)$$

$$\begin{aligned} \frac{Z(s)}{s} \Big|_{s^2=p} &= (p+1)(p+3)/p(p+2)(p+4) \\ &= \frac{\frac{3}{8}}{p} + \frac{\frac{1}{4}}{p+2} + \frac{\frac{3}{8}}{p+4} \end{aligned}$$
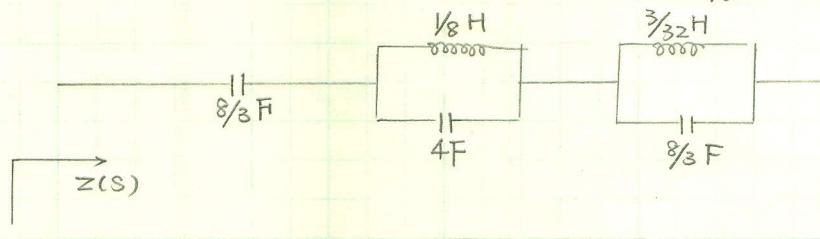
$$Z(s) = \frac{1}{\frac{8}{3}s} + \frac{1}{4s + \frac{1}{8s}} + \frac{1}{\frac{8}{3}s + \frac{1}{\frac{3}{32}s}}$$




CHECK:
$$\begin{aligned} Z(s) &= \frac{1}{\frac{8}{3}s} + \frac{1}{4s + \frac{8}{s}} + \frac{1}{\frac{8}{3}s + \frac{32}{3s}} \\ &= \frac{3/8}{s} + \frac{0.25s}{s^2+2} + \frac{3/8s}{s^2+4} \\ &= \frac{3/8(s^2+2)(s^2+4) + 0.25s^2(s^2+4) + 3/8s^2(s^2+2)}{s(s^2+2)(s^2+4)} \\ &= \frac{s^4 + 4s^2 + 3}{s(s^2+2)(s^2+4)} = \frac{(s^2+1)(s^2+3)}{s(s^2+2)(s^2+4)} \quad \text{CHECKED!} \end{aligned}$$

FOSTER'S SECOND FORM:

$$Y(s) = s(s^2+2)(s^2+4)/(s^2+1)(s^2+3)$$

$$\begin{aligned} \frac{Y(s)}{s} \Big|_{s^2=p} &= (p+2)(p+4)/(p+1)(p+3) \\ &= \frac{\frac{3}{2}}{p+1} + \frac{\frac{1}{2}}{p+3} + 1 \end{aligned}$$
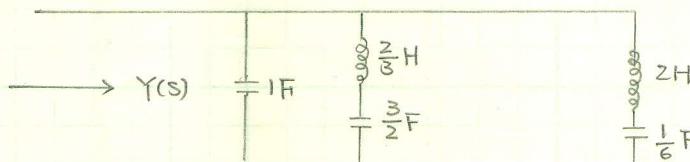
$$Y(s) = \frac{1}{\frac{2}{3}s + \frac{1}{\frac{3}{2}s}} + \frac{1}{2s + \frac{1}{\frac{1}{6}s}} + s$$



CHECK:
$$Y(s) = \frac{1}{\frac{2}{3}s + \frac{2}{3s}} + \frac{1}{2s + \frac{6}{s}} + s = \frac{s(s^4 + 6s^2 + 8)}{(s^2+1)(s^2+3)} \quad \text{CHECKED!}$$

5-7 cd) CONT.

CAUER'S FIRST FORM:

$$Y(S) = \frac{S(S^2+2)(S^2+4)}{(S^2+1)(S^2+3)}$$

$$= \frac{(S^5+6S^3+8S)}{(S^4+4S^2+3)}$$

$$S^4+4S^2+3 \overline{) S^5+6S^3+8S}$$

$$\underline{S^5+4S^3+3S}$$

$$2S^3+5S$$

$$S^4+4S^2+3 \overline{) S^4+5/2S^2}$$

$$\underline{S^4+5/2S^2}$$

$$3/2S^2+3$$

$$2S^3+4S \overline{) 2S^3+5S}$$

$$\underline{2S^3+4S}$$

$$S$$

$$3/2S^2+3 \overline{) S}$$

$$\underline{3/2S^2}$$

$$3$$

$$3 \overline{) 3}$$

$$\underline{3}$$

$$0$$

✓

CHECK: $Y(S) = S + \frac{1}{\frac{1}{2}S + \frac{1}{\frac{4}{3}S + \frac{1}{\frac{1}{2}S + \frac{3}{8}}}}$

$$= S + \frac{1}{0.5S + \frac{1}{\frac{4}{3}S + \frac{2S}{3S^2+6}}} = S + \frac{1}{0.5S + \frac{3S^2+6}{4S(S^2+2)}}$$

$$= \frac{(S^5+6S^3+8S)}{(S^4+4S^2+3)} \quad \text{CHECKED!}$$

CAUER'S SECOND FORM:

$$Z(S) = \frac{(S^4+4S^2+3)}{(S^5+6S^3+8S)}$$

$$8S+6S^3+S^5 \overline{) 3+4S^2+S^4}$$

$$\underline{3+9/4S^2+3/8S^4}$$

$$7/4S+5/8S^3$$

$$8S+6S^2+S^4 \overline{) 8S+20S^2}$$

$$\underline{8S+20S^2}$$

$$22/7S+S^3$$

$$7/4+5/8S^2 \overline{) 7/4+49/88S^2}$$

$$\underline{7/4+49/88S^2}$$

$$6/88S$$

$$22/7+S^3 \overline{) 22/7+S^2}$$

$$\underline{22/7}$$

$$S$$

$$S \overline{) 3/44s}$$

$$\underline{3/44}$$

$$3/44$$

$$0$$

✓

check -3



5-7 (e)

$$Y(s) = (s^2 + 2)(s^2 + 4) / s(s^2 + 1)(s^2 + 3)$$

$Y(s)$ is not realizable, because the zeros and poles of $Y(s)$ do not alternate with each other along the imaginary axis.

$$\infty \text{ (zero)}, j4 \text{ (zero)}, \dots$$

5-8

$$Z(s) = \frac{(s^2 + 1)(s^2 + 4)}{s(s^2 + 3)(s^2 + 5)}$$

(a) START WITH CAUER'S FIRST FORM (FOR TWO ELEMENTS), AND COMPLETE THE REALIZATION WITH CAUER'S SECOND FORM.


$$\text{FIRST FORM: } Y(s) = (s^5 + 8s^3 + 15s) / (s^4 + 5s^2 + 4)$$

$$\begin{array}{r} s \\ s^4 + 5s^2 + 4 \overline{) s^5 + 8s^3 + 15s} \\ \underline{s^5 + 5s^3 + 4s} \\ 3s^3 + 11s \end{array} \quad \begin{array}{r} \frac{1}{3}s \\ s^4 + 5s^2 + 4 \\ \underline{s^4 + \frac{11}{3}s^2} \\ \frac{4}{3}s^2 + 4 \end{array}$$

$$Y(s) = s + \frac{1}{\frac{1}{3}s + Z'(s)}$$

$$\text{SECOND FORM: } Z'(s) = \frac{1}{Y(s) - s} - \frac{1}{3}s = \frac{4s^2 + 12}{9s^3 + 33s}$$
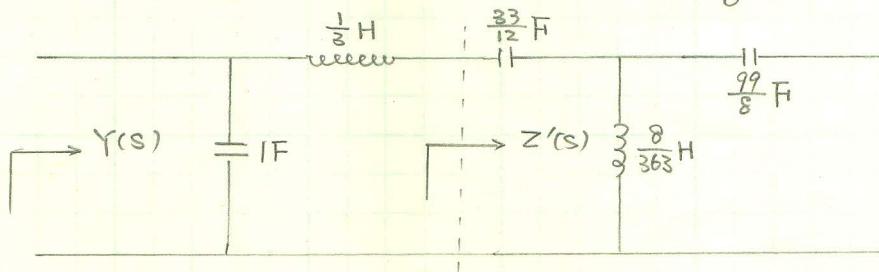
$$\begin{array}{r} \frac{12}{33s} \\ 33s + 9s^3 \overline{) 12 + 4s^2} \\ \underline{12 + \frac{36}{11}s^2} \\ \frac{8}{11}s \end{array} \quad \begin{array}{r} \frac{363}{8s} \\ 33 + 9s^2 \\ \underline{33} \\ 9s \end{array} \quad \begin{array}{r} \frac{8}{99s} \\ \frac{8}{11} \\ \underline{\frac{8}{11}} \\ 0 \end{array}$$



5-8 (a) CONT.

$$\text{CHECK: } Z'(s) = \frac{12}{33s} + \frac{1}{\frac{363}{88} + \frac{99}{8}s}$$

$$= \frac{12}{33s} + \frac{88}{33(3s^2+11)} = \frac{4s^2+12}{9s^3+33s}$$

$$Y(s) = s + \frac{1}{\frac{1}{3}s + \frac{4s^2+12}{9s^3+33s}} = \frac{s^5+8s^3+15s}{(s^4+5s^2+4)}$$

✓ CHECKED!

(b) START WITH CAUER'S SECOND FORM (FOR 3 ELEMENTS); COMPLETE THE REALIZATION WITH CAUER'S FIRST FORM.

Cauer's 2nd F: $Z(s) = \frac{s^4 + 5s^2 + 4}{s^5 + 8s^3 + 15s}$

$$15s + 8s^3 + s^5 \overline{) 4 + 5s^2 + s^4}$$

$$\begin{array}{r} 4 + \frac{32}{15}s^2 + \frac{4}{15}s^4 \\ \hline \frac{43}{15}s + \frac{11}{15}s^3 \end{array} \overline{) 15 + 8s^2 + s^4}$$

$$\begin{array}{r} 15 + \frac{165}{43}s^2 \\ \hline \frac{179}{43}s + s^3 \end{array} \overline{) \frac{43}{15} + \frac{11}{15}s^2}$$

$$\begin{array}{r} \frac{43}{15} + \frac{1849}{2685}s^2 \\ \hline \frac{24}{537}s \end{array} \overline{) \frac{32041}{344s} + s^2}$$

$$Z(s) = \frac{1}{15s} + \frac{1}{\frac{225}{43s} + \frac{1}{\frac{1849}{2685s} + Z'(s)}}$$

$$Z'(s) = \frac{1}{\frac{32041}{344s} + \frac{537s}{24}} = \frac{344s}{7697s^2 + 32041}$$


Cauer's 1st: $Y'(s) = \frac{7697s^2 + 32041}{344s}$

$$344s \overline{) \frac{7697s^2 + 32041}{7697s^2}}$$

$$\begin{array}{r} 344s \\ \hline 32041 \\ \hline 344s \\ \hline 0 \end{array}$$

42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-383 100 SHEETS 5 SQUARE
NATIONAL INSTRUMENTS

5-8 (b) CONT.

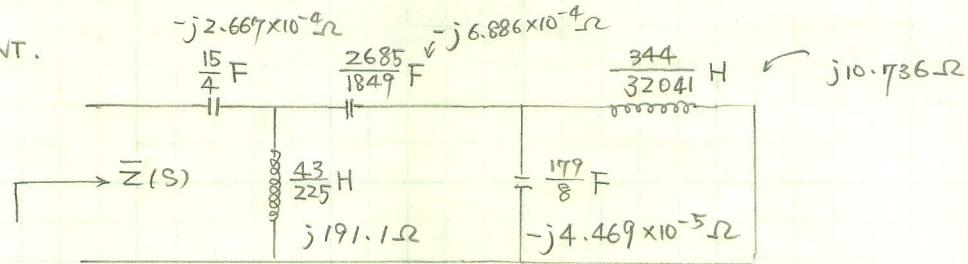

IN ORDER TO CHECK THE REALIZATION WITH A EASY WAY, WE LET

$$s = j\omega \quad \text{AND} \quad \omega = 1000 \text{ rad/s}$$

$$\bar{Z}'(j1000) = -j0.001000003 \Omega$$

$$Z(s) \Big|_{s=j1000} = \frac{1000^4 - 5 \times 1000^2 + 4}{j(1000^5 - 8 \times 1000^3 + 15 \times 1000)} = -j0.001000003 \Omega$$

80% CHECKED!!

-2

5-8 (c) Cauer's first form for 1 element. Cauer's second form for 1 element.

Complete the realization with Foster's first form

$$\text{Cauer's 1st: } Y(s) = \frac{s^5 + 8s^3 + 15s}{s^4 + 5s^2 + 4}$$

$$Y(s) \triangleq s + Y_1(s)$$

$$Y_1(s) = Y(s) - s = \frac{s^5 + 8s^3 + 15s}{s^4 + 5s^2 + 4} - s = \frac{3s^3 + 11s}{s^4 + 5s^2 + 4}$$

$$\text{Cauer's 2nd: } Z_1(s) \triangleq 1/Y_1(s) = (s^4 + 5s^2 + 4) / (3s^3 + 11s)$$

$$\triangleq \frac{4}{11s} + Z_2(s)$$

$$Z_2(s) = Z_1(s) - \frac{4}{11s} = \frac{s^4 + 5s^2 + 4}{3s^3 + 11s} - \frac{4}{11s}$$

$$= \frac{11s^3 + 43s}{33s^2 + 121}$$


Foster's 1st:

$$\frac{Z_2(s)}{s} \Big|_{s=p} = \frac{11p + 43}{33p + 121} = \frac{1}{3} + \frac{\frac{8}{3}}{33p + 121}$$

$$Z_2(s) = \frac{1}{3}s + \frac{\frac{8}{3}s}{33s^2 + 121}$$

$$= \frac{1}{3}s + \frac{1}{\frac{99}{8}s + \frac{1}{\frac{8}{363}}}$$

5-8 (c) CONT.

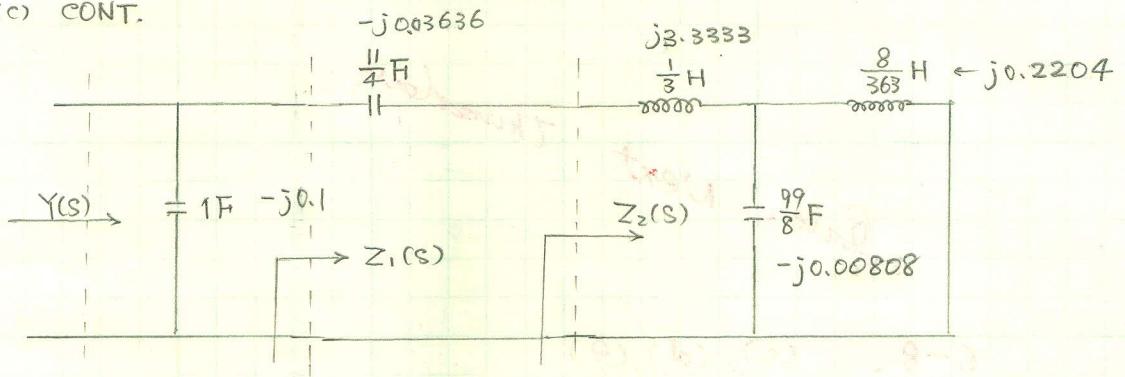

CHECK = SAME AS part (b), we check the answer
in easy way. Let $s = j \cdot 10$

$$Y(j \cdot 1) = j 9.69589 \text{ } \Omega$$

$$Y(s) \Big|_{s=j \cdot 1} = (j10^5 - j8 \times 10^3 + j150) / (10^4 - 5 \times 10^2 + 4)$$

$$= j 9.69592 \text{ } \Omega$$

90% CHECKED!!

4340
BENMEI CHEN

6-1. DETERMINE WHICH OF THE FOLLOWING $Z(s)$ ARE REALIZABLE AS RC DP IMPEDANCE FUNCTIONS:

$\frac{50}{50}$

$$(b) \quad Z(s) = \frac{s^2 + 5s}{s^2 + 3s + 2}$$

$$= \frac{s(s+5)}{(s+1)(s+2)}$$

$$s=0 \text{ (zero)}; s=-1 \text{ (pole)}; s=-2 \text{ (pole)}; s=-5 \text{ (zero)}$$

SO, $Z(s)$ IS NOT REALIZABLE.

$$(d) \quad Z(s) = (s+1.5)/(s^2+2s+1)$$

$$= (s+1.5)/(s+1)(s+1)$$

$$s=-1 \text{ is not a simple pole}$$

SO, $Z(s)$ IS NOT REALIZABLE.

$$(f) \quad Z(s) = (s^2 + 7s + 12)/(s^3 + 3s^2 + 3s + 1)$$

$$= (s+3)(s+4)/(s+1)(s+1)(s+1)$$

$$s=-1 \text{ IS NOT A SIMPLE POLE}$$

SO, $Z(s)$ IS NOT REALIZABLE.

$$(h) \quad Z(s) = (s^3 + 8s^2 + 17s + 10)/(s^3 + 11.5s^2 + 39s + 36)$$

$$= (s+5)(s+1)(s+2)/(s+6)(s+1.5)(s+4)$$

$Z(s)$ DOES NOT SATISFY PROPERTY ZRC 5

$$1.5 > 1, \text{ SO, } Z(s) \text{ IS NOT REALIZABLE.}$$

$$(j) \quad Z(s) = (s^3 + 6s^2 + 8.75s + 3)/(s^2 + 3s + 2) \triangleq A(s)/B(s)$$

BECAUSE DEGREE OF $A(s) = 3 >$ DEGREE OF $B(s) = 2$

SO, $Z(s)$ IS NOT REALIZABLE.

6-2. DETERMINE WHICH OF THE FOLLOWING $Y(s)$ ARE REALIZABLE AS RC DP ADMITTANCE FUNCTIONS:

$$(a) \quad Y(s) = (s^2 + 7s + 12) / (s^2 + 3s + 2) \\ = (s+3)(s+4) / (s+1)(s+2)$$

$$s = -1 \text{ (pole)} ; s = -2 \text{ (pole)} ; s = -3 \text{ (zero)} ; z = -4 \text{ (zero)}$$

SO, $Y(s)$ IS NOT REALIZABLE. ✓

$$(c) \quad Y(s) = (s^2 + 3s + 2) / (s + 5) = (s+1)(s+2) / (s+5)$$

$$s = -1 \text{ (zero)} ; s = -2 \text{ (zero)} ; s = -5 \text{ (pole)}$$

SO, $Y(s)$ IS NOT REALIZABLE. ✓

$$(e) \quad Y(s) = (s + 1.5) / (s^2 + 2s + 1) \triangleq A(s) / B(s)$$

Because degree of $A(s) = 1 <$ degree of $B(s) = 2$.

SO, $Y(s)$ IS NOT REALIZABLE. ✓

$$(g) \quad Y(s) = (s^3 + 6s^2 + 11s + 6) / (s^2 + 4s + 3.75)$$

$$= (s+3)(s+1)(s+2) / (s+1.5)(s+2.5)$$

$Y(s)$ satisfies ALL PROPERTIES FOR 1-5.

$$Y(s) = [(s^3 + 4s^2 + 3.75s) + (2s^2 + 7.25s + 6)] / [(s+1.5)(s+2.5)]$$

$$= s + (2s^2 + 7.25s + 6) / [(s+1.5)(s+2.5)]$$

$$= s + [(2s^2 + 8s + 7.5) - (0.75s + 1.5)] / [(s+1.5)(s+2.5)]$$

$$= s + 2 - \frac{0.375}{s+1.5} - \frac{0.375}{s+2.5}$$

SATISFY PROPERTY YRC 6.

$Y(s)$ DOES'NT HAVE A POLE AT $s=0$. PRO. YRC 7 HOLDS.

$$Y(0) = 0 + 2 - \frac{0.375}{0+1.5} - \frac{0.375}{0+2.5}$$

$$\frac{dY(\sigma)}{d\sigma} = 1 + \frac{0.375}{(\sigma+1.5)^2} + \frac{0.375}{(\sigma+2.5)^2} > 0 \quad \text{PRO. YRC 8 HOLDS.}$$

SO, $Y(s)$ IS REALIZABLE. ✓

6-2 CONT.

$$(i) \quad Y(s) = (s^2 + 3s + 2) / (s^3 + 6s^2 + 8.75s + 3) \triangleq A(s) / B(s)$$

Because degree of $A(s) = 2 <$ degree of $B(s) = 3$

SO, $Y(s)$ IS NOT REALIZABLE. ✓

6-8. Realize the following RC DP admittance functions by Foster's two forms and Cauer's two forms.

$$(c) \quad Y(s) = (s+1)(s+5)/(s+4)(s+6)$$


$$= (s^2+6s+5)/(s^2+10s+24)$$

FOSTER'S FIRST FORM:

$$Z(s) = (s^2+10s+24)/(s^2+6s+5) = [(s^2+6s+5) + (4s+19)]/(s^2+6s+5)$$

$$= 1 + (4s+19)/(s+1)(s+5) = 1 + \frac{15/4}{s+1} + \frac{1/4}{s+5}$$
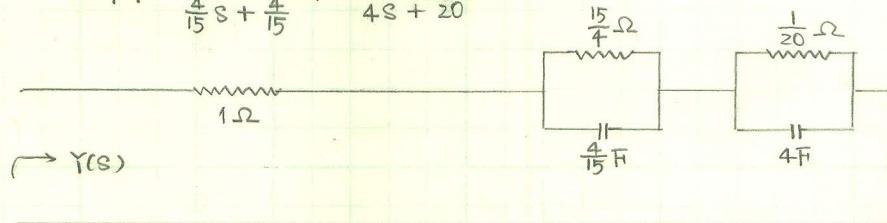
$$= 1 + \frac{1}{\frac{4}{15}s + \frac{4}{15}} + \frac{1}{4s+20}$$



CHECK: $1 + \frac{15/4}{s+1} + \frac{1/4}{s+5} = (s^2+6s+5 + \frac{15}{4}s + \frac{75}{4} + \frac{s}{4} + \frac{1}{4})/(s+1)(s+5)$


$$= (s^2+10s+24)/(s+1)(s+5) = Z(s) \quad \text{CHECKED!}$$

FOSTER'S SECOND FORM:

$$Y(s) = (s+1)(s+5)/(s+4)(s+6)$$

$$Y(s)/s = (s+1)(s+5)/s(s+4)(s+6) = \frac{5/24}{s} + \frac{3/8}{s+4} + \frac{5/12}{s+6}$$
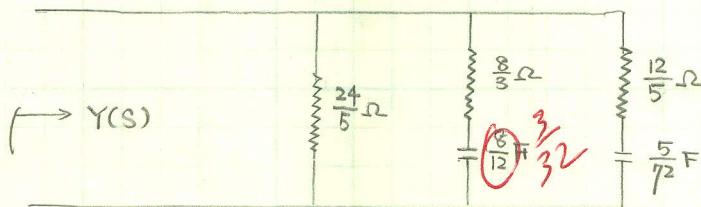
$$Y(s) = 5/24 + \frac{1}{\frac{8}{3} + \frac{1}{8/12 \cdot s}} + \frac{1}{\frac{12}{5} + (\frac{5}{72} s)^{-1}}$$



CHECK: $5/24 + \frac{3s}{8(s+4)} + \frac{5s}{12(s+6)}$

$$= [5(s+4)(s+6) + 9s(s+6) + 10s(s+4)]/24(s+4)(s+6)$$

$$= (s^2+6s+5)/(s+4)(s+6) = Y(s) \quad \text{CHECKED!!}$$

42,381 50 SHEETS 5 SQUARE
42,382 100 SHEETS 5 SQUARE
42,383 200 SHEETS 5 SQUARE
NATIONAL MANUFACTURING

CAUER'S FIRST FORM:

$$Y(s) = (s^2 + 6s + 5) / (s^2 + 10s + 24)$$

$$Z(s) = (s^2 + 10s + 24) / (s^2 + 6s + 5)$$

$$\begin{array}{r} 1 \\ s^2 + 6s + 5 \overline{) s^2 + 10s + 24} \\ \underline{4s + 19} \\ 8s + 19/4s \\ \underline{5/4s + 5} \\ 4s + 19 \\ \underline{4s + 16} \\ 3 \end{array}$$

$$\begin{array}{r} 5/12s \\ 5/4s + 5 \overline{) 5/4s + 5} \\ \underline{5/4s} \\ 5 \\ \underline{3} \\ 3 \\ \underline{0} \end{array}$$

CHECK: IT'S MORE DIFFICULT TO CHECK THE RESULT THAN TO RE-DO IT.

IN ORDER TO CHECK IN EASY WAY, WE LET $s = j\omega$. CHOOSE

$$\omega = 1 \text{ rad/s}, Z_{\text{GIVEN}}(j1) = 2.923 - j1.885 \Omega$$

$$Z_{\text{REALIZ.}} = 2.92308 - j1.88462 \Omega$$

Now, I DARE TO SAY 95% CHECKED!

Cauer's second Form: $Y(s) = (s^2 + 6s + 5) / (s^2 + 10s + 24)$

$$Z(s) = (s^2 + 10s + 24) / (s^2 + 6s + 5)$$

$$\begin{array}{r} 5/24 \\ 24 + 10s + s^2 \overline{) 5 + 6s + s^2} \\ \underline{5 + 25/12s + 5/24s^2} \\ 47/12s + 19/24s^2 \\ \underline{24 + 228/47s} \\ 242/47 + s \\ \underline{2209/2904} \\ 47/12 + 19/24s \\ \underline{47/12 + 2209/2904s} \\ 166.139/s \\ 242/47 + s \\ \underline{242/47} \\ 45 \\ \underline{1452} \\ 45 \\ \underline{1452} \\ 0 \end{array}$$


check - 2

d) $Y(s) = s(s+4)(s+6)/(s+1)(s+5)$

FOSTER'S FIRST FORM:

$Z(s) = (s+1)(s+5)/s(s+4)(s+6)$

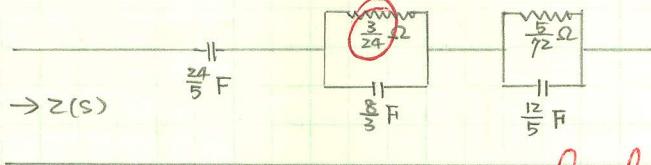$= \frac{5/24}{s} + \frac{3/8}{s+4} + \frac{5/12}{s+6} = \frac{1}{\frac{24}{5}s} + \frac{1}{\frac{8}{3}s + \frac{24}{3}} + \frac{1}{\frac{12}{5}s + \frac{72}{5}}$




check?

-4

FOSTER'S SECOND FORM:

$Y(s)/s = (s+4)(s+6)/(s+1)(s+5) = 1 + \frac{15/4}{s+1} + \frac{1/4}{s+5}$

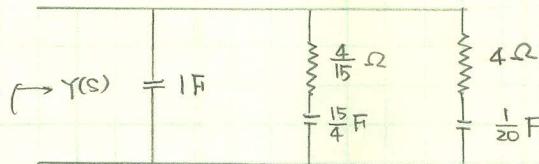$Y(s) = s + \frac{1}{\frac{4}{15} + \frac{1}{15}s} + \frac{1}{4 + \frac{1}{20}s}$




check?

-2

CAUER'S FIRST FORM:

$Y(s) = (s^2 + 10s^2 + 24s)/(s^2 + 6s + 5)$

$$\begin{array}{r} s \\ s^2 + 6s + 5 \overline{) s^3 + 10s^2 + 24s} \\ \underline{s^3 + 6s^2 + 5s} \\ 4s^2 + 19s \end{array} \quad \begin{array}{r} \frac{1}{4} \\ s^2 + 6s + 5 \overline{) s^2 + \frac{19}{4}s} \\ \underline{\frac{5}{4}s + 5} \\ \frac{16}{5}s \end{array} \quad \begin{array}{r} \frac{16}{5}s \\ 4s^2 + 19s \overline{) 4s^2 + 16s} \\ \underline{3s + 5} \\ 3s \end{array} \quad \begin{array}{r} \frac{5}{12} \\ \frac{5}{4}s \overline{) \frac{5}{4}s + 5} \\ \underline{\frac{5}{4}s} \\ 5 \end{array} \quad \begin{array}{r} \frac{3}{5}s \\ 3s \overline{) 3s} \\ \underline{0} \\ 0 \end{array}$$

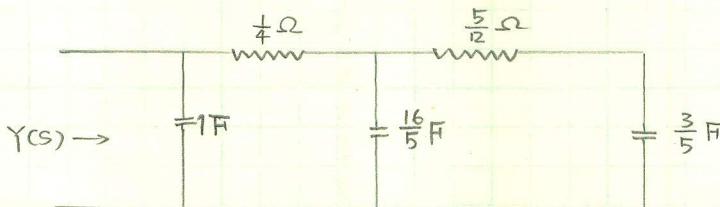

check?

-2

6-8 d) (CONT.)

Cauer's second form: $Z(s) = (s^2 + 6s + 5) / (s^3 + 10s^2 + 24s)$

$$24s + 10s^2 + s^3 \overline{) 5 + 6s + s^2}$$


$$\begin{array}{r} 5 \\ \hline 5 + \frac{25}{12}s + \frac{5}{24}s^2 \\ \hline \frac{47}{12} + \frac{19}{24}s \end{array} \overline{) 24 + 10s + s^2}$$

$$\begin{array}{r} \frac{288}{47} \\ \hline 24 + \frac{288}{47}s \\ \hline \frac{242}{47}s + s^2 \end{array} \overline{) \frac{47}{12} + \frac{19}{24}s}$$

$$\begin{array}{r} \frac{2209}{2904}s \\ \hline \frac{47}{12} + \frac{19}{24}s \\ \hline \frac{47}{12} + \frac{2209}{2904}s \end{array} \overline{) \frac{166139}{1000}}$$

$$\begin{array}{r} \frac{45}{1452} \\ \hline \frac{242}{47} + s \\ \hline \frac{242}{47} \\ \hline s \end{array} \overline{) \frac{1452s}{1452}}$$
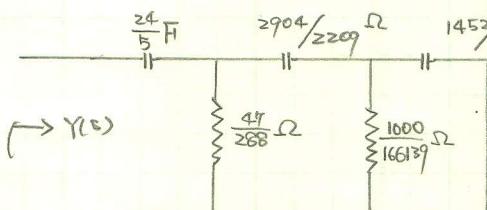
$$\begin{array}{r} \frac{45}{1452} \\ \hline \frac{45}{1452} \\ \hline 0 \end{array}$$



check - 2


6-8 e) $Y(s) = (s+1)(s+5)(s+10) / (s+2)(s+6)(s+12)$

$Z(s) = (s+2)(s+6)(s+12) / (s+1)(s+5)(s+10)$

FOSTER'S FIRST FORM:

$$Z(s) = 1 + \frac{1.5278}{s+1} + \frac{1.05}{s+5} + \frac{1.4222}{s+10}$$
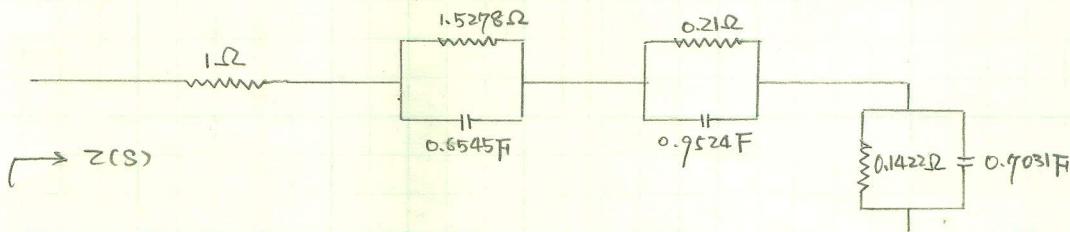
$$= 1 + \frac{1}{0.6545s + \frac{1}{1.5278}} + \frac{1}{0.9524s + \frac{1}{0.21}} + \frac{1}{0.7031s + \frac{1}{0.1422}}$$




check - 2

FOSTER'S SECOND FORM:

$Y(s)/s = (s+1)(s+5)(s+10) / s(s+2)(s+6)(s+12)$

$$= \frac{0.3472}{s} + \frac{0.3}{s+2} + \frac{0.1389}{s+6} + \frac{0.2139}{s+12}$$
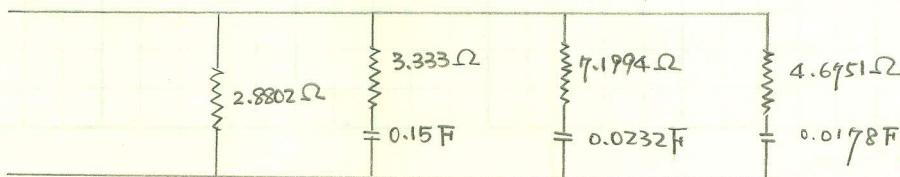
$$= \frac{1}{2.8802s} + \frac{1}{3.333s + \frac{1}{0.15}} + \frac{1}{7.1994s + \frac{1}{0.0232}} + \frac{1}{4.6751s + \frac{1}{0.0178}}$$



check - 2

6-8 e) (CONT.) Cauer's first FORM:

$$Y(s) = (s+1)(s+5)(s+10)/(s+2)(s+6)(s+12)$$

$$= (s^3 + 16s^2 + 65s + 50)/(s^3 + 20s^2 + 108s + 142)$$

$$Z(s) = (s^3 + 20s^2 + 108s + 142)/(s^3 + 16s^2 + 65s + 50)$$

$$\frac{1}{s^3 + 16s^2 + 65s + 50} \sqrt{s^3 + 20s^2 + 108s + 142}$$

$$\frac{\frac{1}{4}s}{s^3 + 16s^2 + 65s + 50}$$

$$\frac{4s^2 + 43s + 92}{s^3 + \frac{43}{4}s^2 + 23s}$$

$$\frac{\frac{16}{21}}{\frac{21}{4}s^2 + 42s + 50}$$

$$\frac{\frac{121}{179}}{4s^2 + 32s + \frac{800}{21}}$$

$$\frac{0.4021}{11s + \frac{1132}{21}}$$

$$\frac{\frac{21}{4}s}{4s^2 + 43s + 92}$$

$$\frac{\frac{21}{4}s^2 + 283s}{11s + \frac{1132}{21}}$$

$$\frac{\frac{121}{179}}{\frac{179}{11}s + 50}$$

$$\frac{0.1781s}{11s + 33.799}$$

$$\frac{20.106}{3.58s + 50}$$

$$\frac{20.106}{3.58s}$$

$$\frac{0.4021}{20.106}$$

$$\frac{20.106}{20.106}$$

$$0$$

Cauer's second FORM:

check -2

$$\frac{0.3521}{50 + 65s + 16s^2 + s^3}$$

$$\frac{5.265/s}{26.97s + 8.96s^2 + 0.6479s^3}$$

$$\frac{5.265/s}{142 + 108s + 20s^2 + s^3}$$

$$\frac{38.01/s}{60.82 + 16.59s + s^2}$$


$$\frac{0.182}{8.8 + s}$$

$$\frac{0.0231s}{1.6 + 0.205s}$$

$$\frac{0.0231}{1.6 + 0.182s}$$

$$\frac{0.0231s}{8.8 + s}$$

$$\frac{0.0231}{8.8}$$
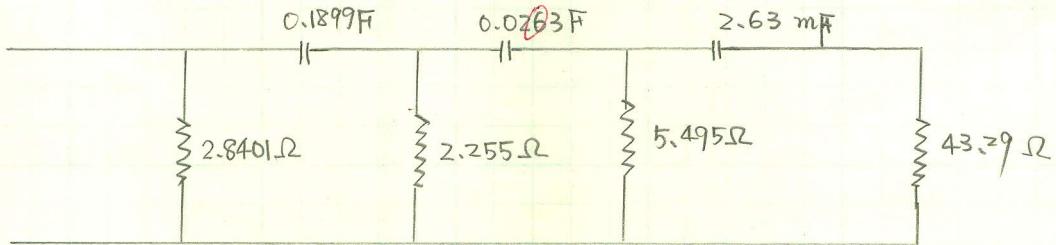
$$0$$


check -2

6-10 (b) $Z(s) = (s+2)(s+4)/(s+1)(s+3)(s+5)$
 $= (s^2+6s+8)/(s^3+9s^2+23s+15)$

Cauer's second form = (FOR TWO CAPACITORS)

$$8+6s+s^2 \sqrt{\frac{15}{8} / (15+23s+9s^2+s^3)}$$

$$15 + \frac{45}{4}s + \frac{15}{8}s^2$$

$$\frac{47}{4}s + \frac{57}{8}s^2 + s^3$$

$$\frac{32}{47s}$$

$$8 + \frac{228}{47}s + \frac{32}{47}s^2$$

$$\frac{2209}{216}$$

$$\frac{54}{47} + \frac{15}{47}s$$

$$\sqrt{\frac{47}{4} + \frac{57}{8}s + s^2}$$

$$\frac{47}{4} + \frac{705}{216}s$$

$$\frac{834}{216}s + s^2$$

$$\frac{0.2976/s}{\frac{54}{47} + \frac{15}{47}s}$$

$$\frac{54}{47} + 0.2976s$$

$$178.76$$

$$0.0216 \sqrt{3.86 + s}$$

$$3.86$$

$$\frac{0.0216/s}{0.0216} \quad s$$

$$0$$


$$Y_1(s) = \frac{1}{178.76} + \frac{s}{0.0216}$$

$$= \frac{0.0216 + 178.76s}{3.86} = 46.3s + 0.0056$$

Cauer's first form = (COMPLETION)

$Y_1(s) = 46.3s + 0.0056 = 46.3s + \frac{1}{178.76}$

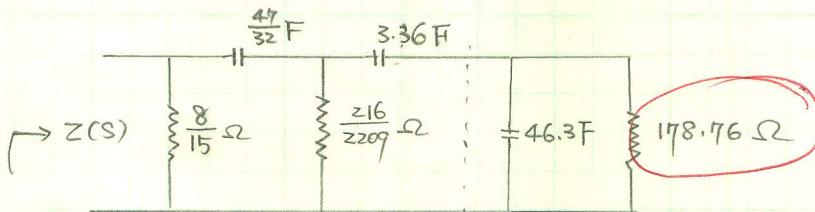$Z_1(s) = \frac{1}{46.3s + \frac{1}{178.76}}$



-3
check.

(c) 1. Cauer's first form for one capacitor:

$Y(s) = (s^3+9s^2+23s+15)/(s^2+6s+8) = (s^3+6s^2+8s+3s^2+15s+15)/(s^2+6s+8)$
 $= s + (3s^2+15s+15)/(s^2+6s+8)$

2. Cauer's second form for one capacitor:

$$8+6s+s^2 \sqrt{\frac{15}{8} / (15+15s+3s^2)}$$

$$15 + \frac{45}{4}s + \frac{15}{8}s^2$$


$$\frac{32}{15s}$$

$$\frac{15}{4}s + \frac{9}{8}s^2$$

$$\sqrt{8+6s+s^2}$$

$$8 + \frac{12}{5}s$$


$$\frac{18}{5} + s$$

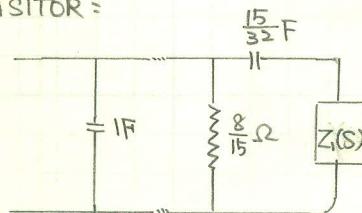

-3
check

$\frac{15}{8} + \frac{1}{Z_1(s) + \frac{32}{15s}} = (3s^2+15s+15)/(s^2+6s+8)$

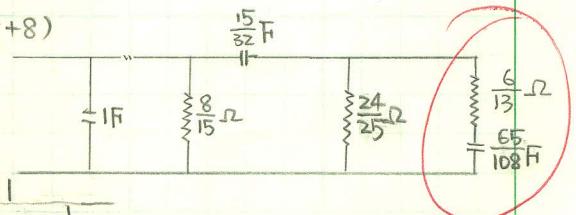$\therefore Z_1(s) = \frac{40s+144}{45s+150}$



FOSTER'S SECOND FORM FOR COMPLETION = $Y_1(s) = \frac{25}{24} + \frac{1}{\frac{6}{13} + \frac{1}{\frac{65}{108}s}}$

6-12 d) $Z(s) = (s+2)(s+4)/s(s+3) + (s^2+3)(s^2+6)/s(s^2+4)$

$$Z_1(s) = (s+2)(s+4)/s(s+3)$$


$$= 1 + \frac{\frac{10}{3}}{s} + \frac{\frac{1}{3}}{s+3} = 1 + \frac{1}{\frac{3}{10}s} + \frac{1}{3s+\frac{1}{3}}$$

$$Z_2(s) = (s^2+3)(s^2+6)/s(s^2+4)$$

$$\frac{Z_2(s)}{s} \Big|_{s^2=p} = (p+3)(p+6)/p(p+4) = 1 + \frac{\frac{9}{2}}{p} + \frac{\frac{1}{2}}{p+4}$$

$$Z_2(s) = s + \frac{1}{\frac{2}{9}s} + \frac{1}{2s + \frac{1}{8}s}$$


RLC REALIZATION:

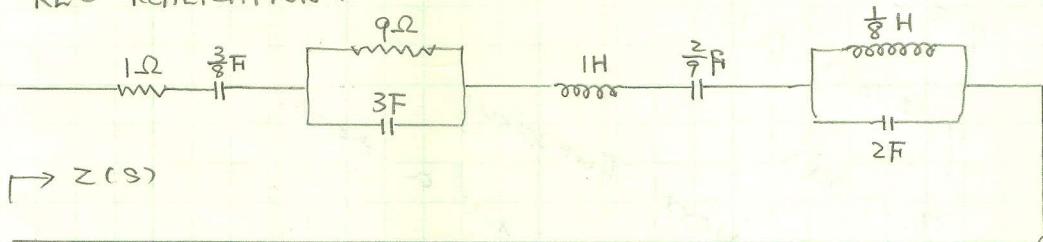

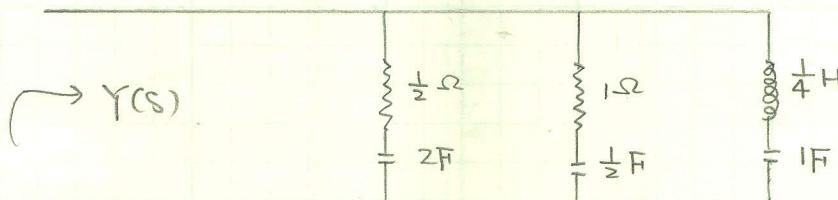6-13 f) $Y(s) = (3s^4 + 9s^3 + 24s^2 + 28s) / (s+1)(s+2)(s^2+4)$

$$\frac{Y(s)}{s} = \frac{2}{s+1} + \frac{1}{s+2} + \frac{4}{s^2+4}$$

$$Y(s) = \frac{1}{\frac{1}{2} + \frac{1}{2s}} + \frac{1}{1 + \frac{1}{2}s} + \frac{1}{\frac{1}{4}s + \frac{1}{s}}$$



CHECK: $\frac{1}{4}s + \frac{1}{s} = \frac{s^2+4}{4s} \Rightarrow \frac{4s}{s^2+4}$

$$1 + \frac{2}{s} = \frac{s+2}{s} \Rightarrow \frac{s}{s+2}$$

$$\frac{1}{2} + \frac{1}{2s} = \frac{s+1}{2s} \Rightarrow \frac{2s}{s+1}$$

$$Y(s) = \frac{2s}{s+1} + \frac{s}{s+2} + \frac{4s}{s^2+4}$$

$$= [2s(s+2)(s^2+4) + s(s+1)(s^2+4) + 4s(s+1)(s+2)] / (s+1)(s+2)(s^2+4)$$

$$= (3s^4 + 9s^3 + 24s^2 + 28s) / (s+1)(s+2)(s^2+4) \quad \text{CHECKED!}$$

Handwritten signature and date: 6/15/18

PROBLEM 1. FROM $\xi_i = a^2 \xi_{11} + 2ab \xi_{12} + b^2 \xi_{22} \geq 0 \Rightarrow \xi_{11} \xi_{22} - \xi_{12}^2 \geq 0$ 30
30

SOLUTION: $\xi_i = a^2 \xi_{11} + 2ab \xi_{12} + b^2 \xi_{22} \geq 0 \quad \dots (19)$

IF $ab > 0$, WE GET

$$\frac{1}{2} \left[\frac{a}{b} \xi_{11} + \frac{b}{a} \xi_{22} \right] + \xi_{12} \geq 0 \quad \dots (a)$$

IF $ab < 0$, THEN $\frac{a}{b} < 0$ and $\frac{b}{a} < 0$

LET $x = -\frac{a}{b} > 0$, WE GET

$$\frac{1}{2} \left[\frac{a}{b} \xi_{11} + \frac{b}{a} \xi_{22} \right] + \xi_{12} \leq 0$$

$$\Rightarrow -\frac{1}{2} \left[x \xi_{11} + \frac{1}{x} \xi_{22} \right] + \xi_{12} \leq 0$$

$$\frac{1}{2} \left[x \xi_{11} + \frac{1}{x} \xi_{22} \right] - \xi_{12} \geq 0 \quad \dots (b)$$

FROM (a) AND (b), WE OBTAIN

$$\frac{1}{2} \left[\frac{\alpha}{b} \xi_{11} + \frac{b}{\alpha} \xi_{22} \right] \pm \xi_{12} \geq 0 \quad \dots (c)$$

$$\text{WHERE } \alpha = \begin{cases} a & \text{IF } ab > 0 \\ -a & \text{IF } ab < 0 \end{cases}$$


INEQUALTION (c) is just same as the inequalTION (21)

ON PAGE 261 IN NOTES. HENCE, WITH THE SAME MOTHEd

IN THE NOTES, WE HAVE

$$\xi_{11} \xi_{22} - \xi_{12}^2 \geq 0.$$

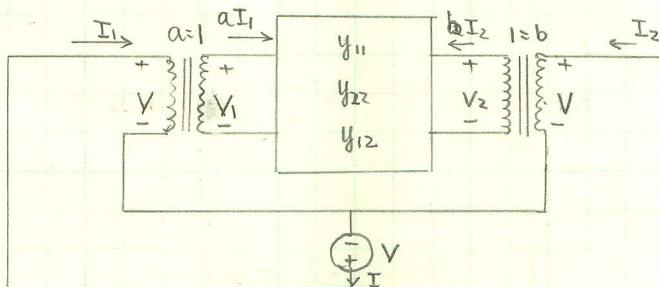PROBLEM 2: Develop residue and real part conditions FOR the y -parameters OF a 2-port RLC network.



$$\begin{cases} aI_1 = y_{11}V_1 + y_{12}V_2 \\ bI_2 = y_{12}V_1 + y_{22}V_2 \end{cases} \quad \text{and} \quad \begin{cases} V_1 = V/a \\ V_2 = V/b \end{cases}$$

$$\begin{aligned} I = I_1 + I_2 &= \frac{1}{a}(y_{11}V_1 + y_{12}V_2) + \frac{1}{b}(y_{12}V_1 + y_{22}V_2) \\ &= \left(\frac{1}{a^2}y_{11} + \frac{2}{ab}y_{12} + \frac{1}{b^2}y_{22}\right) \cdot V \end{aligned}$$

$$\therefore Y_{in}(s) = \frac{1}{a^2}y_{11} + \frac{2}{ab}y_{12} + \frac{1}{b^2}y_{22}$$

Suppose $Y_{in}(s)$ has a pole at $s = p_i$

$$z_{11}^{(i)} \triangleq y_{11}(s - p_i) \Big|_{s=p_i}$$

$$z_{12}^{(i)} \triangleq y_{12}(s - p_i) \Big|_{s=p_i}$$

$$z_{22}^{(i)} \triangleq y_{22}(s - p_i) \Big|_{s=p_i}$$

$$\therefore z^{(i)} = \frac{1}{a^2}z_{11}^{(i)} + \frac{2}{ab}z_{12}^{(i)} + \frac{1}{b^2}z_{22}^{(i)}$$

FOR AN RC NETWORK, WE KNOW THAT THE POLE OF Y_{RC} ARE SIMPLE, AND HAVE NEGATIVE RESIDUES AT FINITE POLES, ALSO HAVE A POSITIVE RESIDUE AT INFINITY POLE. SO, $z^{(i)} \leq 0$ p_i IS FINITE.


$z^{(i)} \geq 0$ p_i IS INFINITY.

FOR AN LC NETWORK, THE POLES OF Y_{LC} ARE SIMPLE AND HAVE POSITIVE RESIDUES. SO, $z^{(i)} \geq 0$.



Now, how can I derive equations like (26) and (29) in the notes' book?

PROBLEM 3 : USE T AND π NETWORKS TO VERIFY (30) AND (31)

SOLUTION: FOR NETWORK :

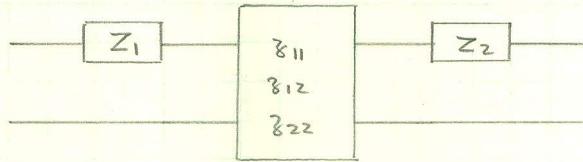


EQUALS TO : (T NETWORK)

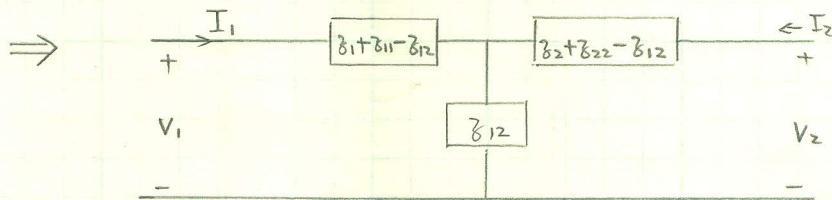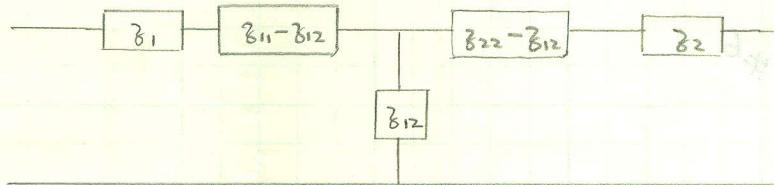

$$\begin{cases} V_1 = I_1(z_1 + z_{11} - z_{12}) + (I_1 + I_2)z_{12} \\ V_2 = I_2(z_2 + z_{22} - z_{12}) + (I_1 + I_2)z_{12} \end{cases}$$

$$\Rightarrow \begin{cases} V_1 = I_1 \cdot (z_1 + z_{11}) + I_2 \cdot z_{12} \\ V_2 = I_1 \cdot z_{12} + I_2 \cdot (z_2 + z_{22}) \end{cases} \Rightarrow \begin{cases} z'_{11} = z_1 + z_{11} \text{ and } z'_{12} = z_{12} \\ z'_{22} = z_2 + z_{22} \end{cases}$$

FOR NETWORK :

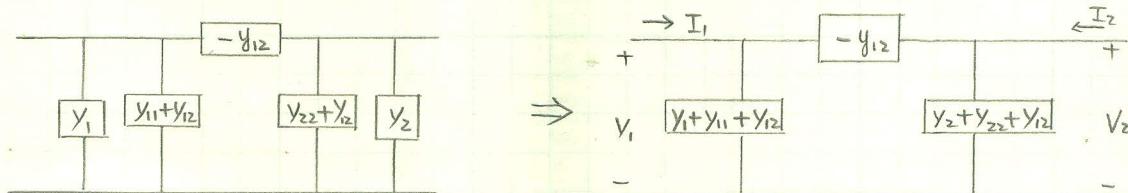


$$\begin{cases} I_1 = V_1(y_1 + y_{11} + y_{12}) + (V_1 - V_2)(-y_{12}) \\ I_2 = V_2(y_2 + y_{22} + y_{12}) + (V_2 - V_1)(-y_{12}) \end{cases}$$

$$\Rightarrow \begin{cases} I_1 = V_1 \cdot (y_1 + y_{11}) + y_{12} \cdot V_2 \\ I_2 = V_1 y_{12} + V_2 \cdot (y_2 + y_{22}) \end{cases} \Rightarrow \begin{cases} y'_{11} = y_1 + y_{11} \text{ and } y'_{12} = y_{12} \\ y'_{22} = y_2 + y_{22} \end{cases}$$

HOMEWORK PROBLEM 3.28 ON PAGE 280 IN NOTES :

 $\frac{30}{30}$

A LATTICE NETWORK :

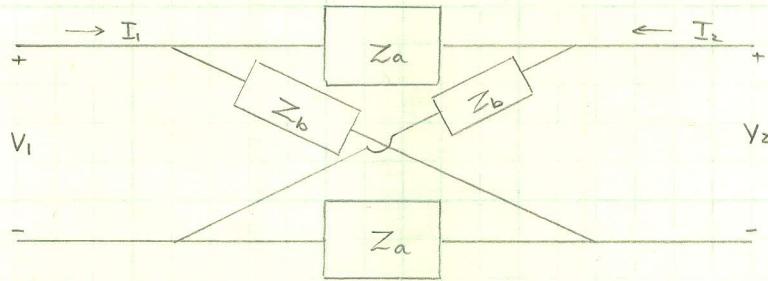


$$\text{LET } \begin{cases} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{12} I_1 + Z_{22} I_2 \end{cases}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{1}{2} (Z_a + Z_b)$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{1}{2} (Z_a + Z_b)$$

$$Z_{12} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{1}{2} (Z_b - Z_a)$$

(a) SHUNT-TYPE CAUER equivalent :

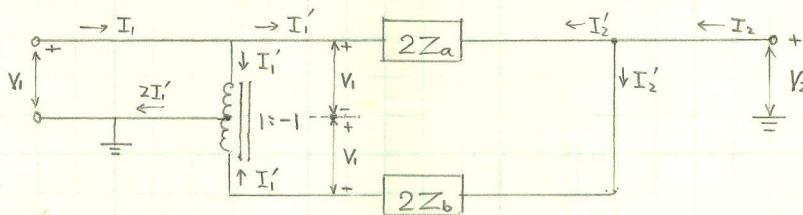

$$I_2=0 : 2V_1 = I_1' \cdot (2Z_a + 2Z_b) = 2I_1' (Z_a + Z_b) = I_1 (Z_a + Z_b)$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{1}{2} (Z_a + Z_b)$$

$$V_2 = I_1' \cdot 2Z_b - V_1 = -I_1' \cdot 2Z_a + V_1 \Rightarrow V_1 = (Z_a + Z_b) I_1'$$

$$\Rightarrow V_2 = I_1' \cdot (Z_b - Z_a)$$

$$Z_{12} = \frac{V_2}{I_1} \Big|_{I_2=0} = \frac{V_2}{2I_1'} = \frac{1}{2} (Z_b - Z_a)$$


$$I_1=0 : V_2 = 2Z_a \cdot I_2' + V_1 = 2Z_b \cdot I_2' - V_1 \Rightarrow V_1 = (Z_b - Z_a) I_2'$$

$$V_2 = (Z_a + Z_b) I_2'$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = \frac{1}{2} (Z_a + Z_b)$$

CHECKED!

(b) Hybrid lattice equivalent:

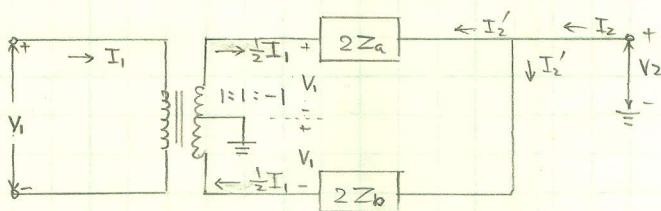

$$I_2 = 0 : 2V_1 = \frac{1}{2} I_1 \cdot (2Z_a + 2Z_b) = (Z_a + Z_b) \cdot I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{1}{2} (Z_a + Z_b)$$

$$V_2 = -\frac{1}{2} I_1 \cdot 2Z_a + V_1 = \frac{1}{2} I_1 \cdot 2Z_b - V_1 \Rightarrow \frac{1}{2} (Z_a + Z_b) \cdot I_1$$

$$\Rightarrow V_2 = \frac{1}{2} (Z_b - Z_a) \cdot I_1$$


$$Z_{12} = \frac{V_2}{V_1} = \frac{1}{2} (Z_b - Z_a)$$

 $I_1 = 0$: same as Z_{22} in part (a)

$$Z_{22} = \frac{1}{2} (Z_a + Z_b)$$

CHECKED!

(c) Bridged-T equivalent:

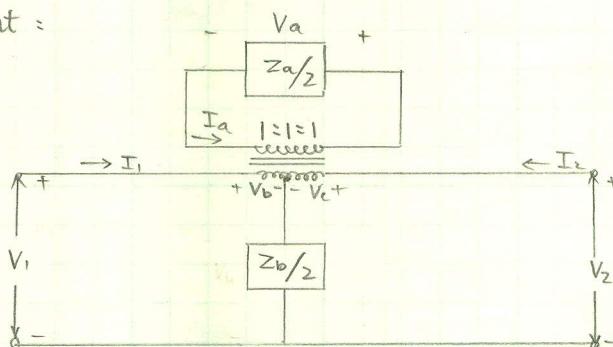

$$I_2 = 0 : I_a = I_1, V_b = V_a = -I_a \cdot \frac{Z_a}{2} = -I_1 \cdot \frac{Z_a}{2}$$

$$V_1 = V_b + I_1 \cdot \frac{Z_b}{2} = \frac{1}{2} (Z_a + Z_b) \cdot I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{1}{2} (Z_a + Z_b)$$

$$V_c = -V_b = -\frac{Z_a}{2} \cdot I_1$$

$$V_2 = -\frac{Z_a}{2} I_1 + I_1 \cdot \frac{Z_b}{2} = \frac{1}{2} (Z_b - Z_a) \cdot I_1$$


$$I_1 = 0 : I_a = -I_2, V_c = -V_a = \frac{1}{2} \cdot Z_a \cdot I_2$$

$$V_2 = \frac{1}{2} (Z_a + Z_b) I_2$$

$$Z_{22} = \frac{1}{2} (Z_a + Z_b)$$

CHECKED!

(d) Series-type Coupler equivalent.

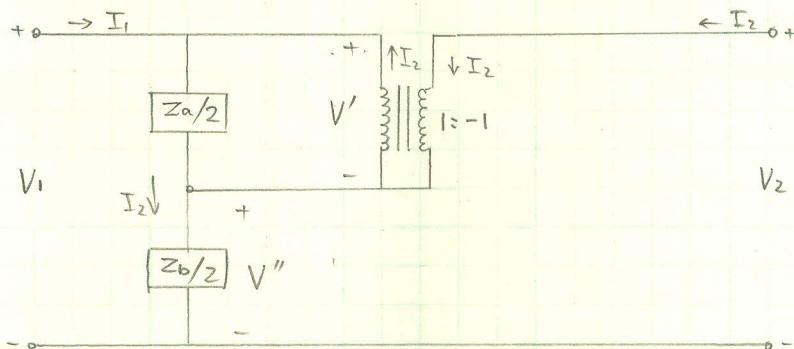

$$\text{Let } I_2 = 0, \quad V_1 = \left(\frac{1}{2} Z_a + \frac{1}{2} Z_b\right) I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{1}{2} (Z_a + Z_b)$$

$$V_2 = -V' + V'' = \frac{1}{2} (Z_b - Z_a) \cdot I_1$$

$$Z_{12} = \frac{V_2}{I_1} = \frac{1}{2} (Z_b - Z_a)$$


$$\text{Let } I_1 = 0, \quad V_2 = (Z_a/2 + Z_b/2) \cdot I_2$$

$$Z_{22} = \frac{1}{2} (Z_a + Z_b)$$

· SHOWN !

FOR HOMEWORK

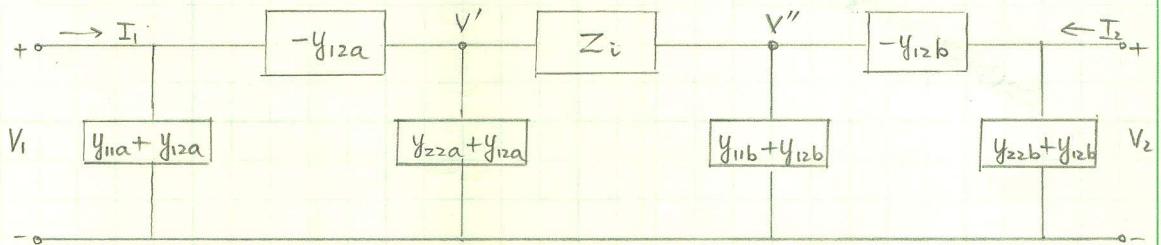Repeat the analysis on pages 281-283 by considering a shunt element of a ladder between the ends of the ladder represented by π networks and y -parameters. Show that zero impedance of the shunt element may not necessarily imply zero transmission.



$$\frac{V'}{V_1} = H_a(s) = -\frac{y_{12a}}{y_{22a}}$$

$$\frac{V_2}{V''} = H_b(s) = -\frac{y_{12b}}{y_{22b}}$$

$$\frac{V''}{V'} = H'(s) = \frac{1}{(y_{11b} + y_{12b})Z_i + 1}$$

$$\begin{aligned} \therefore H(s) &= \frac{V_2}{V_1} = \frac{V_2}{V''} \cdot \frac{V''}{V'} \cdot \frac{V'}{V_1} = H_b(s) \cdot H'(s) \cdot H_a(s) \\ &= \frac{y_{12a} y_{12b}}{y_{22a} y_{22b} [(y_{11b} + y_{12b})Z_i + 1]} \end{aligned}$$

Suppose Z_i has a zero at $s = s_0$.

$$H(s_0) = y_{12a}(s_0) \cdot y_{12b}(s_0) / (y_{22a}(s_0) \cdot y_{22b}(s_0))$$

is not necessarily to be zero.

So, zero impedance of the shunt element may not necessarily imply zero transmission.

120

120

ANALOG AND DIGITAL FILTER

HOMEWORK #8

NOV. 3, 1986

BENMEI CHEN

CHAPTER SEVEN: PROBLEM 7.3 (c) (e) (h)

7.6(e) (g)

42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-389 200 SHEETS 5 SQUARE
MADE IN U.S.A.



7-3 SYNTHESIZE EACH OF THE FOLLOWING TRANSFER FUNCTIONS BY TWO RC LADDER NETWORKS [VIA $Z_{11}(s)$ AND $Y_{22}(s)$]

(c) $H(s) = \frac{k}{(s+1)(s+4)}$


1. $Z_{11}(s) = \frac{(s+1)(s+4)}{(s+0.5)(s+2)} = \frac{s^2 + 5s + 4}{s^2 + 2.5s + 1}$

$Z_{21}(s) = \frac{k}{(s+0.5)(s+2)}$


$$\begin{aligned} & \frac{1}{s^2 + 2.5s + 1} \sqrt{\frac{s^2 + 5s + 4}{s^2 + 2.5s + 1}} \\ & \frac{\frac{2}{5}s}{2.5s + 3} \sqrt{\frac{s^2 + 2.5s + 1}{s^2 + \frac{6}{5}s}} \\ & \frac{\frac{25}{13}}{1.3s + 1} \sqrt{\frac{2.5s + 3}{2.5s + \frac{25}{13}}} \\ & \frac{\frac{169}{140}s}{\frac{14}{13}} \sqrt{\frac{1.3s + 1}{1.3s}} \\ & \frac{14/13}{1} \sqrt{\frac{14/13}{14/13}} \end{aligned}$$

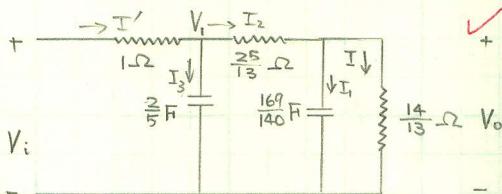2. $Y_{22}(s) = \frac{(s+1)(s+4)}{s+2} = \frac{s^2 + 5s + 4}{s+2}$; $Y_{12}(s) = -\frac{k}{s+2}$

$$\begin{aligned} & \frac{s}{s+2} \sqrt{\frac{s^2 + 5s + 4}{s+2s}} \\ & \frac{\frac{1}{3}}{3s + 4} \sqrt{\frac{s+2}{s+\frac{4}{3}}} \\ & \frac{\frac{9}{2}s}{\frac{2}{3}} \sqrt{\frac{3s+4}{3s}} \\ & \frac{\frac{1}{6}}{4} \sqrt{\frac{\frac{2}{3}}{\frac{2}{3}}} \end{aligned}$$



(VIA $Z_{11}(s)$)

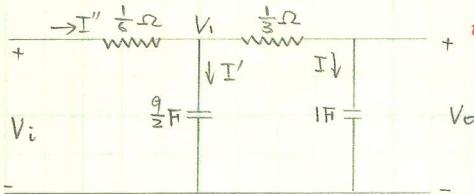

(VIA $Y_{22}(s)$)

CHECK: LET $I = 1A$ $V_0 = \frac{14}{13} V$

$I_1 = \frac{14}{13} / \frac{140}{169s} = \frac{13s}{10} \Rightarrow I_2 = 1 + 1.3s \Rightarrow$

$V_1 = 3 + 2.5s \Rightarrow I_3 = 1.2s + s^2$

$I' = s^2 + 2.5s + 1 \Rightarrow V_i = s^2 + 5s + 4$

$H(s) = V_0/V_i = \frac{14}{13} / (s+1)(s+4)$ CHECKED!

CHECK: LET $I = 1A \Rightarrow V_0 = 1/s$

$\Rightarrow V_1 = \frac{1}{3} + \frac{1}{s} \Rightarrow I' = \frac{3}{2}s + \frac{9}{2}$

$\Rightarrow I'' = \frac{3}{2}s + \frac{11}{2} \Rightarrow V_i = \frac{1}{4}s + \frac{11}{2} + \frac{1}{3} + \frac{1}{s} = \frac{1}{4}s + \frac{5}{4} + \frac{1}{s}$

$\Rightarrow H(s) = \frac{1/s}{(\frac{1}{4}s + \frac{5}{4} + \frac{1}{s})}$

$= \frac{1}{4} / (s^2 + 5s + 4) = \frac{1}{4} / (s+1)(s+4)$ CHECKED!

42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-389 200 SHEETS 5 SQUARE
MADE IN U.S.A.
NATIONAL

7.3 (e) $H(s) = ks^2 / [(s+1)(s+4)]$

1. $Z_{11}(s) = \frac{(s+1)(s+4)}{(s+0.5)(s+2)} = \frac{s^2 + 5s + 4}{s^2 + 2.5s + 1}$; $Z_{12}(s) = \frac{ks^2}{(s+0.5)(s+2)}$

$$\begin{array}{r} \frac{1}{4} \\ 4+5s+s^2 \overline{) 1+2.5s+s^2} \\ \underline{1+1.25s+\frac{1}{4}s^2} \\ 1.25s+\frac{3}{4}s^2 \\ \underline{1.25s+\frac{3}{4}s^2} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{16}{5s} \\ 1+1.25s+\frac{1}{4}s^2 \overline{) \frac{16}{5s}} \\ \underline{1+1.25s+\frac{1}{4}s^2} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{25}{52} \\ 4+\frac{12}{5}s \overline{) \frac{25}{52}} \\ \underline{4+\frac{12}{5}s} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{25}{52} \\ 1.25+\frac{3}{4}s \overline{) \frac{25}{52}} \\ \underline{1.25+\frac{3}{4}s} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{338}{35s} \\ 1.25+\frac{3}{4}s \overline{) \frac{338}{35s}} \\ \underline{1.25+\frac{3}{4}s} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{13}{5} + s \\ \frac{13}{5} + s \overline{) \frac{13}{5} + s} \\ \underline{\frac{13}{5} + s} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{7}{26} \\ \frac{7}{26} \overline{) \frac{7}{26}} \\ \underline{\frac{7}{26}} \\ 0 \end{array}$$


2. $V_{22}(s) = \frac{(s+1)(s+4)}{s+2} = \frac{s^2 + 5s + 4}{s+2}$; $Y_{12}(s) = -\frac{ks^2}{s+2}$

$$\begin{array}{r} \frac{2}{3s} \\ 2+s \overline{) \frac{2}{3s}} \\ \underline{2+s} \\ 0 \end{array}$$


$$\begin{array}{r} \frac{2}{3s} \\ 2+\frac{2}{3}s \overline{) \frac{2}{3s}} \\ \underline{2+\frac{2}{3}s} \\ 0 \end{array}$$

$$\begin{array}{r} \frac{9}{3+s} \\ \frac{9}{3+s} \overline{) \frac{9}{3+s}} \\ \underline{\frac{9}{3+s}} \\ 0 \end{array}$$
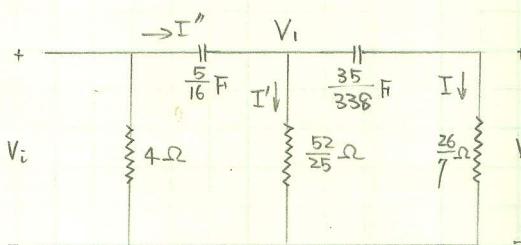
$$\begin{array}{r} \frac{1}{3s} \\ \frac{1}{3s} \overline{) \frac{1}{3s}} \\ \underline{\frac{1}{3s}} \\ 0 \end{array}$$



(VIA $Z_{11}(s)$)

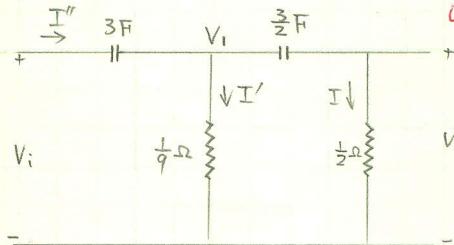

(VIA $Y_{22}(s)$)

CHECK = LET $I = 1A$, $V_o = \frac{26}{7} \Rightarrow$

$V_i = 3.7143 + 9.6571/s \Rightarrow I' = 1.7857 + 4.6429/s$

$\Rightarrow I'' = 2.7857 + 4.6429/s$

$\Rightarrow V_i = (2.7857 + 4.6429/s) \times 3.2/s + 3.7143 + 9.6571/s$

$= 14.9571/s^2 + 18.5713/s + 3.7143$

$= (s^2 + 5s + 4) / 0.2692s^2$

$H(s) = V_o/V_i = s^2 / (s^2 + 5s + 4)$ CHECKED!

CHECK = $I = 1A \Rightarrow V_o = \frac{1}{2} V$

$\Rightarrow V_i = \frac{1}{2} + \frac{2}{3s} \Rightarrow I' = \frac{9}{2} + \frac{6}{s}$

$\Rightarrow I'' = \frac{11}{2} + \frac{6}{s} \Rightarrow$

$V_i = (\frac{11}{2} + \frac{6}{s}) \cdot \frac{1}{3s} + \frac{1}{2} + \frac{7}{3s}$

$= \frac{2}{s^2} + \frac{5}{2s} + \frac{1}{2}$

$= \frac{s^2 + 5s + 4}{2s^2}$

$H(s) = s^2 / (s^2 + 5s + 4)$ CHECKED!

42.381 50 SHEETS 5 SQUARE
42.386 100 SHEETS 5 SQUARE
NATIONAL
MADE IN U.S.A.

7.3 (a) $H(s) = ks^2 / [(s+1)(s+2)(s+3)]$

1. $Z_{11}(s) = \frac{(s+1)(s+2)(s+3)}{(s+0.5)(s+1.5)(s+2.5)} = \frac{s^3 + 6s^2 + 11s + 6}{s^3 + 4.5s^2 + 5.75s + 1.875}$

USING CAUER'S FIRST FORM FOR ONE CAPACITOR.

$Z_{11}(s) = 1 + \frac{1.5s^2 + 5.25s + 4.125}{s^3 + 4.5s^2 + 5.75s + 1.875}$

$= 1 + \frac{1}{\frac{2}{3}s + \frac{s^2 + 3s + 1.875}{1.5s^2 + 5.25s + 4.125}}$

$Y'(s) = \frac{s^2 + 3s + 1.875}{1.5s^2 + 5.25s + 4.125}$


$= 0.4545 + \frac{1}{6.7226/s + \frac{1}{0.1972 + \frac{1}{139.2932/s + \frac{1}{0.0149}}}}$

2. $Y_{22}(s) = \frac{(s+1)(s+2)(s+3)}{(s+1.5)(s+2.5)} = \frac{s^3 + 6s^2 + 11s + 6}{s^2 + 4s + 3.75}$


USING CAUER'S SECOND FORM FOR TWO CAPACITORS.

$Y_{22}(s) = 1.6 + \frac{1}{0.8152/s + \frac{1}{11.138 + \frac{1}{0.1764/s + Z'(s)}}$

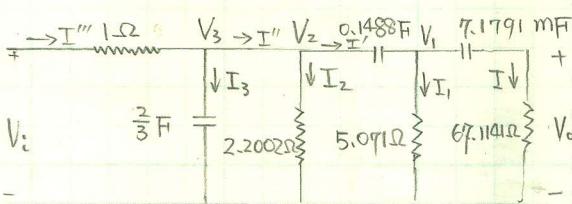$Z'(s) = \frac{1}{278.7738 + \frac{1}{0.0084/s}} = \frac{1}{278.7738 + 119.0476s}$



(VIA $Z_{11}(s)$)

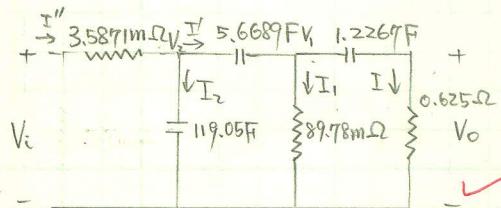

(VIA $Y_{22}(s)$)

CHECK: LET $I = 1A$, $V_o = 67.1141V \Rightarrow V_i = 67.1141 + 139.2932/s$

$\Rightarrow I_1 = 13.2349 + 27.4606/s \Rightarrow I' = 14.2349 + 27.4606/s$

$\Rightarrow V_2 = 67.1141 + 234.9579/s + 184.547/s^2 \Rightarrow I_2 = 30.5036 + 106.789/s + 83.8774/s^2$

$\Rightarrow I'' = 44.7385 + 134.2499/s + 83.8774/s^2$

$\Rightarrow I_3 = 44.7427s + 156.6386 + 123.0313/s$

$\Rightarrow I''' = 44.7427s + 201.3976 + 267.8689/s + 83.8774/s^2$

$\Rightarrow V_i = 44.7427s + 268.5117 + 502.8268/s + 268.4244/s^2$

$\Rightarrow H(s) = 1.5 s^2 / (s^2 + 6.0012s^2 + 11.2s + 599.93)$

CHECKED

CHECK: $I = 1 \Rightarrow V_o = 0.625 \Rightarrow V_i = 0.625 + 0.8152/s$

$\Rightarrow I_1' = 9.0797/s + 6.9613 \Rightarrow I' = 7.9613 + 9.0797/s$

$\Rightarrow V_2 = 2.2196/s + 1.6017/s^2 + 0.625$

$\Rightarrow I_2 = 264.2434 + 190.6824/s + 74.4063s$

$\Rightarrow I'' = 74.4063s + 272.2047 + 199.762/s$

$\Rightarrow V_i = 0.2669s + 0.9764 + 0.7165/s$

$+ 2.2196/s + 1.6017/s^2 + 0.625$

$= 0.2669s + 1.6014 + 2.9361/s + 1.6017/s^2$


$\Rightarrow H(s) = 234s^2 / (s^3 + 6s^2 + 11.0007s + 6.0011)$

$$7.6 \quad (e) \quad H(s) = \frac{8s^4}{(s^2+1)(s^2+4)}$$

$$1. \quad Z_{11}(s) = \frac{(s^2+1)(s^2+4)}{s(s^2+2)} = \frac{s^4 + 5s^2 + 4}{s^3 + 2s}$$

$$\begin{aligned} & 2s + s^3 \sqrt{\frac{2/s}{4 + 5s^2 + s^4}} \\ & \frac{4 + 2s^2}{3s + s^3} \sqrt{\frac{2/s}{2 + s^2}} \\ & \frac{2 + \frac{2}{3}s^2}{\frac{1}{3}s} \sqrt{\frac{9/s}{3 + s^2}} \\ & \frac{\frac{1}{3}s}{3} \sqrt{\frac{\frac{1}{3}s}{\frac{1}{3}}} \\ & \frac{1/3}{0} \end{aligned}$$
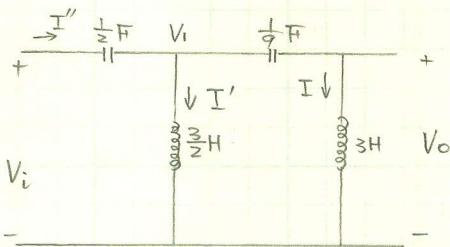
$$\begin{aligned} 2. \quad Y_{22}(s) &= \frac{(s^2+1)(s^2+4)}{s(s^2+2)} \\ &= \frac{2}{s} + \frac{1}{\frac{2}{3s} + \frac{1}{\frac{9}{s} + \frac{1}{\frac{1}{3s}}}} \end{aligned}$$



(VIA $Z_{11}(s)$)

CHECK: LET $I = 1 \text{ A}$

$$V_0 = 3s$$

$$V_1 = 3s + \frac{9}{s}$$

$$I' = 2 + \frac{6}{s^2}$$

$$I'' = 3 + \frac{6}{s^2}$$


$$V_i = \frac{6}{s} + \frac{12}{s^3} + 3s + \frac{9}{s}$$

$$= (3s^4 + 15s^2 + 12)/s^3$$

$$H(s) = V_0/V_i$$

$$= 3s^4 / (3s^4 + 15s^2 + 12)$$
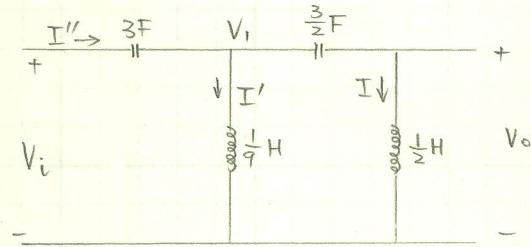
$$= s^4 / (s^2 + 1)(s^2 + 4) \quad \text{CHECKED!}$$



(VIA $Y_{22}(s)$)

CHECK: LET $I = 1 \text{ A}$

$$V_0 = \frac{1}{2}s$$

$$V_1 = \frac{1}{2}s + \frac{2}{3s}$$

$$I' = \frac{9}{2} + \frac{6}{s^2}$$

$$I'' = \frac{11}{2} + \frac{6}{s^2}$$

$$V_i = \frac{11}{6s} + \frac{2}{s^3} + \frac{1}{2}s + \frac{2}{3s}$$

$$= (s^4 + 5s^2 + 4)/2s^3$$

$$H(s) = V_0/V_i$$

$$= s^4 / (s^4 + 5s^2 + 4)$$

$$= s^4 / (s^2 + 1)(s^2 + 4) \quad \text{CHECKED!}$$

$$7.6 (g) \quad H(s) = ks^2 / [(s^2+2)(s^2+5)(s^2+6)]$$

$$1. \quad Z_{11}(s) = (s^2+2)(s^2+5)(s^2+6) / [s(s^2+4)(s^2+5.5)]$$

$$= (s^6 + 13s^4 + 52s^2 + 60) / (s^5 + 9.5s^3 + 22s)$$

$$= s + \frac{1}{0.2857s + \frac{1}{3.7692s + \frac{1}{0.07942s + \frac{1}{126.947s + \frac{1}{0.001535s}}}}}$$

$$Y'(s) = \frac{1}{126.947s + \frac{1}{0.001535s}}$$

$$= \frac{1}{\frac{1}{0.001535s} + \frac{1}{126.947s}}$$

$$2. \quad Y_{22}(s) = \frac{(s^2+2)(s^2+5)(s^2+6)}{s(s^2+4)(s^2+5.5)}$$

$$= \frac{s^6 + 13s^4 + 52s^2 + 60}{s^5 + 9.5s^3 + 22s}$$


$$= 2.7273/s + \frac{1}{0.8432/s + Z'(s)}$$

$$Z'(s) = \frac{1}{Y_{22}(s) - 2.7273/s} - 0.8432/s$$

$$= \frac{0.1568s^3 + 0.8381s}{s^4 + 10.2727s^2 + 26.0907}$$

$$Y'(s) = \frac{s^4 + 10.2727s^2 + 26.0907}{0.1568s^3 + 0.8381s}$$
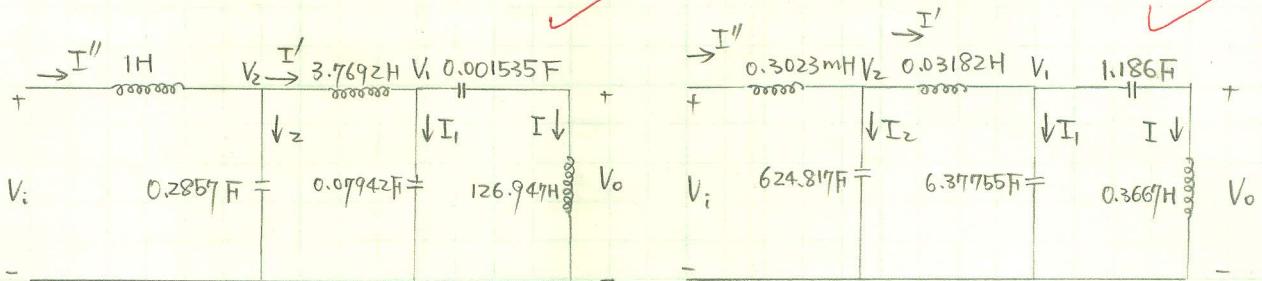
$$= 6.377755s + \frac{1}{0.03182s + \frac{1}{624.817s + \frac{1}{0.0003023s}}}$$



CHECK: $I = 1 \text{ A}$

$$V_o = 126.947 \text{ S}$$

$$V_i = 126.947 \text{ S} + 651.4658/\text{S}$$

$$I_1 = 10.0821 \text{ S}^2 + 51.7394$$

$$I' = 10.0821 \text{ S}^2 + 52.7394$$

$$V_2 = 38.0015 \text{ S}^3 + 325.7323 \text{ S} + 651.4658/\text{S}$$

$$I_2 = 10.857 \text{ S}^4 + 93.0617 \text{ S}^2 + 186.1238$$

$$I'' = 10.857 \text{ S}^4 + 103.1438 \text{ S}^2 + 238.8632$$

$$V_i = 10.857 \text{ S}^5 + 141.1453 \text{ S}^3 + 564.5955 \text{ S}$$

$$+ 651.4658/\text{S}$$

$$= (10.857 \text{ S}^6 + 141.1453 \text{ S}^4 + 564.5955 \text{ S}^2$$

$$+ 651.4658) / \text{S}$$

$$= 10.857 (s+2)(s+5)(s+6) / \text{S}$$

$$\therefore H(s) = V_o/V_i = 11.69264 \text{ S}^2 / [(s+2)(s+5)(s+6)]$$

CHECKED!

CHECK: $I = 1 \text{ A}$

$$V_o = 0.3667 \text{ S}$$

$$V_i = 0.3667 \text{ S} + 0.8432/\text{S}$$

$$I_1 = 2.3386 \text{ S}^2 + 5.378$$

$$I' = 2.3386 \text{ S}^2 + 6.378$$

$$V_2 = 0.0744 \text{ S}^3 + 0.5696 \text{ S} + 0.8432/\text{S}$$

$$I_2 = 46.4864 \text{ S}^4 + 355.8958 \text{ S}^2 + 526.846$$

$$I'' = 46.4864 \text{ S}^4 + 358.2344 \text{ S}^2 + 533.224$$

$$V_i = 0.0141 \text{ S}^5 + 0.1827 \text{ S}^3 + 0.7308 \text{ S} + 0.8432/\text{S}$$

$$= 0.0141 (s^5 + 12.9574 s^3 + 51.8298 s + 59.8014) / \text{S}$$

$$= (s+1.9976)(s+5.17)(s+5.78) / 70.92199 \text{ S}$$

$$H(s) = 26 \text{ S}^2 / (s+1.9976)(s+5.17)(s+5.78)$$

CHECKED!

Could I let the computer do check later on?


yes you can.

7.9 (c) $H(s) = \frac{-s^3 + 2s^2 - 2s + 1}{s^3 + 2s^2 + 2s + 1}$

$$= \frac{1 - \frac{s^3 + 2s}{2s^2 + 1}}{1 + \frac{s^3 + 2s}{2s^2 + 1}} \quad Z_a = \frac{s^3 + 2s}{2s^2 + 1}, \quad Z_b = 1$$

$$= \frac{\frac{2s^2 + 1}{s^3 + 2s} - 1}{\frac{2s^2 + 1}{s^3 + 2s} + 1} \quad Z_b = \frac{2s^2 + 1}{s^3 + 2s}, \quad Z_a = 1$$

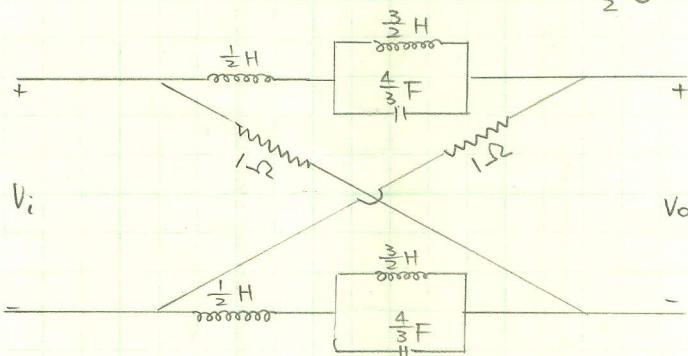
1. $Z_a = \frac{s^3 + 2s}{2s^2 + 1} = \frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{2}{3}s}}$



CHECK: $Z_a = \frac{1}{2}s + \frac{\frac{3}{2}s \cdot \frac{3}{4s}}{\frac{3}{2}s + \frac{3}{4s}} = \frac{s^3 + 2s}{2s^2 + 1}, \quad Z_b = 1$

$H(s) = \frac{Z_b - Z_a}{Z_b + Z_a} = \frac{1 - \frac{s^3 + 2s}{2s^2 + 1}}{1 + \frac{s^3 + 2s}{2s^2 + 1}} = \frac{-s^3 + 2s^2 - 2s + 1}{s^3 + 2s^2 + 2s + 1}$ CHECKED!

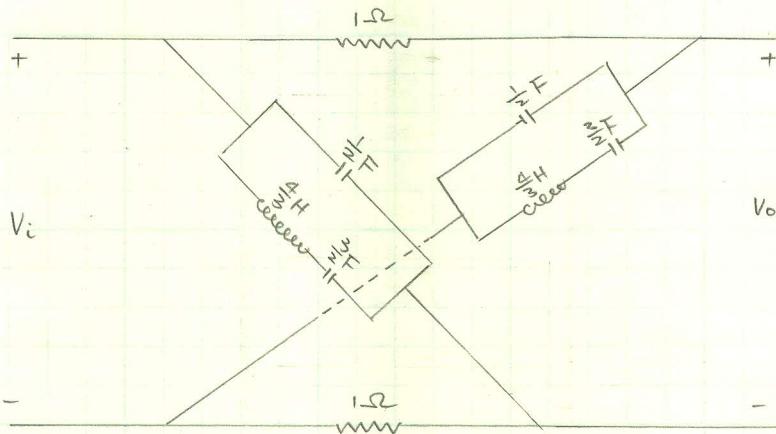2. $Z_b = \frac{2s^2 + 1}{s^3 + 2s}, \quad Y_b = \frac{s^3 + 2s}{2s^2 + 1} = \frac{1}{2}s + \frac{1}{\frac{4}{3}s + \frac{1}{\frac{2}{3}s}}$



CHECK: $Z_b = (\frac{4}{3}s + \frac{2}{3s}) \cdot \frac{2}{3} / (\frac{4}{3}s + \frac{2}{3s} + \frac{2}{3}) = (\frac{4}{3}s^2 + \frac{2}{3}) \cdot 2 / (\frac{4}{3}s^3 + \frac{2}{3}s + 2s)$
 $= (2s^2 + 1) / (s^3 + 2s), \quad Z_a = 1$

$H(s) = \frac{Z_b - Z_a}{Z_b + Z_a} = \frac{-s^3 + 2s^2 - 2s + 1}{s^3 + 2s^2 + 2s + 1}$ CHECKED!

7.10 $H(s) = p(-s)/p(s)$, $p(s)$ is a polynomial.

SHOW $\Phi_H(\omega) = 2\Phi_p(\omega) + \alpha$

PROOF: $H(s) = p(-s)/p(s)$

LET $p(s) = m(s) + n(s)$, WHERE $m(s)$ is even and $n(s)$ is odd.

$$p(-s) = m(s) - n(s)$$

$$p(j\omega) = m(\omega) + jn(\omega)$$

$$p(-j\omega) = m(\omega) - jn(\omega), \text{ WHERE } m(\omega) \text{ and } n(\omega) \text{ are real.}$$

$$H(j\omega) = p(-j\omega)/p(j\omega)$$

$$= [m(\omega) - jn(\omega)] / [m(\omega) + jn(\omega)]$$

$$= \frac{1 - j \frac{n(\omega)}{m(\omega)}}{1 + j \frac{n(\omega)}{m(\omega)}}$$

$$= \frac{(1 - j \frac{n(\omega)}{m(\omega)})(1 - j \frac{n(\omega)}{m(\omega)})}{1 + n^2(\omega)/m^2(\omega)}$$

$$\Phi_p(\omega) = -\angle p(j\omega) = -\tan^{-1} \frac{n(\omega)}{m(\omega)}$$

$$\Phi_H(\omega) = -\angle H(j\omega) = \begin{cases} 2\Phi_p(\omega) & -45^\circ < \Phi_p(\omega) < 45^\circ \\ 2\Phi_p(\omega) + 180^\circ & -90^\circ < \Phi_p(\omega) < -45^\circ \\ 2\Phi_p(\omega) - 180^\circ & 45^\circ < \Phi_p(\omega) < 90^\circ \end{cases}$$


$$\therefore \Phi_H(\omega) = 2\Phi_p(\omega) + k \cdot 180^\circ, \quad k = 0, 1, -1 \quad \checkmark$$

SORRY FOR LATE-HAND IN THIS HOMEWORK, BECAUSE I THOUGHT
IT WAS DUE THURSDAY.

OK 

20
20

Derive the transfer function:

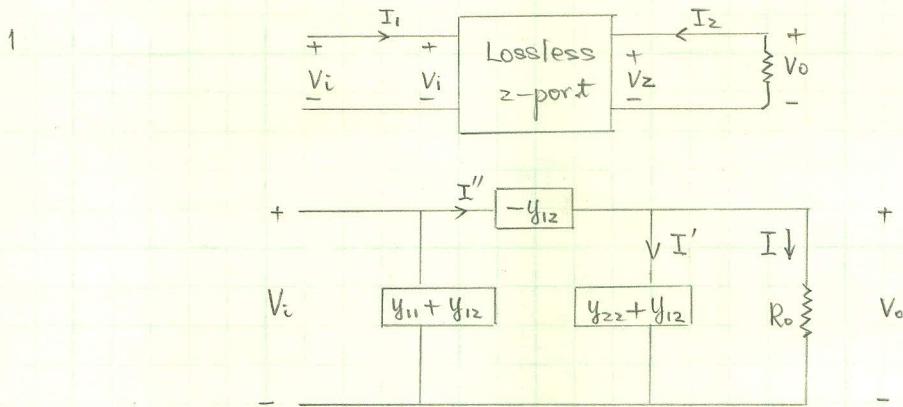

SEE THE EQUIVALENT CIRCUIT ABOVE.

LET $I = 1$, $V_o = R_o$

$$I' = (y_{22} + y_{12}) \cdot R_o$$

$$I'' = (y_{22} + y_{12}) R_o + 1$$


$$V_i = I'' / (-y_{12}) + V_o$$

$$= \frac{(y_{22} + y_{12}) \cdot R_o + 1}{-y_{12}} + R_o$$

$$= \frac{y_{22} R_o + 1}{-y_{12}}$$

$$H(s) = \frac{V_o}{V_i} = \frac{-y_{12} R_o}{y_{22} R_o + 1} = \frac{-y_{12}}{\frac{1}{R_o} + y_{22}}$$


2.

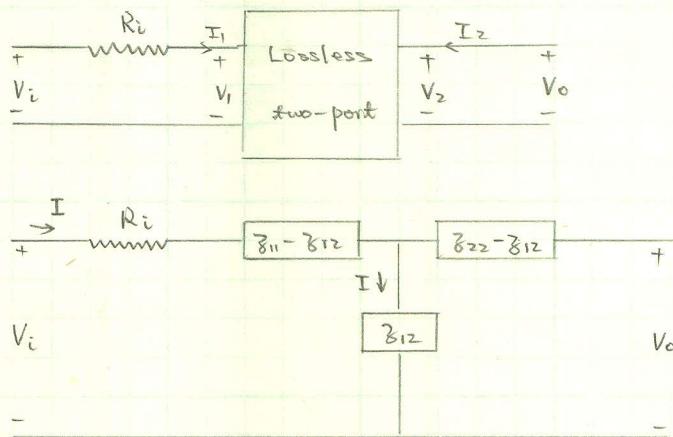

LET $I = 1A$; $V_o = z_{12}$, $V_i = R_i + z_{11}$

$$H(s) = \frac{V_o}{V_i} = \frac{z_{12}}{R_o + z_{11}}$$

3.

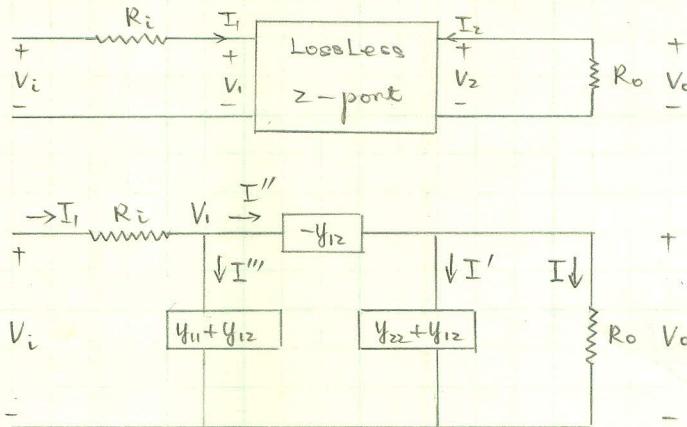

$$\text{LET } I = 1A, \quad V_o = R_o$$

$$I' = (y_{22} + y_{12}) R_o$$

$$I'' = (y_{22} + y_{12}) R_o + 1$$

$$V_i = I'' / (-y_{12}) + V_o$$

$$= (y_{22} R_o + 1) / (-y_{12})$$

$$I''' = V_i (y_{11} + y_{12})$$

$$= (y_{11} + y_{12}) (y_{22} R_o + 1) / (-y_{12})$$

$$I_1 = I'' + I''' = (y_{22} + y_{12}) R_o + 1 + (y_{11} + y_{12}) (y_{22} R_o + 1) / (-y_{12})$$

$$V_i = I_1 R_i + V_o = (y_{22} + y_{12}) R_i R_o + R_i + (y_{11} + y_{12}) (y_{22} R_o + 1) R_i / (-y_{12})$$

$$= V_i + (-y_{12} y_{22} R_i R_o - y_{12}^2 R_i R_o - y_{12} R_i + y_{11} y_{22} R_o R_i + y_{12} y_{22} R_o R_i + y_{11} R_i / R_o + y_{12} R_i) / (-y_{12})$$

$$H(s) = \frac{-y_{12}}{-y_{12} V_i / R_o + (-y_{12} y_{22} R_i - y_{12}^2 R_i - y_{12} R_i / R_o + y_{11} y_{22} R_i + y_{12} y_{22} R_o R_i + y_{11} R_i / R_o + y_{12} R_i / R_o)}$$

$$= \frac{-y_{12}}{(y_{22} + 1/R_o) - y_{12} R_i (y_{22} + 1/R_o) + y_{11} R_i (y_{22} + 1/R_o) + y_{12} R_i (y_{22} + 1/R_o) - y_{12}^2 R_i}$$

$$= \frac{-y_{12}}{(\frac{1}{R_o} + y_{22}) \cdot [y_{11} R_i - y_{12}^2 R_i / (\frac{1}{R_o} + y_{22}) + 1]}$$

$$= \frac{-y_{12}}{(\frac{1}{R_o} + y_{22})} \cdot \left[\frac{1}{R_i [y_{11} - y_{12}^2 / (\frac{1}{R_o} + y_{22})] + 1} \right]$$

60
60

Analog and Digital Filter (EE448)

Homework # 10

Nov. 9, 1986

Benmei Chen

Chapter 7: Problem 7.12 (e), 7.13 (c)


7.14 (d) 7.16 (d)

7.17 (d)

12.381 50 SHEETS 5 SQUARE
42.386 100 SHEETS 5 SQUARE
42.386 200 SHEETS 5 SQUARE
MADE IN U.S.A.



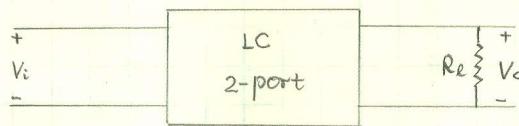7.12 Realize each of the following transfer functions by a lossless 2-port terminated at only one end by a load resistor, as shown in Fig below.



$$(e) \quad H(s) = \frac{ks}{s^3 + 6s^2 + 15s + 15}$$

$$= \frac{ks / (6s^2 + 15)}{1 + \frac{s^3 + 15s}{6s^2 + 15}}$$


$$y_{22}(s) = \frac{s^3 + 15s}{6s^2 + 15}, \quad y_{12} = -\frac{ks}{6s^2 + 15}$$

$$y_{22}(s) = \frac{s^3 + 15s}{6s^2 + 15} = \frac{1}{\frac{1}{s} + Z_R(s)}$$

$$Z_R(s) \triangleq \frac{1}{y_{22}(s)} - \frac{1}{s} = \frac{6s^2 + 15}{s^3 + 15s} - \frac{1}{s} = \frac{5s}{s^2 + 15}$$

$$Y_R(s) \triangleq \frac{1}{Z_R(s)} = \frac{s^2 + 15}{5s}$$
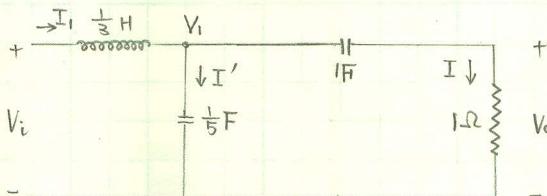
$$5s \overline{\begin{array}{r} \frac{1}{5}s \\ s^2 + 15 \\ \hline s^2 \\ 15 \end{array}} \quad \frac{1}{3}s \overline{\begin{array}{r} \frac{1}{3}s \\ 5s \\ \hline 5s \\ 0 \end{array}}$$



CHECK: LET $I = 1 \text{ A}$, $V_o = 1 \text{ A} \times 1 \Omega = 1 \text{ V}$

$$V_i = \frac{1}{s} + 1, \quad I' = V_i \cdot \frac{1}{5} s = \frac{1}{5} + \frac{1}{5} s$$


$$I_1 = I + I' = 1 + \frac{1}{5} + \frac{1}{5} s = \frac{6}{5} + \frac{1}{5} s$$

$$V_i = I_1 \cdot \frac{1}{3} s + V_o = \frac{2}{5} s + \frac{1}{15} s^2 + \frac{1}{5} + 1 = \frac{6s^2 + s^3 + 15 + 15s}{15s}$$

$$H(s) = \frac{V_o}{V_i} = \frac{15s}{s^3 + 6s^2 + 15s + 15}$$

CHECKED!

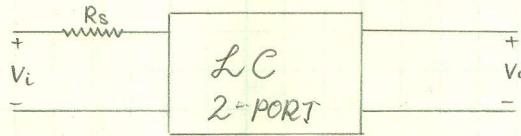7-13. Realize each of the transfer functions in Problem 9-12 by a lossless 2-port terminated at only one end by a source resistance, as shown in Fig. below.




$$(c) \quad H(s) = ks^2 / (s^2 + 4s + 4)$$

$$= \frac{ks^2 / (4s)}{1 + \frac{s^2 + 4}{4s}}$$

$$Z_{11}(s) \triangleq \frac{s^2 + 4}{4s} \quad \cdot \quad Z_{12}(s) = \frac{ks^2}{4s} = \frac{k}{4}s$$
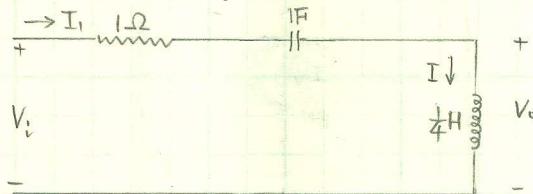
$$4s \frac{\frac{1}{s}}{\sqrt{4+s^2}} = \frac{4}{s} \frac{\frac{4}{s}}{\sqrt{\frac{4}{s^2} + 1}} = \frac{4}{s} \frac{4}{\sqrt{4+s^2}}$$



$$\text{CHECK: LET } I = 1 \text{ A, } V_o = \frac{1}{4}s$$

$$V_i = 1 + \frac{1}{s} + \frac{1}{4}s$$

$$H(s) = \frac{s/4}{(4s + 4 + s^2)/4s}$$

$$= \frac{s^2}{s^2 + 4s + 4}$$

CHECKED!

7.14 (d) Realize each of the following transfer functions by a lossless 2-port terminated at both ends with $R_s = R_e = 1\Omega$, as shown in Fig. below.

$$H(s) = ks / (s^2 + \sqrt{2}s + 1)$$

$$\begin{aligned} p(s) \cdot p(-s) &= 1 - \frac{4}{R_e} H(s)H(-s) \\ &= 1 + \frac{4k^2 s^2}{(s^2 + \sqrt{2}s + 1)(s^2 - \sqrt{2}s + 1)} \\ &= \frac{s^4 + 4k^2 s^2 + 1}{(s^2 + \sqrt{2}s + 1)(s^2 - \sqrt{2}s + 1)} \end{aligned}$$

$$\text{LET } (s^2 + as + b)(s^2 - as + b) = s^4 + 4k^2 s^2 + 1, \quad a > 0, b > 0$$

$$\therefore s^4 + (2b - a^2)s^2 + b^2 = s^4 + 4k^2 s^2 + 1$$

$$b = 1, \quad 2 - a^2 = 4k^2, \quad a = \sqrt{2 - 4k^2}$$


$$p(s) = \frac{s^2 + \sqrt{2 - 4k^2} + 1}{s^2 + \sqrt{2}s + 1}$$

$$\begin{aligned} Z_{in_1}(s) &= \frac{1 + p(s)}{1 - p(s)} = \frac{s^2 + \sqrt{2}s + 1 + s^2 + \sqrt{2 - 4k^2} + 1}{s^2 + \sqrt{2}s + 1 - s^2 - \sqrt{2 - 4k^2} - 1} \\ &= \frac{2s^2 + (\sqrt{2} + \sqrt{2 - 4k^2})s + 2}{(\sqrt{2} - \sqrt{2 - 4k^2})s} \\ &= \underbrace{\frac{2}{\sqrt{2} - \sqrt{2 - 4k^2}}}_{\text{series L}} s + \underbrace{\frac{2}{\sqrt{2} - \sqrt{2 - 4k^2}}}_{\text{series C}} \frac{1}{s} + \underbrace{\frac{\sqrt{2} + \sqrt{2 - 4k^2}}{\sqrt{2} - \sqrt{2 - 4k^2}}}_{R_e} \end{aligned}$$

$$R_e = 1 = \frac{\sqrt{2} + \sqrt{2 - 4k^2}}{\sqrt{2} - \sqrt{2 - 4k^2}}$$

$$\sqrt{2 - 4k^2} = 0, \quad k = 0.707 = \frac{\sqrt{2}}{2}$$
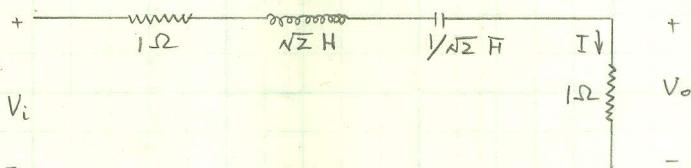
$$C = 1/\sqrt{2} \text{ F}, \quad L = \sqrt{2} \text{ H}$$



$$\text{CHECK: } I = 1 \text{ A}, \quad V_o = 1 \text{ V}$$

$$V_i = 1 + \sqrt{2}B + \sqrt{2}/s + 1 = (\sqrt{2}s^2 + 2s + \sqrt{2})/s$$

$$\therefore H(s) = \frac{1}{\sqrt{2}} s / (s^2 + \sqrt{2}s + \sqrt{2}) \quad \text{CHECKED!}$$

7.14 (d) (CONT.)


$$Z_{in}(s) = (\sqrt{2} - \sqrt{2-4k^2})s / (2s^2 + (\sqrt{2} + \sqrt{2-4k^2})s + 2)$$

$$Y_{in}(s) = (2s^2 + (\sqrt{2} + \sqrt{2-4k^2})s + 2) / (\sqrt{2} - \sqrt{2-4k^2})s$$

$$= \underbrace{\frac{2}{\sqrt{2} - \sqrt{2-4k^2}}}_{\text{SHUNT } C} s + \underbrace{\frac{2}{\sqrt{2} - \sqrt{2-4k^2}}}_{\text{SHUNT } L} \cdot \frac{1}{s} + \frac{\sqrt{2} + \sqrt{2-4k^2}}{\sqrt{2} - \sqrt{2-4k^2}}$$

$$\frac{1}{R_e} = 1$$
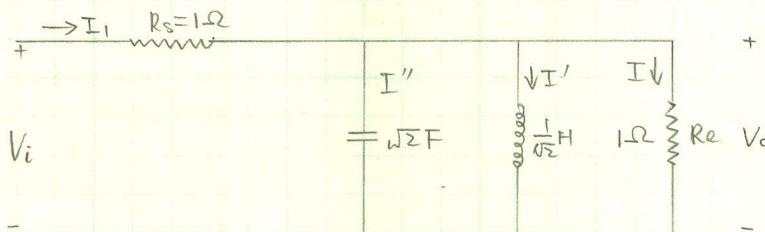
$$\therefore C = \sqrt{2} \text{ F} \quad L = \frac{1}{\sqrt{2}} \text{ H}$$



CHECK: LET $I = 1 \text{ A}$, $V_o = 1 \text{ V}$, $I' = \sqrt{2}/s$, $I'' = \sqrt{2}s$

$$I_1 = 1 + \sqrt{2}/s + \sqrt{2}s, \quad V_i = 1 + \sqrt{2}/s + \sqrt{2}s + 1 = 2 + \sqrt{2}/s + \sqrt{2}s$$

$$H(s) = \frac{1}{\sqrt{2}} s / (s^2 + \sqrt{2}s + 1) \quad \text{CHECKED!}$$

7.16 (d) Realize each of the following transfer functions with a lossless 2-port terminated at both ends by $R_s = 1$ and $R_e = 2\Omega$

$$H(s) = \frac{k s^3}{(s+1)^3} = \frac{k s^3}{s^3 + 3s^2 + 3s + 1}$$

$$\begin{aligned} p(s) \cdot p(-s) &= 1 - \frac{4}{2} \cdot H(s) \cdot H(-s) \\ &= 1 - 2 \cdot \frac{k^2 s^6}{(s^3 + 3s^2 + 3s + 1)(s^3 - 3s^2 + 3s - 1)} \\ &= \frac{(1 - 2k^2)s^6 - 3s^4 + 3s^2 - 1}{(s^3 + 3s^2 + 3s + 1)(s^3 - 3s^2 + 3s - 1)} \end{aligned}$$

FROM $H(\infty) = \frac{R_e}{R_s + R_e} = \frac{2}{3} = k$, WE HAVE

$$\begin{aligned} p(s) \cdot p(-s) &= \frac{\frac{1}{9} s^6 - 3s^4 + 3s^2 - 1}{(s^3 + 3s^2 + 3s + 1)(s^3 - 3s^2 + 3s - 1)} \\ &= \frac{1}{3} \frac{s^3 + 6.588s^2 + 8.15s + 3}{s^3 + 3s^2 + 3s + 1} \cdot \frac{1}{3} \frac{-s^3 + 6.588s^2 - 8.15s + 3}{-s^3 + 3s^2 - 3s + 1} \end{aligned}$$

$$p(s) = \frac{s^3 + 6.588s^2 + 8.15s + 3}{3s^3 + 9s^2 + 9s + 3}$$

7.16 (d) (CONT.)

$$Z_{in1} = \frac{1 - p(s)}{1 + p(s)}$$

$$= \frac{3s^3 + 9s^2 + 9s + 3 - s^3 - 6.588s^2 - 8.15s - 3}{3s^3 + 9s^2 + 9s + 3 + s^3 + 6.588s^2 + 8.15s + 3}$$


$$= \frac{2s^3 + 2.42s^2 + 0.85s}{4s^3 + 15.588s^2 + 17.15s + 6}$$

$$Z_{in2}(s) = \frac{4s^3 + 15.588s^2 + 17.15s + 6}{2s^3 + 2.42s^2 + 0.85s}$$

HENCE, $Z_{in}(\infty) = R_L = 3$, $Z_{in1}(\infty) = \frac{1}{2}$ and $Z_{in2}(\infty) = 2$ SO, WE CHOOSE $Z_m(s) = Z_{in2}(s)$

$$0.85s + 2.42s^2 + 2s^3 \begin{matrix} \frac{7.09/s}{6 + 17.15s + 15.588s^2 + 4s^3} \\ \frac{0.61/s}{6 + 17.15s + 14.18s^2} \\ \frac{0.7/s}{1.4s + 4s^2} \\ \frac{0.85 + 2.42s + 2s^2}{0.85 + 2.42s} \end{matrix} \begin{matrix} \frac{0.7/s}{1.4 + 4s} \\ \frac{1.4}{4} \\ \frac{1}{2} \\ \frac{2}{0} \end{matrix}$$

$$Z_m(s) = \frac{7.09}{s} + \frac{1}{\frac{0.61}{s} + \frac{1}{\frac{0.7}{s} + \frac{1}{\frac{1}{2}}}}$$

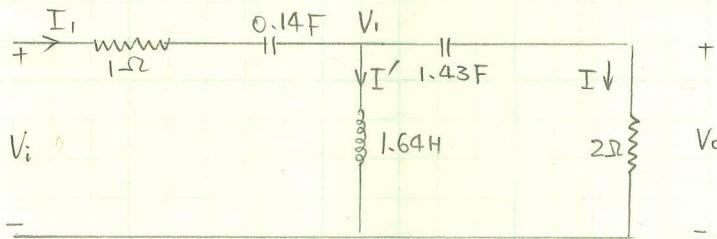CHECK: LET $I = 1A$, $V_o = 2V$,

$$V_1 = 2 + \frac{0.7}{s}, \quad I' = 1.22/s + 0.43/s^2$$

$$I' = 1 + 1.22/s + 0.43/s^2$$

$$V_2 = \left(1 + \frac{7.09}{s}\right) \left(1 + 1.22/s + 0.43/s^2\right) + 2 + 0.7/s$$

$$= 1 + 1.22/s + 0.43/s^2 + 7.09/s + 8.65/s^2 + 3.05/s^3 + 2 + 0.7/s$$

$$= 3 + 9.01/s + 9.08/s^2 + 3.05/s^3$$

$$\approx 3(s^3 + 3.00s^2 + 3.03s + 1.02) / s^3$$

$$H(s) = \frac{3s^3}{s^3 + 3.00s^2 + 3.03s + 1.02} \quad \text{close enough}$$

CHECKED!

20
/ 20

Analog and Digital Filter EE448

Homework #11

Benmei Chen

Nov. 20, 1986

12-381 50 SHEETS SQUARE
42-381 100 SHEETS SQUARE
42-386 200 SHEETS SQUARE
MADE IN U. S. A.
NATIONAL

8-3. (a) Find the minimum order of Butterworth filter to meet the following specifications:

(i) The 3dB cutoff frequency is at 1 rad/sec.

(ii) The pass-band requirement is $|H(j\omega)| \geq 0.99$ for $0 \leq \omega \leq 0.25$ rad/sec.

(iii) The stopband requirement is $|H(j\omega)| \leq 0.001$ for $\omega \geq 2$ rad/s.

(b) Find the transfer function of the desired filter.

(c) Realized the filter in (b) with $R_s = 1\Omega$ and $R_e = 1\Omega$.

(d) Realized the filter in (b) with $R_s = 1\Omega$ and $R_e = 3\Omega$.

(e) Realized the filter in (b) with $R_s = 1\Omega$ and $R_e = 0.5\Omega$.

SOLUTION: (a) $|H(j\omega)|^2 = \frac{1}{1 + \omega^{2n}}$

(i) $|H(j\omega)|^2 = 1 = 0\text{dB}$, $|H(j\cdot 1)|^2 = 0.5$, $|H(j\cdot 1)| = 0.707 = -3\text{dB}$.

(ii) $|H(j\omega)| \geq 0.99$, $|H(j\omega)|^2 \geq 0.9801$

$$\frac{1}{1 + \omega^{2n}} \geq 0.9801, \quad 1 + \omega^{2n} \leq 1.0203, \quad \omega^{2n} \leq 0.0203$$

$$\omega^{2n} \leq 0.25^{2n} \leq 0.0203, \quad n \geq 2$$

(iii) $|H(j\omega)| \leq 0.001$, $|H(j\omega)|^2 \leq 0.001^2 = 0.000001$

$$1 + \omega^{2n} \geq 10^6, \quad \omega^{2n} \geq 2^{2n} \geq 10^6 - 1, \quad n \geq 10$$

SO, 10th-order of Butterworth filter needed to meet the conditions.

(b) $n=10$ even, $\theta_k = \frac{2k-1}{20}\pi$, $k=1, 2, \dots, 10$

$$\theta_1 = \frac{\pi}{20}, \theta_2 = \frac{3\pi}{20}, \theta_3 = \frac{5\pi}{20}, \theta_4 = \frac{7\pi}{20}, \theta_5 = \frac{9\pi}{20}, \dots, \theta_{10} = \frac{19\pi}{20}$$

$$H(s) = \frac{1}{s^2 + 0.3129s + 1} \cdot \frac{1}{s^2 + 0.9080s + 1} \cdot \frac{1}{s^2 + 1.4142s + 1} \cdot \frac{1}{s^2 + 1.7820s + 1} \cdot \frac{1}{s^2 + 1.9754s + 1}$$

$$= \frac{1}{s^4 + 1.2209s^3 + 2.2841s^2 + 1.2209s + 1} \cdot \frac{1}{s^4 + 3.1962s^3 + 4.5201s^2 + 3.1962s + 1} \cdot \frac{1}{s^2 + 1.9754s + 1}$$

$$= \frac{1}{s^2 + 1.9754s + 1} \cdot \frac{1}{s^8 + 4.4171s^7 + 10.7064s^6 + 17.2361s^5 + 18.1288s^4 + 17.2361s^3 + 10.7064s^2 + 4.4171s + 1}$$

$$= \frac{1}{s^{10} + 6.3925s^9 + 20.4319s^8 + 42.8026s^7 + 62.8834s^6 + 70.2838s^5 + 62.8834s^4 + 42.8026s^3 + 20.4319s^2 + 6.3925s + 1}$$


8.3 CONT. (c) $n=10$, FROM the equation 8-46 in the text book

$$C_m = 2 \sin \left[\frac{(2m-1)\pi}{20} \right] \quad m = 1, 3, 5, 7, 9$$

$$C_1 = 0.3129 \text{ F}, \quad C_3 = 1.4142 \text{ F}, \quad C_5 = 1.9754 \text{ F}, \quad C_7 = 1.7820 \text{ F}, \quad C_9 = 0.9080 \text{ F}$$

$$L_m = 2 \sin \left[(2m-1)\pi/20 \right] \quad m = 2, 4, 6, 8, 10$$
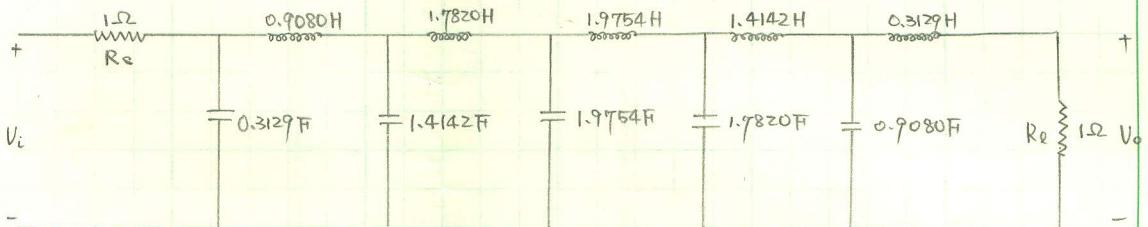
$$L_2 = 0.9080 \text{ H}, \quad L_4 = 1.7820 \text{ H}, \quad L_6 = 1.9754 \text{ H}, \quad L_8 = 1.4142 \text{ H}, \quad L_{10} = 0.3129 \text{ H}$$



(d) $R_c = 1 \Omega$ and $R_e = 3 \Omega$

$$\lambda = \left(\frac{R_e - 1}{R_e + 1} \right)^{1/n} = 0.9330$$

$$\alpha_1 = 0.3129, \quad \alpha_2 = 0.6180, \quad \alpha_3 = 0.9080, \quad \alpha_4 = 1.1756, \quad \alpha_5 = 1.4142 \dots$$

$$\beta_1 = 1.9754, \quad \beta_2 = 1.9021, \quad \beta_3 = 1.7820, \quad \beta_4 = 1.6180, \quad \beta_5 = 1.4142 \dots$$

$$\tilde{C}_1 = \frac{\alpha_1}{3(1-\lambda)} = \frac{0.3129}{3 \times 0.067} = 1.5567 \text{ F}$$

$$\tilde{L}_2 = \frac{1}{\tilde{C}_1} \cdot \frac{\alpha_1 \cdot \alpha_3}{1 - \lambda \beta_2 + \lambda^2} = 1.9045 \text{ H}$$

$$\tilde{C}_3 = \frac{1}{\tilde{L}_2} \cdot \frac{\alpha_3 \cdot \alpha_5}{1 - \lambda \beta_4 + \lambda^2} = 1.8682 \text{ F}$$

$$\tilde{L}_4 = \frac{1}{\tilde{C}_3} \cdot \frac{\alpha_5 \cdot \alpha_7}{1 - \lambda \beta_6 + \lambda^2} = 1.7435 \text{ H}$$

$$\tilde{C}_5 = \frac{1}{\tilde{L}_4} \cdot \frac{\alpha_7 \cdot \alpha_9}{1 - \lambda \beta_8 + \lambda^2} = 1.5604 \text{ F}$$


$$\tilde{L}_6 = \frac{1}{\tilde{C}_5} \cdot \frac{\alpha_9 \cdot \alpha_{11}}{1 - \lambda \beta_{10} + \lambda^2} = 1.3369 \text{ H}$$

$$\tilde{C}_7 = \frac{1}{\tilde{L}_6} \cdot \frac{\alpha_{11} \cdot \alpha_{13}}{1 - \lambda \beta_{12} + \lambda^2} = 1.0760 \text{ F}$$

$$\tilde{L}_8 = \frac{1}{\tilde{C}_7} \cdot \frac{\alpha_{13} \cdot \alpha_{15}}{1 - \lambda \beta_{14} + \lambda^2} = 0.9893 \text{ H}$$

$$\tilde{C}_9 = \frac{1}{\tilde{L}_8} \cdot \frac{\alpha_{15} \cdot \alpha_{17}}{1 - \lambda \beta_{16} + \lambda^2} = 0.4813 \text{ F}$$
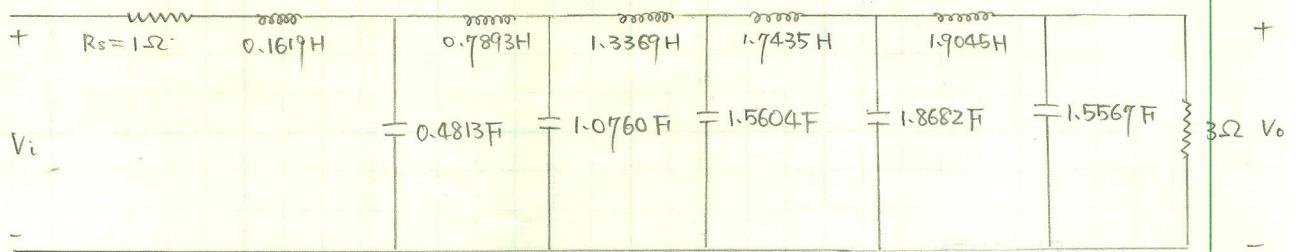
$$\tilde{L}_{10} = \frac{1}{\tilde{C}_9} \cdot \frac{\alpha_{17} \cdot \alpha_{19}}{1 - \lambda \beta_{18} + \lambda^2} = 0.1619 \text{ H}$$



(e) $R_s = 1\Omega$ and $R_L = 0.5\Omega$

$$\lambda = \left(\frac{1-0.5}{1+0.5} \right)^{1/10} = 0.8960$$

$$\hat{L}_1 = \frac{\alpha_1 R_L}{1-\lambda} = 1.5036 \text{ H}$$

$$\hat{C}_2 = \frac{1}{L_1} \cdot \frac{\alpha_1 \cdot \alpha_3}{1-\lambda\beta_2 + \lambda^2} = 1.9177 \text{ F}$$

$$\hat{L}_3 = \frac{1}{C_2} \cdot \frac{\alpha_3 \cdot \alpha_5}{1-\lambda\beta_4 + \lambda^2} = 1.8966 \text{ H}$$

$$\hat{C}_4 = \frac{1}{L_3} \cdot \frac{\alpha_5 \cdot \alpha_7}{1-\lambda\beta_6 + \lambda^2} = 1.7729 \text{ F}$$

$$\hat{L}_5 = \frac{1}{C_4} \cdot \frac{\alpha_7 \cdot \alpha_9}{1-\lambda\beta_8 + \lambda^2} = 1.5896 \text{ H}$$


$$\hat{C}_6 = \frac{1}{L_5} \cdot \frac{\alpha_9 \cdot \alpha_{11}}{1-\lambda\beta_{10} + \lambda^2} = 1.3616 \text{ F}$$

$$\hat{L}_7 = \frac{1}{C_6} \cdot \frac{\alpha_{11} \cdot \alpha_{13}}{1-\lambda\beta_{12} + \lambda^2} = 1.0971 \text{ H}$$

$$\hat{C}_8 = \frac{1}{L_7} \cdot \frac{\alpha_{13} \cdot \alpha_{15}}{1-\lambda\beta_{14} + \lambda^2} = 0.8043 \text{ F}$$

$$\hat{L}_9 = \frac{1}{C_8} \cdot \frac{\alpha_{15} \cdot \alpha_{17}}{1-\lambda\beta_{16} + \lambda^2} = 0.4908 \text{ H}$$
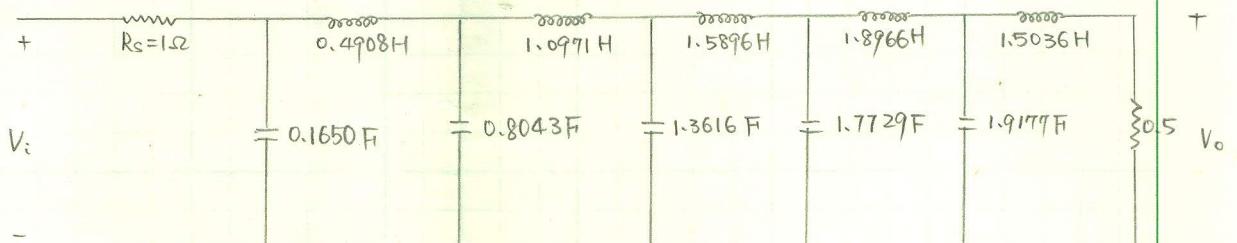
$$\hat{C}_{10} = \frac{1}{L_9} \cdot \frac{\alpha_{17} \cdot \alpha_{19}}{1-\lambda\beta_{18} + \lambda^2} = 0.1650 \text{ F}$$



~~100~~
100

EE 448 FILTER DESIGN

HOMEWORK # "FORGOT"

Butterworth and Chebyshev Lowpass

Dec. 3 , 1986 Wednesday

Benmei Chen

42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-383 200 SHEETS 5 SQUARE
MADE IN U.S.A.
NATIONAL

Ben mei Chen.

E-E 448 FILTER DESIGN
R. A. Birgenheier
November 20, 1986

FIRST THUR. NEXT WEEK

Homework


Design a normalized Butterworth LPF of minimum order to meet the following specs.

<u>Filter</u>	<u>Passband Attenuation</u>	<u>Stopband Attenuation</u>	<u>Output Load</u>
A	<.5dB for $\omega < .8$ rps	>40dB for $\omega > 2$ rps	.25 Ω
B	<.8dB for $\omega < .85$ rps	>30dB for $\omega > 1.6$ rps	0.5 Ω
C	<.1dB for $\omega < .75$ rps	>20dB for $\omega > 1.25$ rps	0.5 Ω
D	<.4dB for $\omega < .85$ rps	>30dB for $\omega > 1.4$ rps	2 Ω
E	<.1dB for $\omega < .75$ rps	>30dB for $\omega > 1.5$ rps	2 Ω


- Determine and plot pole locations.
- Determine $H(s)$
- Obtain a Realization (schematic)
- Determine the frequency response from a SPICE run for (i) 8 significant figures and (ii) 3 significant figures for component values.

(A)	(B)	(C)	(D)	(E)
G.A.	R.H.	F.H.	K.P.	H.R.
L.A.	A.H.	T.M.	T.R.	T.W.
C.C.	B.K.	S.N.	M.R.	D.Y.
B.C.	B.M.	M.P.		


a) Determine and plot pole locations.

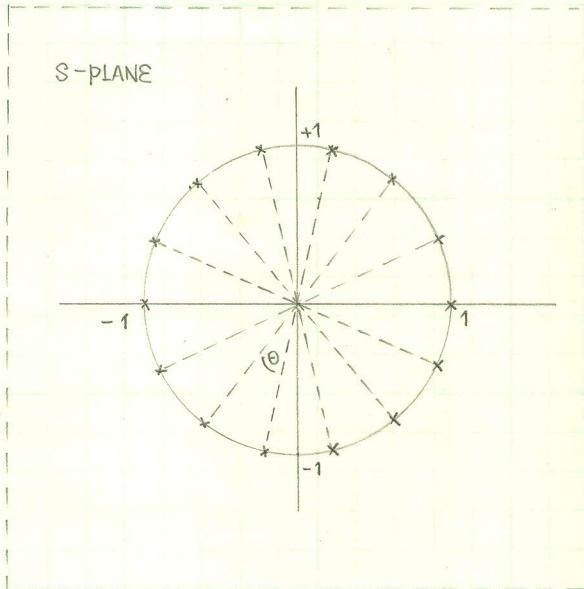


FILTER A , $n=7$, $\theta=25.7^\circ$

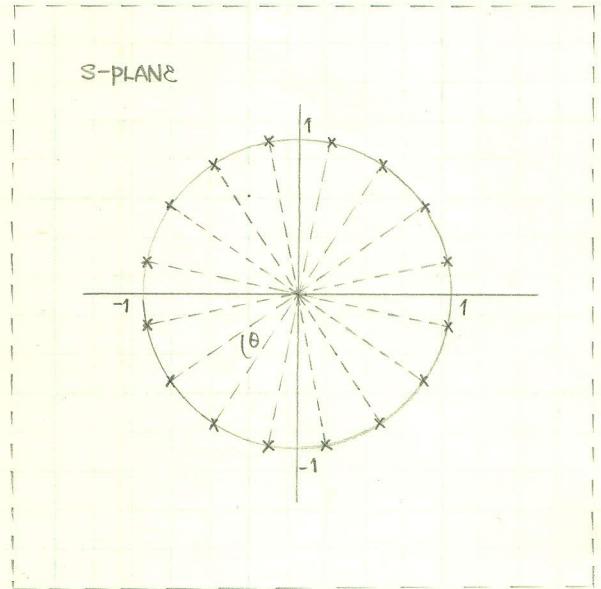

FILTER B , $n=8$, $\theta=22.5^\circ$

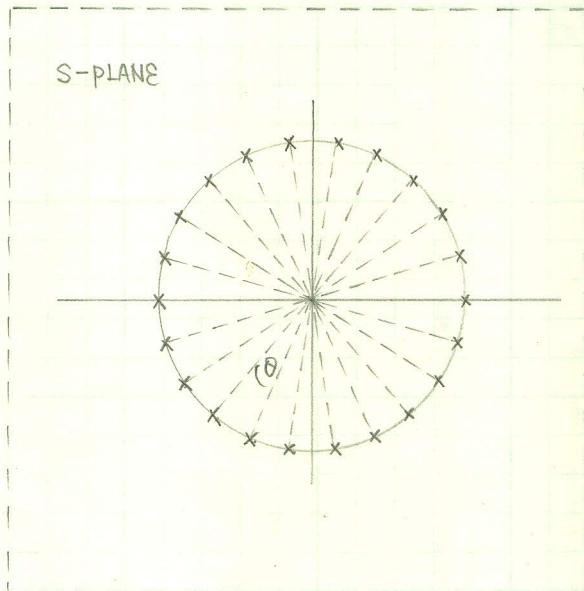

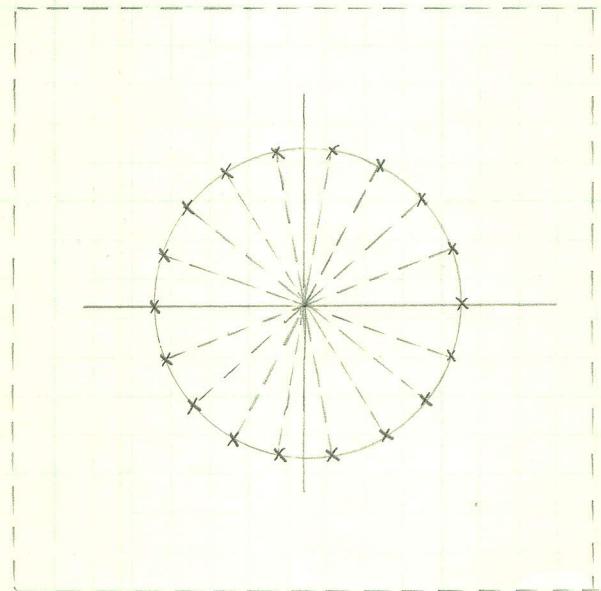FILTER C AND D , $n=11$, $\theta=16.36^\circ$



FILTER E , $n=9$, $\theta=20^\circ$

43,381 50 SHEETS 5 SQUARE
42,388 100 SHEETS 5 SQUARE
42,389 200 SHEETS 5 SQUARE
MADE IN U.S.A.
NATIONAL

(b) Determine H(s). (WE CAN FIND H(S) IN TABLE A8-1 ON PAGE 301 WITH $n \leq 9$)

FILTER A :

$$H(s) = \frac{1}{s^7 + 4.49396s^6 + 10.09783s^5 + 14.59179s^4 + 14.59179s^3 + 10.09783s^2 + 4.49396s + 1}$$

$$= \frac{1}{(s^2 + 0.44504s + 1)(s^2 + 1.24698s + 1)(s^2 + 1.80194s + 1)(s + 1)}$$

FILTER B :

$$H(s) = \frac{1}{s^8 + 5.1258s^7 + 13.1371s^6 + 21.8462s^5 + 25.6884s^4 + 21.8462s^3 + 13.1371s^2 + 5.1258s + 1}$$

$$= \frac{1}{(s^2 + 0.39023s + 1)(s^2 + 1.1111s + 1)(s^2 + 1.6629s + 1)(s^2 + 1.9616s + 1)}$$

FILTER C :

AND D :

$$H(s) = \frac{1}{(s + 1)(s^2 + 0.2846s + 1)(s^2 + 0.8308s + 1)(s^2 + 1.3097s + 1)(s^2 + 1.6825s + 1)(s^2 + 1.9190s + 1)}$$


FILTER E :

$$H(s) = \frac{1}{(s^2 + 0.3473s + 1)(s^2 + s + 1)(s^2 + 1.5321s + 1)(s^2 + 1.8794s + 1)(s + 1)}$$

(c) Obtain a Realization (schematic):


FILTER A :

$R_e = 0.25\Omega$
 $n = 7$

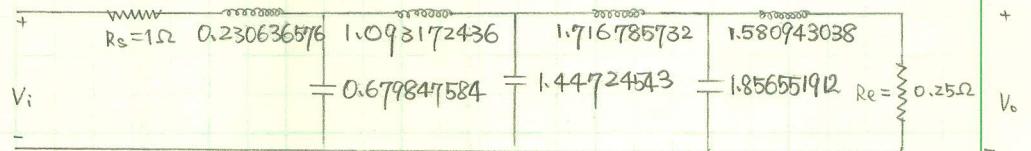


FILTER B :

$R_e = 0.5\Omega$
 $n = 8$

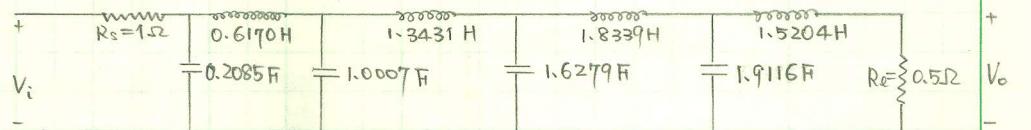


FILTER C :

$R_e = 0.5\Omega$
 $n = 11$

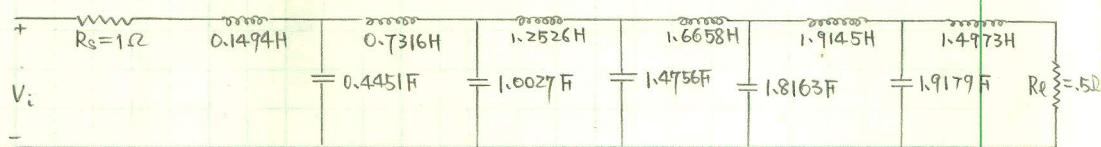


FILTER D :

$R_e = 2\Omega$
 $n = 11$

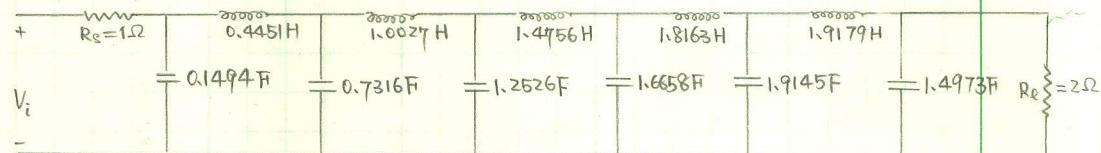

FILTER E :

$R_e = 2\Omega$
 $n = 9$

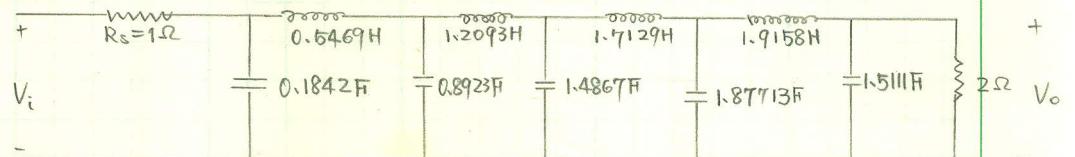


14-381 50 SHEETS SQUARE
 42-386 100 SHEETS SQUARE
 42-388 200 SHEETS SQUARE
 NATIONAL
 MADE IN U.S.A.

BUTTERWORTH LOWPASS FILTER --- 7TH-ORDER

Date/Time run: 12/ 3/86 22:00:29

Temperature: 27.0

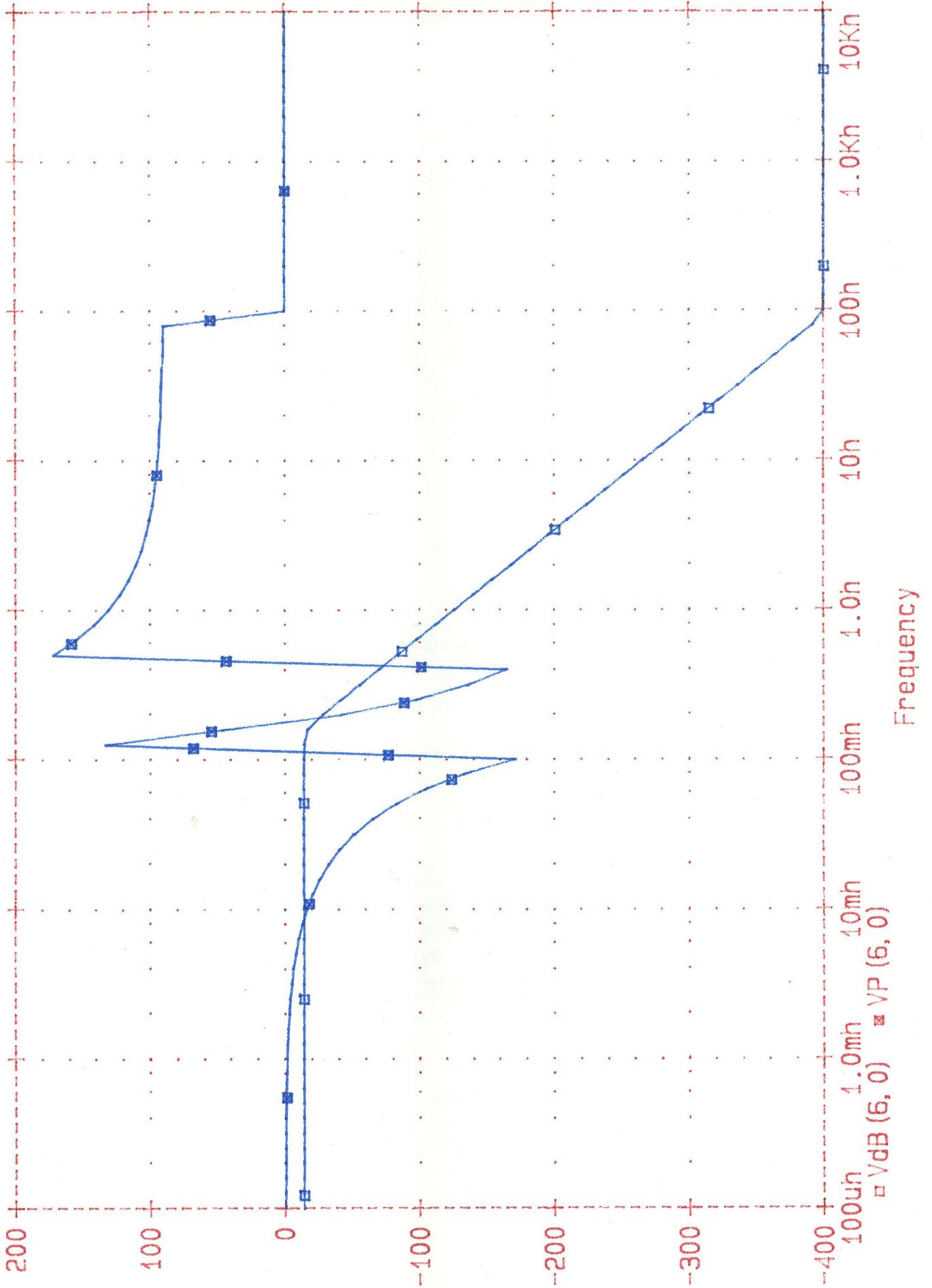

E-E 448 PASSIVE AND ACTIVE FILTER DESIGN

Homework

November 25, 1986

Design a normalized L-P chebyshev filter that satisfies the following specifications:

<u>Filter</u>	<u>Max. Passband Ripple</u>	<u>Stopband Attenuation</u>	<u>Load Resistance</u>
A	.15 dB	>40 dB for $\omega > 1.5$ rps	(a) $.5\Omega$ (b) 1.5Ω
B	.25 dB	>50 dB for $\omega > 1.8$ rps	(a) $.75\Omega$ (b) 1.2Ω
C	.4 dB	>80 dB for $\omega > 2.0$ rps	(a) $.25\Omega$ (b) 1.25Ω
D	1.2 dB	>80 dB for $\omega > 1.8$ rps	(a) $.75\Omega$ (b) 2.0Ω
E	0.8 dB	>40 dB for $\omega > 1.3$ rps	(a) $.5\Omega$ (b) 1.2Ω

- Determine and plot pole locations.
- Determine the transfer function (you may leave it in factored form).
- Use SPICE to determine the frequency response, and thereby verify the specifications.

<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>	<u>E</u>
G.A.	R.H.	F.H.	K.P.	T.W.
L.A.	A.H.	T.M.	M.R.	D.Y.
C.C.	B.K.	S.J.	H.R.	M.P.
B.C.	B.M.	T.R.		

SOLUTION: A normalized L-P Chebyshev Filter:

$$|H(j\omega)|^2 = \frac{1}{1 + \epsilon^2 T_n^2(\omega)}$$

$$\text{WHERE } T_n(\omega) = \begin{cases} \cos(n \cos^{-1} \omega) & |\omega| \leq 1 \\ \cosh(n \cosh^{-1} \omega) & |\omega| \geq 1 \end{cases}$$

$$|H(j\omega)|_{dB} = -10 \log(1 + \epsilon^2 T_n^2(\omega))$$

FOR FILTER A:

$$\epsilon = \sqrt{10^{0.015} - 1} = 0.1875$$

$$10 \log(1 + 0.1875^2 T_n^2(1.5)) > 40 \Rightarrow T_n(1.5) > 533.3067 \Rightarrow n \geq 8$$

FOR FILTER B:

$$\epsilon = \sqrt{10^{0.025} - 1} = 0.2434$$

$$10 \log[1 + 0.2434^2 T_n^2(1.8)] > 50 \Rightarrow T_n(1.8) > 1299.2037 \Rightarrow n \geq 7$$

FOR FILTER C:

$$\epsilon = \sqrt{10^{0.04} - 1} = 0.3106$$

$$10 \log[1 + 0.3106^2 T_n^2(2.0)] > 80 \Rightarrow T_n(2) > 31645.5695 \Rightarrow n \geq 9$$

FOR FILTER D:

$$\epsilon = \sqrt{10^{0.12} - 1} = 0.5641$$

$$10 \log[1 + 0.3183 T_n^2(1.8)] > 80 \Rightarrow T_n(1.8) > 17724.8137 \Rightarrow n \geq 9$$

FOR FILTER E:


$$\epsilon = \sqrt{10^{0.08} - 1} = 0.4497$$

$$10 \log[1 + 0.2023 T_n^2(1.3)] > 40 \Rightarrow T_n(1.3) > 222.3209 \Rightarrow n \geq 9$$

FILTER	A	B	C	D	E
ORDER	8	7	9	9	9
ϵ	0.1875	0.2434	0.3106	0.5641	0.4497


(a) DETERMINE AND PLOT POLE LOCATIONS:

S-PLANE

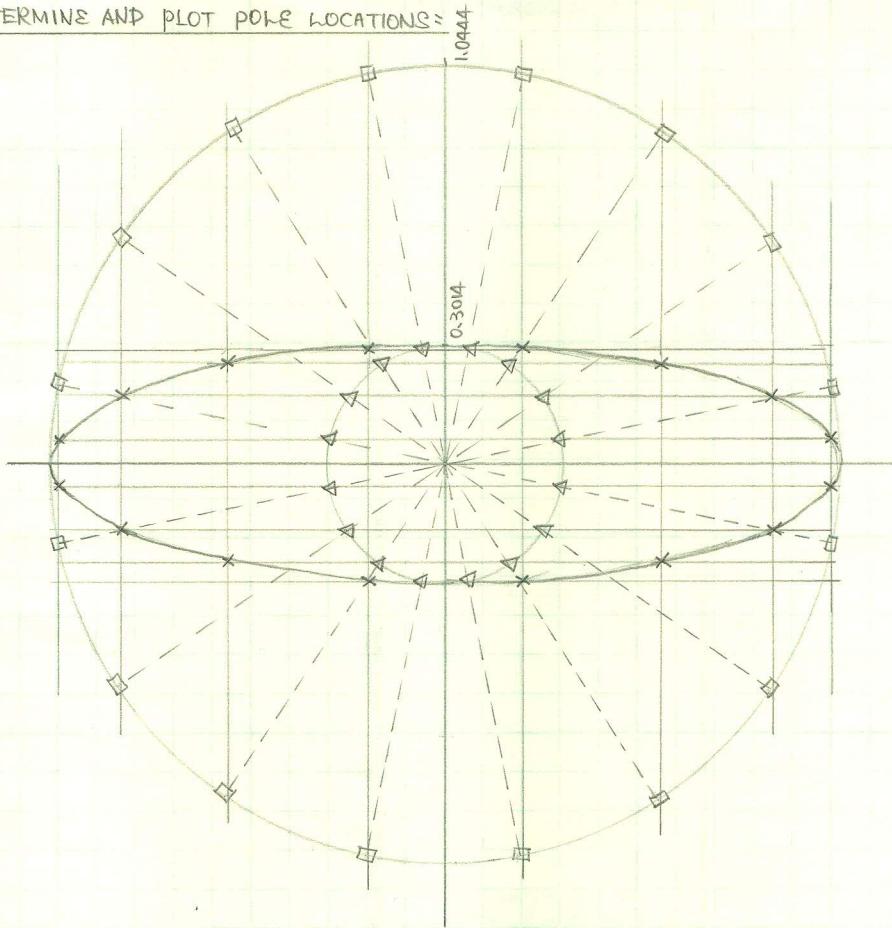


FILTER A, $n=8$, $\theta=22.5^\circ$, $a=0.3014$ $b=1.0444$


S-PLANE

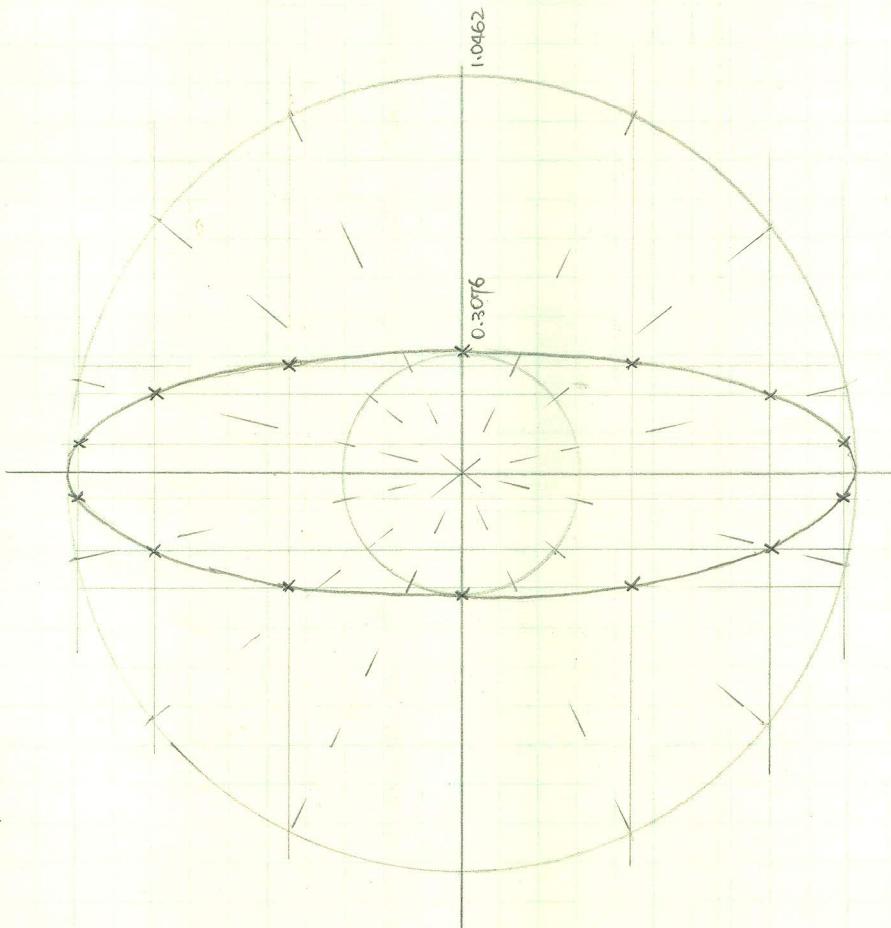

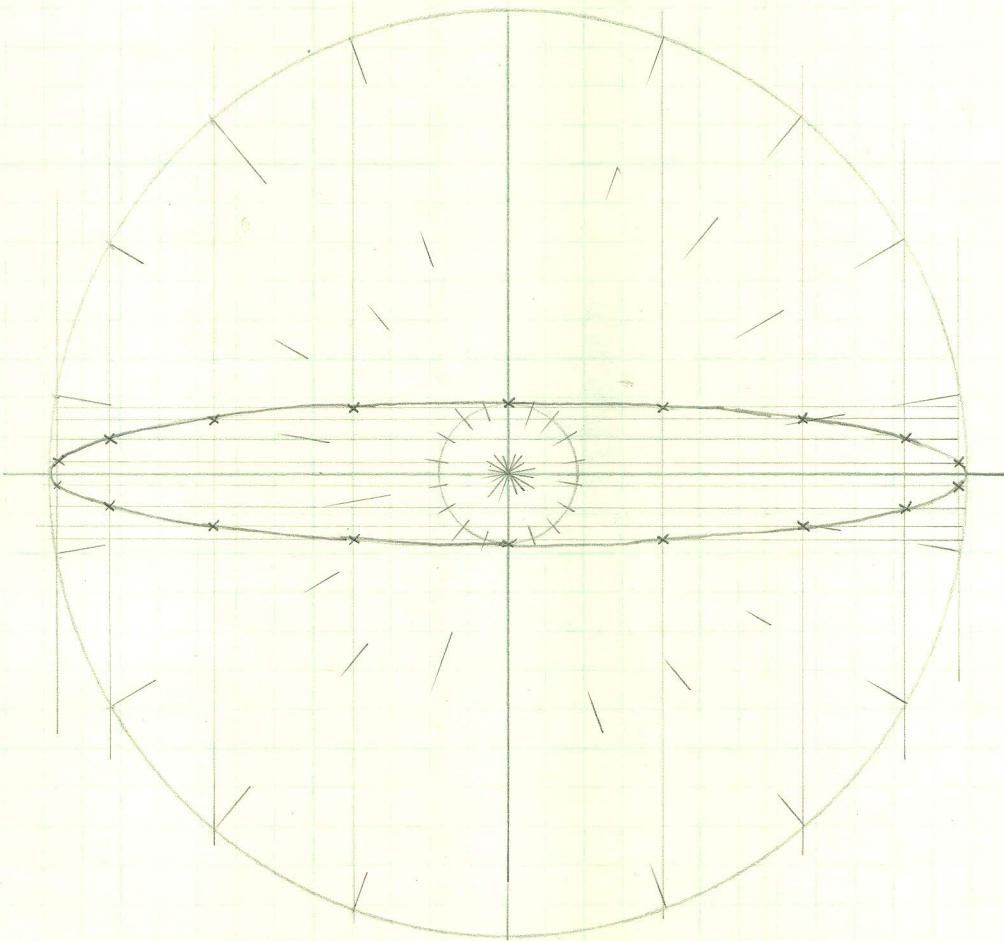FILTER B, $n=7$, $\theta=25.71^\circ$, $a=0.3076$, $b=1.0462$




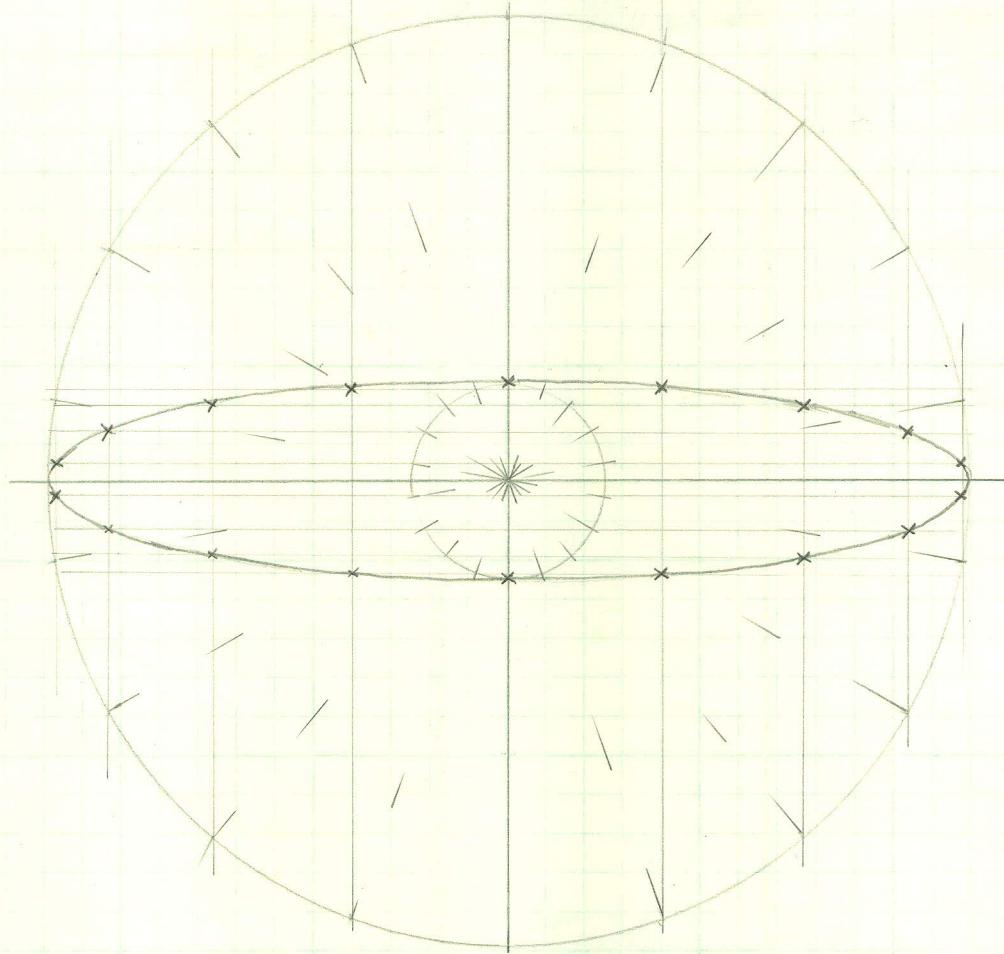FILTER D : $n=9, \theta=20^\circ$ $a=0.1491, b=1.0111$



FILTER C : $n=9, \theta=20^\circ, a=0.2111, b=1.0220$

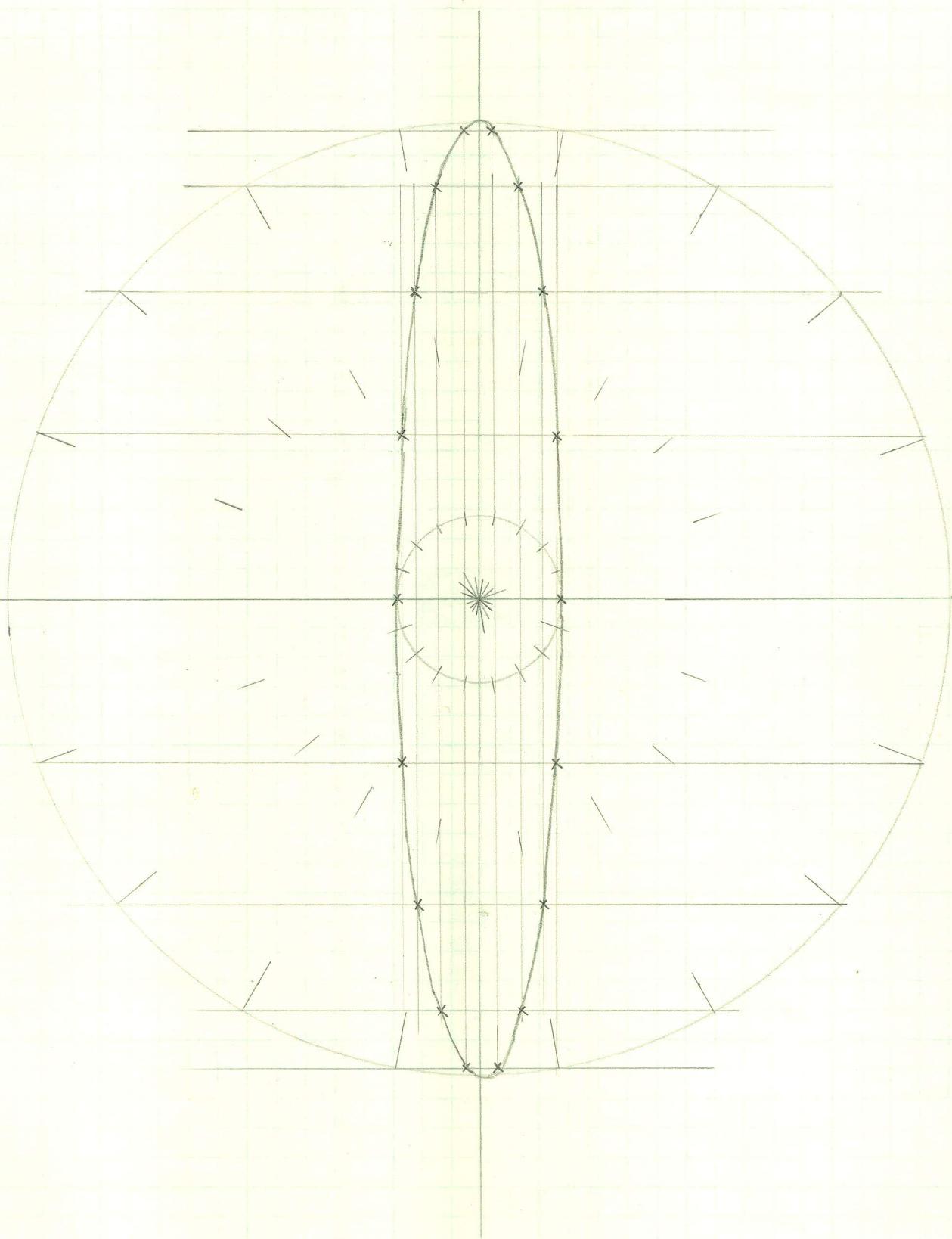42-381 50 SHEETS 5 SQUARE
42-382 100 SHEETS 5 SQUARE
42-383 200 SHEETS 5 SQUARE
MADE IN U.S.A.
NATIONAL



FILTER E: $n=9$, $\theta=20^\circ$, $a=0.1719$, $b=1.0307$

(b)

FILTER A: $\epsilon = 0.1875$, $n = 8$

$$\sigma_k = -\sinh\left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon}\right] \sin \frac{2k-1}{2n} \pi = -0.3014 \cdot \sin[(2k-1) \times 11.25^\circ]$$

$$\omega_k = \cosh\left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon}\right] \cos \frac{2k-1}{2n} \pi = 1.0444 \cdot \cos[(2k-1) \times 11.25^\circ]$$

k	1	2	3	4	5	6	7	8
σ_k	-0.0588	-0.1674	-0.2506	-0.2956	-0.2956	-0.2506	-0.1674	-0.0588
ω_k	1.0243	0.8684	0.5802	0.2038	-0.2038	-0.5802	-0.8684	-1.0243

$$H(s) = \frac{1}{(s+0.0588-j1.0243)(s+0.0588+j1.0243)(s+0.1674-j0.8684)(s+0.1674+j0.8684)}$$

$$\cdot \frac{1}{(s+0.2506-j0.5802)(s+0.2506+j0.5802)(s+0.2956-j0.2038)(s+0.2956+j0.2038)}$$

$$= \frac{1}{(s^2+0.1176s+1.0526)(s^2+0.3348s+0.7821)(s^2+0.5012s+0.3994)(s^2+0.5912s+0.1289)}$$

FILTER B: $\epsilon = 0.2434$, $n = 7$

$$\sigma_k = -\sinh\left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon}\right] \sin \frac{2k-1}{2n} \pi = -0.3076 \cdot \sin[(2k-1) \times 12.85^\circ]$$

$$\omega_k = \cosh\left[\frac{1}{n} \sinh^{-1} \frac{1}{\epsilon}\right] \cos \frac{2k-1}{2n} \pi = 1.0462 \cdot \cos[(2k-1) \times 12.85^\circ]$$

k	1	2	3	4	5	6	7
σ_k	-0.0684	-0.1917	-0.2771	-0.3076	-0.2771	-0.1917	-0.0684
ω_k	1.0200	0.8182	0.4545	0	-0.4545	-0.8182	-1.0200

$$H(s) = \frac{1}{(s+0.0684-j1.0200)(s+0.0684+j1.0200)(s+0.1917-j0.8182)}$$

$$\cdot \frac{1}{(s+0.1917+j0.8182)(s+0.3076)(s+0.2771-j0.4545)(s+0.2771+j0.4545)}$$

$$= \frac{1}{(s^2+0.1368s+1.0451)(s^2+0.3834s+0.7062)(s^2+0.5542s+0.2834)(s+0.3076)}$$

FILTER C:

$$\epsilon = 0.3106, \quad n = 9$$

$$\sigma_k = -\sinh\left[\frac{1}{n} \sinh^{-1}\frac{1}{\epsilon}\right] \sin\frac{2k-1}{2n}\pi = -0.2111 \sin[(2k-1) \times 10^\circ]$$

$$\omega_k = \cosh\left[\frac{1}{n} \sinh^{-1}\frac{1}{\epsilon}\right] \cos\frac{2k-1}{2n}\pi = 1.0220 \cos[(2k-1) \times 10^\circ]$$

k	1	2	3	4	5	6	7	8	9
σ_k	-0.0367	-0.1056	-0.1617	-0.1984	-0.2111	-0.1984	-0.1617	-0.1056	-0.0367
ω_k	1.0065	0.8851	0.6569	0.3495	0	-0.3495	-0.6569	-0.8851	-1.0065

$$H(s) = \frac{1}{(s+0.0367-j1.0065)(s+0.0367+j1.0065)(s+0.1056-j0.8851)(s+0.1056+j0.8851)(s+0.2111)}$$

$$\times \frac{1}{(s+0.1617-j0.6569)(s+0.1617+j0.6569)(s+0.1984-j0.3495)(s+0.1984+j0.3495)}$$

$$= \frac{1}{(s^2+0.0734s+1.0144)(s^2+0.2112s+0.7746)(s^2+0.3234s+0.4577)(s^2+0.3968s+0.1615)(s+0.2111)}$$

FILTER D:

$$\epsilon = 0.5641, \quad n = 9$$

$$\sigma_k = -0.1491 \sin[(2k-1) \times 10^\circ]$$

$$\omega_k = 1.0111 \cos[(2k-1) \times 10^\circ]$$

k	1	2	3	4	5	6	7	8	9
σ_k	-0.0259	-0.0746	-0.1142	-0.1401	-0.1491	-0.1401	-0.1142	-0.0746	-0.0259
ω_k	0.9957	0.8756	0.6499	0.3458	0	-0.3458	-0.6499	-0.8756	-0.9957

$$H(s) = \frac{1}{(s+0.0259-j0.9957)(s+0.0259+j0.9957)(s+0.0746-j0.8756)(s+0.0746+j0.8756)(s+0.1491)}$$

$$\times \frac{1}{(s+0.1142-j0.6499)(s+0.1142+j0.6499)(s+0.1401-j0.3458)(s+0.1401+j0.3458)}$$

$$= \frac{1}{(s^2+0.0518s+0.9921)(s^2+0.1492s+0.7722)(s^2+0.2284s+0.4354)(s^2+0.2802s+0.1392)(s+0.1491)}$$

FILTER E: $\epsilon = 0.4497$, $n = 9$

$$\sigma_k = -0.1719 \sin[(2k-1) \times 10^\circ]$$

$$\omega_k = 1.0307 \cos[(2k-1) \times 10^\circ]$$

K	1	2	3	4	5	6	7	8	9
	-0.0299	-0.0860	-0.1317	-0.1615	-0.1719	-0.1615	-0.1317	-0.0860	-0.0299
	1.0150	0.8926	0.6625	0.3525	0	-0.3525	-0.6625	-0.8926	-1.0150

$$H(s) = \frac{1}{(s+0.0299-j1.0150)(s+0.0299+j1.0150)(s+0.0860-j0.8926)(s+0.0860+j0.8926)(s+0.1719)}$$


$$\times \frac{1}{(s+0.1317-j0.6625)(s+0.1317+j0.6625)(s+0.1615-j0.3525)(s+0.1615+j0.3525)}$$

$$= \frac{1}{(s^2+0.0598s+1.0311)(s^2+0.1720s+0.8041)(s^2+0.2634s+0.4563)(s^2+0.3230s+0.1503)(s+0.1719)}$$


** Circuit Realization =

FILTER A =

$R_l = 0.5 \Omega$ (a)

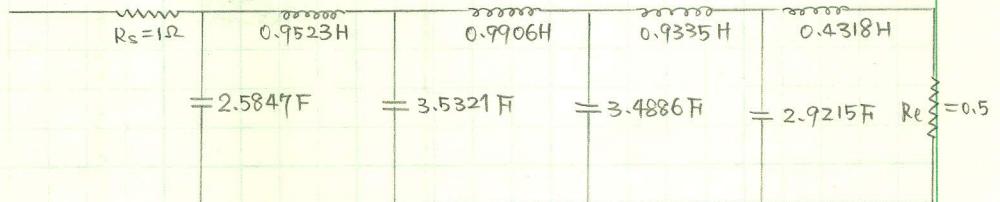


$R_l = 1.5 \Omega$ (b)

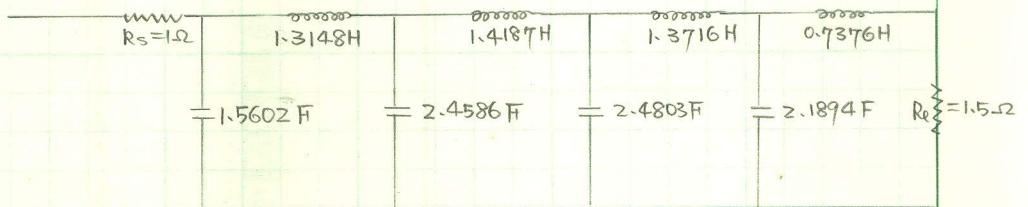


FILTER B = (a)

$R_l = 0.75 \Omega$

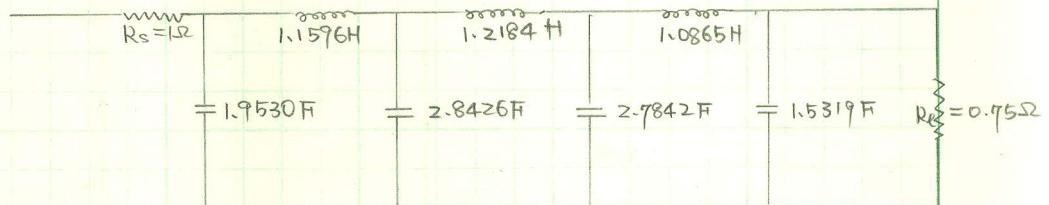


FILTER B: (b)

$R_e = 1.2 \Omega$

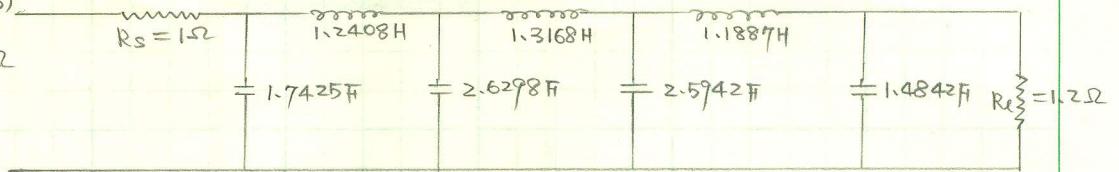


FILTER C:

(a) $R_e = 0.25 \Omega$

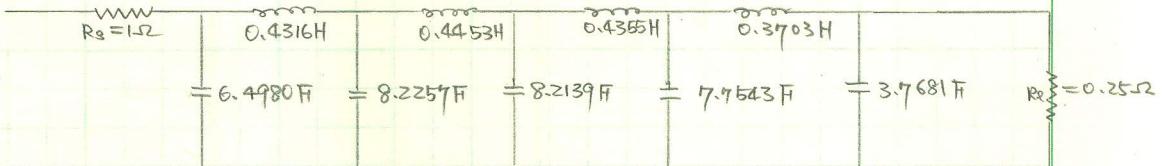


(b) $R_e = 1.25 \Omega$

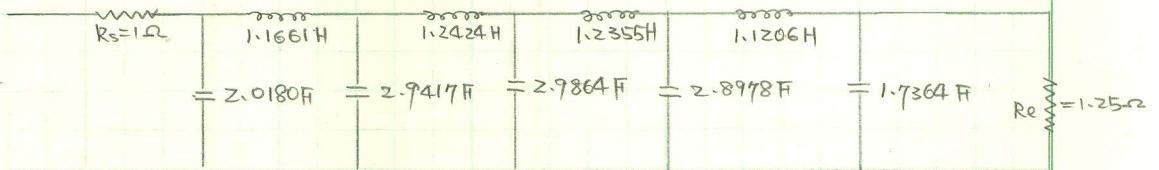


FILTER D:

(a) $R_e = 0.75 \Omega$

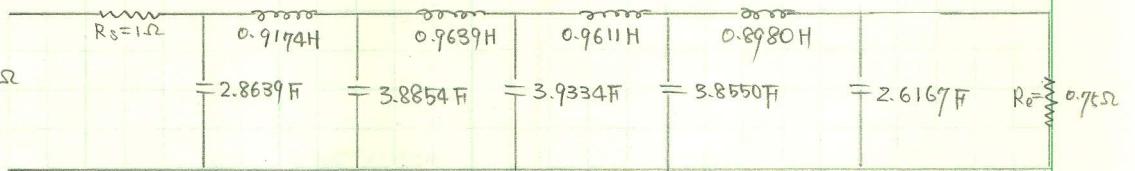


(b) $R_e = 2.0 \Omega$

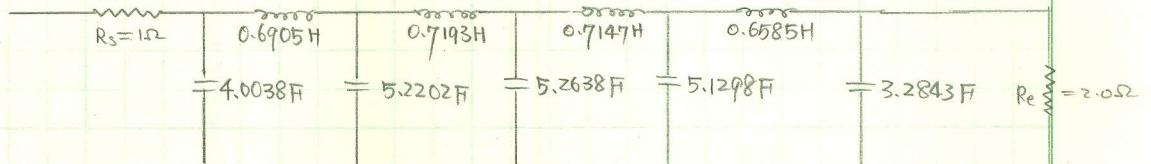


FILTER E:

(a) $R_e = 0.5 \Omega$

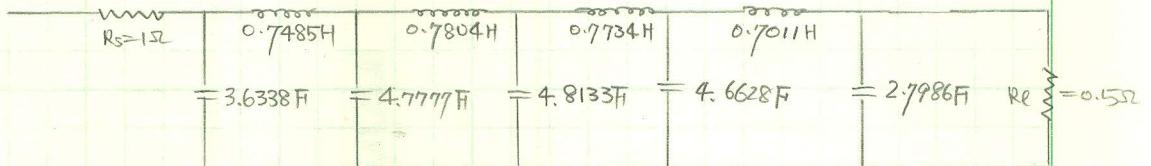

(b) $R_e = 1.2 \Omega$

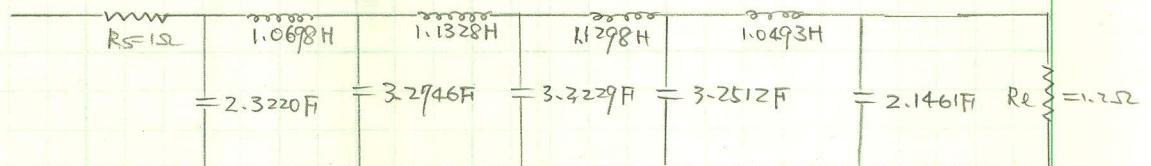


CHEBYSHEV 8TH-ORDER LOWPASS FILTER


$R_0 = 0.5$

Temperature: 27.0

Date/Time run: 1/ 1/80 0: 32: 22

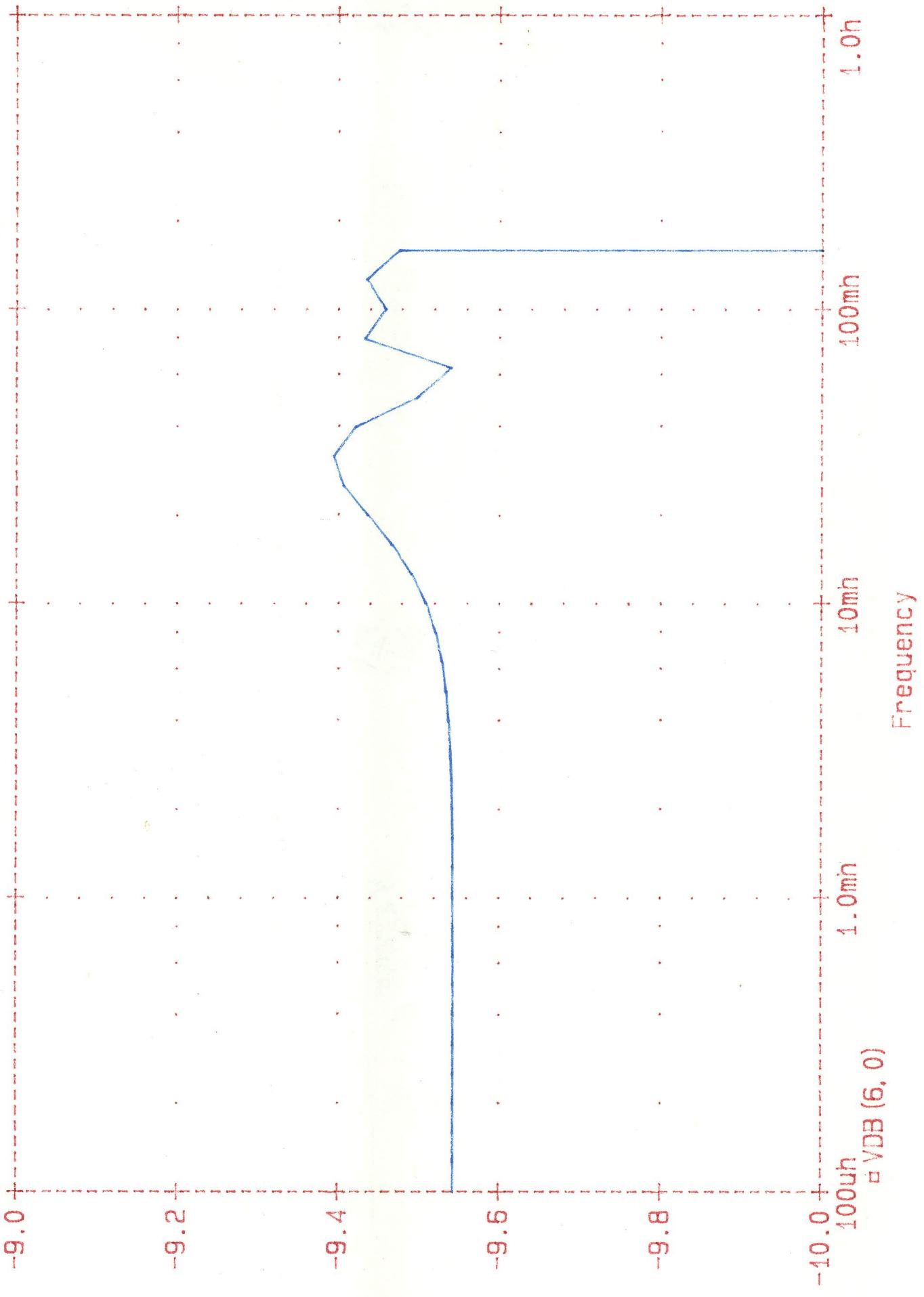

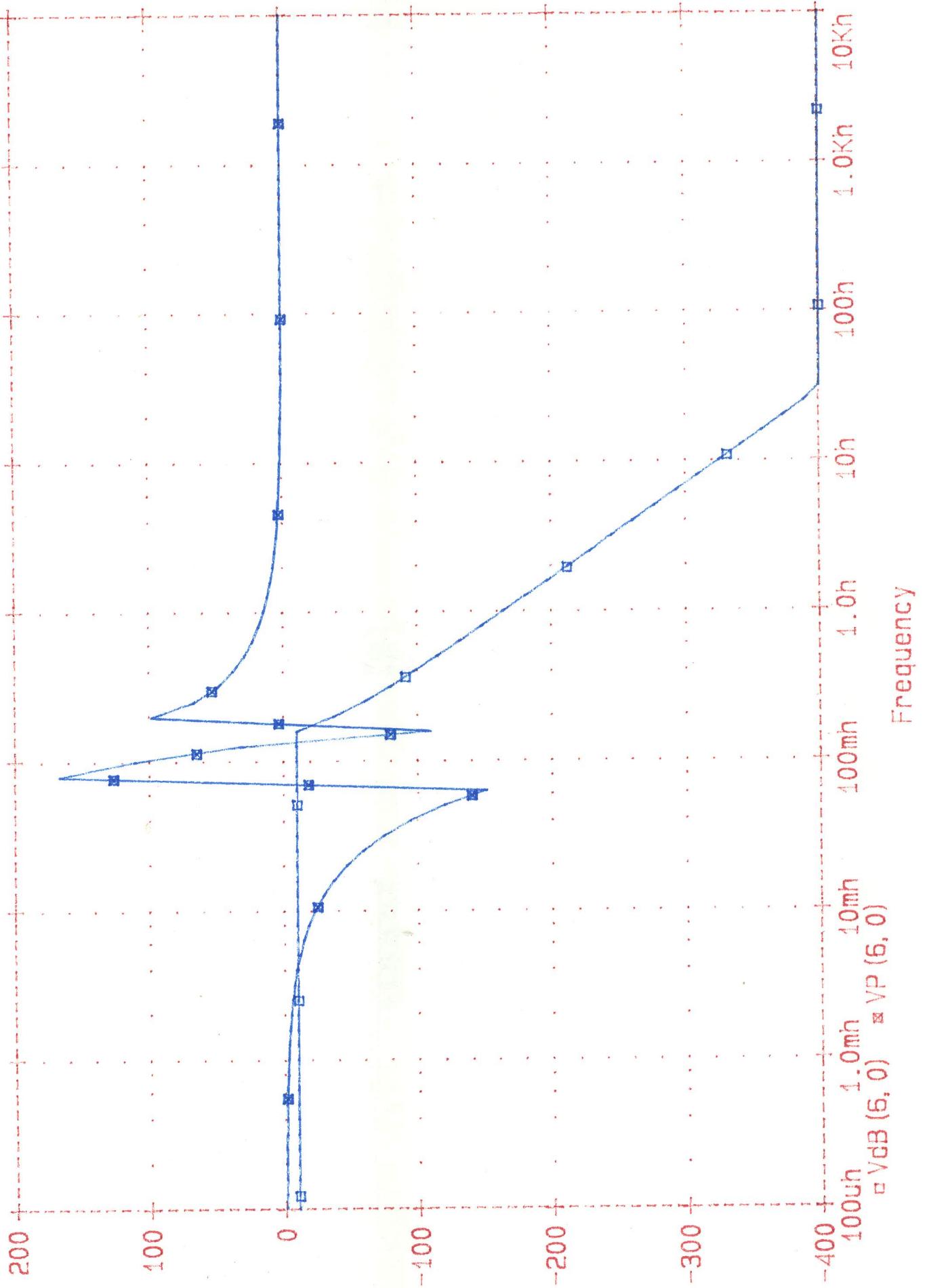
Date/Time run: 1/ 1/80 0: 32: 22
 CHEBYSHEV 8TH-ORDER LOWPASS FILTER $R_0 = 0.15$ Temperature: 27.0



CHEBYSHEV LOWPASS FILTER -- 8TH-ORDER Ro=1.5

Date/Time run: 12/ 3/86 22: 13: 36


Temperature: 27.0

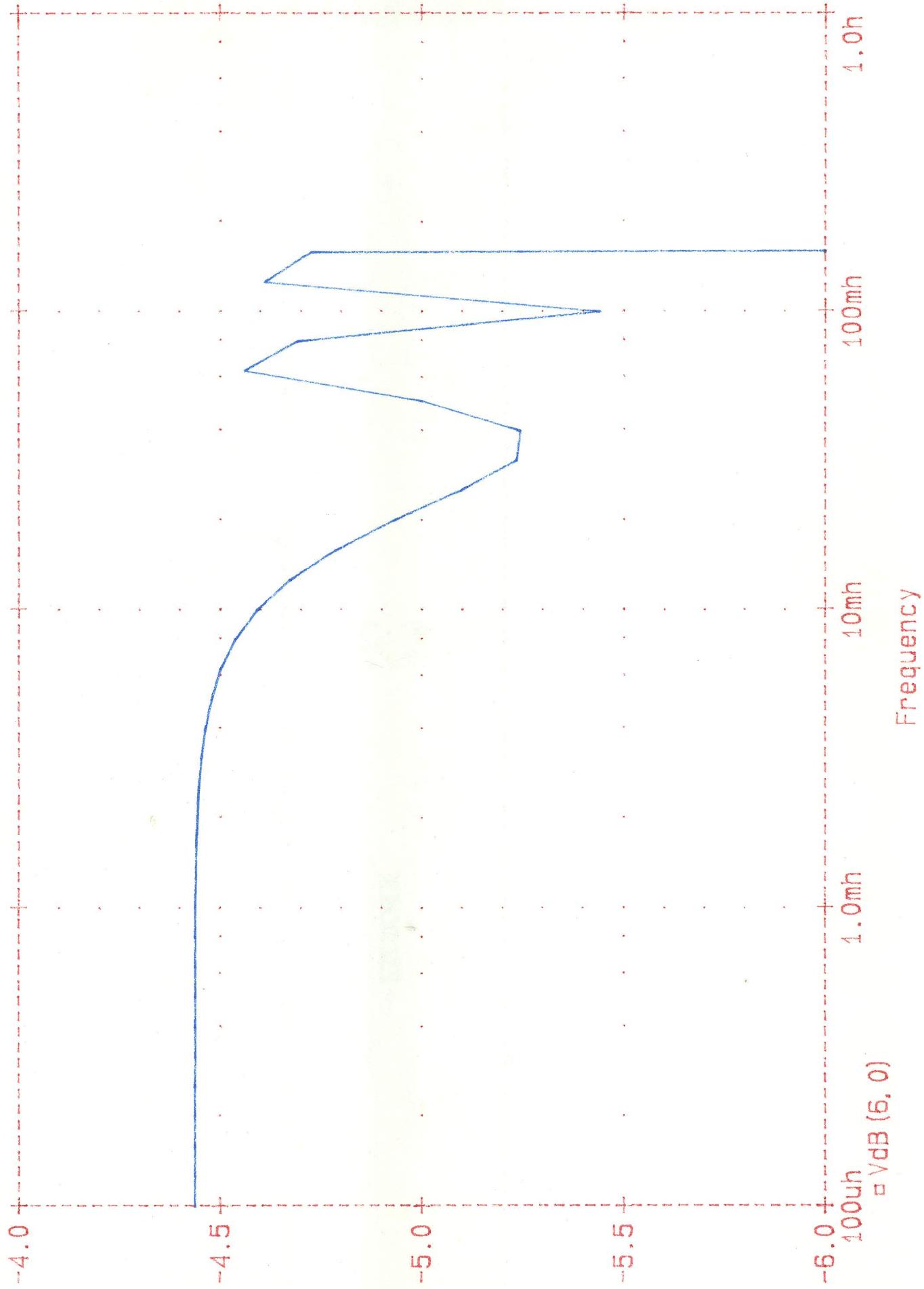

CHEBYSHEV LOWPASS FILTER -- 8TH-ORDER Ro=1.5

Temperature: 27.0

Date/Time run: 12/ 3/86 22: 13: 36

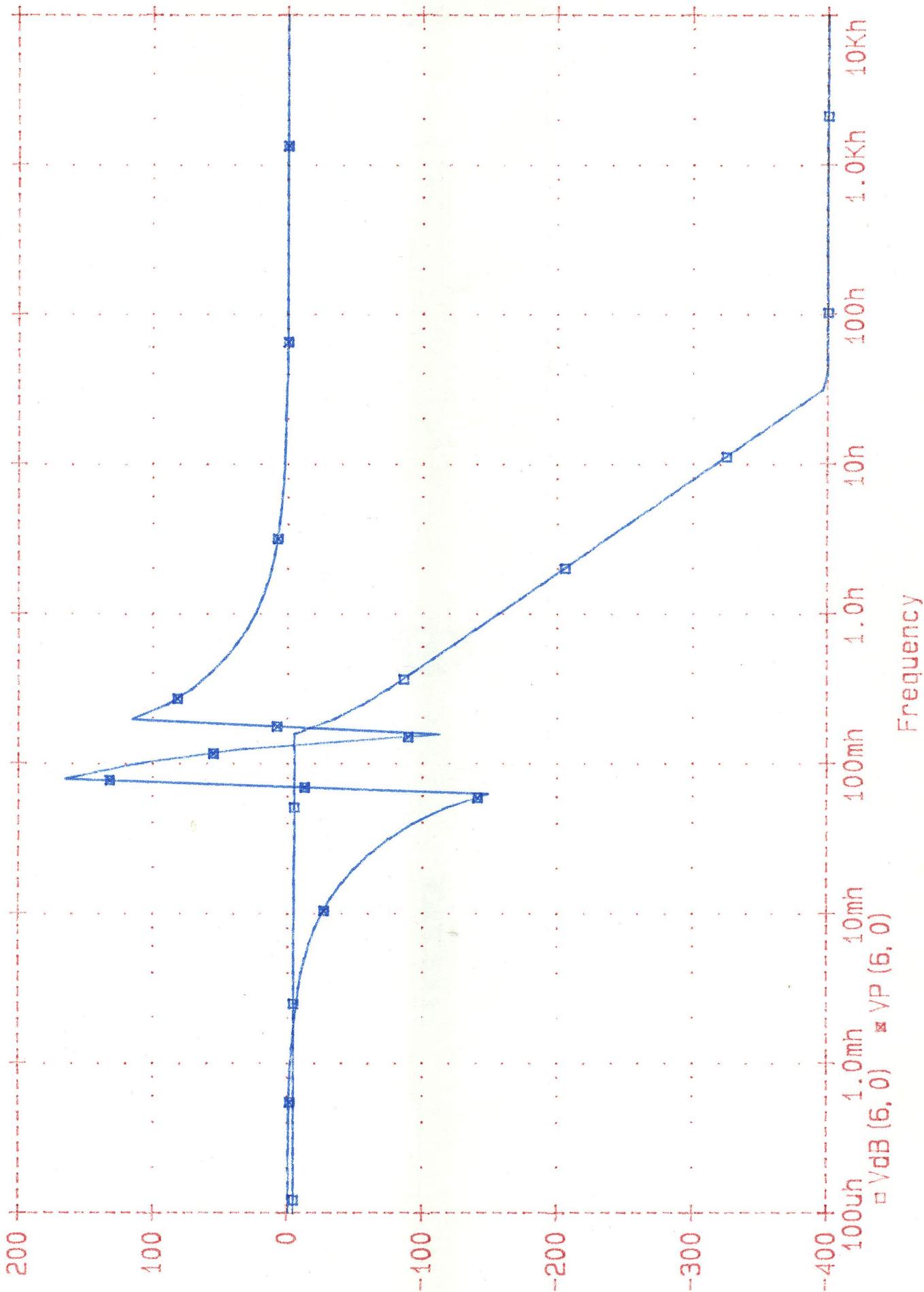

E-E 448 Passive and Active Filter Design
 Homework

100
105

BENMEI CHEN

Compare the magnitude and phase responses of 4-th order Bessel, Butterworth and transitional filters. For each of the three filters, determine the following:

- a) $H(s)$, b) pole locations, c) realization (schematic), and d) from SPICE $|H(j\omega)|^2$ (dB) and $\phi(\omega)$ (degrees) for $0 \leq \tau_0 \omega < 10$ rad.

Make a statement about the relative merits of the three filters.

The group delays (for Bessel filters) and the load resistances are given below:

<u>Filter</u>	<u>Group Delay, $\tau(0)$ (sec.)</u>	<u>Load Resistance (ohms)</u>
A	2	.5
B	2	1.5
C	2.5	2.0
D	2.5	.75
E	3	.80
F	3	2.0

<u>A</u>	<u>B</u>	<u>C</u>	<u>D</u>	<u>E</u>	<u>F</u>
G.A.	B.C.	F.H.	T.M.	K.P.	H.R.
L.A.	R.H.	B.K.	S.N.	T.R.	T.W.
C.C.	A.H.	B.M.	M.P.	M.R.	D.Y.

Compare the magnitude and phase responses of 4-th order Bessel, Butterworth and transitional filters. For each of these three filters, determine the

a) $H(s)$

BESSEL: $B : \tau(0) = 2$

$$\begin{aligned}\hat{B}_4(s) &= (2 \times 4 - 1)\hat{B}_3(s) + s^2 \hat{B}_2(s) = 7\hat{B}_3(s) + s^2 \hat{B}_2(s) \\ &= 7(s^3 + 6s^2 + 15s + 15) + s^2(s^2 + 3s + 3) \\ &= 7s^3 + 42s^2 + 105s + 105 + s^4 + 3s^3 + 3s^2 \\ &= s^4 + 10s^3 + 45s^2 + 105s + 105\end{aligned}$$

$$H(s) = \frac{k}{\hat{B}_4(s)}$$

$$k = \hat{B}_4(0) = 105$$

$$\hat{B}_4(2s) = 16s^4 + 80s^3 + 180s^2 + 210s + 105$$

$$H(s) = \frac{105}{16s^4 + 80s^3 + 180s^2 + 210s + 105}$$

$$\text{Butterworth} = H(s) = \frac{1}{s^4 + 2.61312593s^3 + 3.41421356s^2 + 2.61312593s + 1}$$

$$\text{TRANSITIONAL} = \text{POLES OF BESSEL FILTER} = s_{1,2} = -1.448105302 \pm j0.433617062$$

$$s_{3,4} = -1.051894699 \pm j1.328709021$$

$$\text{POLES OF BUTTERWORTH FILTER} = s_{1,2} = -0.38268343 \pm j0.92387953$$

$$s_{3,4} = -0.92387953 \pm j0.38268343$$

POLES FOR TRAN. FILTER


$$\begin{aligned}s_{1,2} &= \frac{-1.051894699 - 0.38268343}{2} \pm j \frac{1.328709021 + 0.92387953}{2} \\ &= -0.717289065 \pm j1.126294276\end{aligned}$$

$$\begin{aligned}s_{3,4} &= \frac{-1.448105302 - 0.92387953}{2} \pm j \frac{0.433617062 + 0.38268343}{2} \\ &= -1.185992416 \pm j0.408150246\end{aligned}$$

$$\begin{aligned}H(s) &= \frac{k}{(s^2 + 1.434578130s + 1.783042399) \times (s^2 + 2.371984832s + 1.573164634)} \\ &= \frac{2.805019243}{s^4 + 3.806562962s^3 + 6.759004598s^2 + 6.486177104s + 2.805019243}\end{aligned}$$

b) POLE LOCATIONS :

S-PLANE :

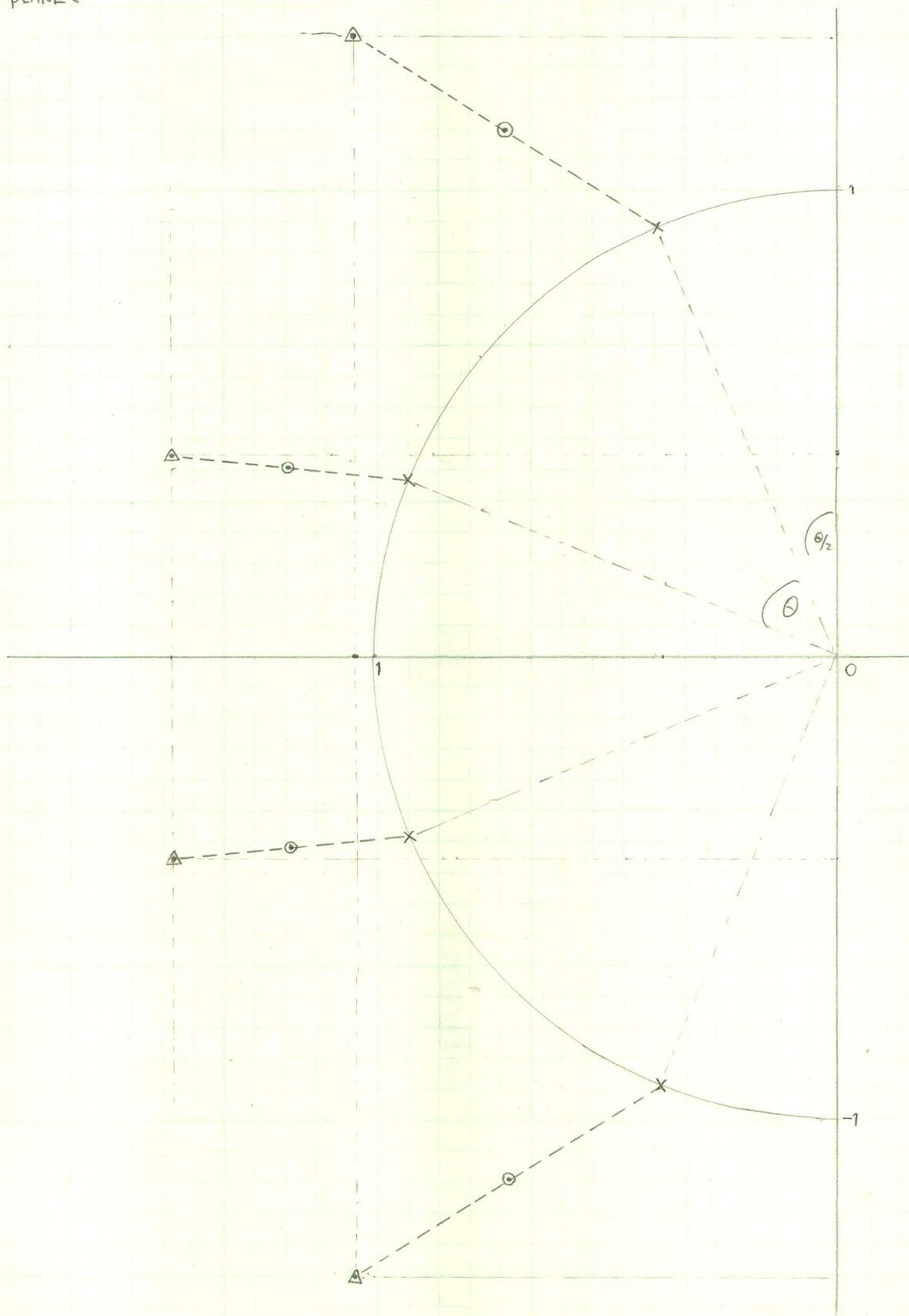

X -- POLES OF BUTTERWORTH FILTER

△ POLES OF BESSEL FILTER

○ POLES OF TRANSITIONAL FIL.

↑ normalize

-5

42,981 50 SHEETS 5 SQUARE
42,982 100 SHEETS 5 SQUARE
42,986 200 SHEETS 5 SQUARE
MADE IN U.S.A.
NATIONAL

c) REALIZATION (SCHEMATIC):

BESSEL FILTER: $H(s) = \frac{k}{16s^4 + 80s^3 + 180s^2 + 210s + 105}$

$H(0) = \frac{k}{105} = \frac{1.5}{1+1.5} \Rightarrow k = 63$

(1)
$$\rho(s)\rho(-s) = 1 - \frac{4}{1.5} \cdot \frac{3969}{(16s^4 + 80s^3 + 180s^2 + 210s + 105)(16s^4 - 80s^3 + 180s^2 - 210s + 105)}$$

$$= \frac{256s^4 - 640s^3 + 2160s^2 - 6300s + 441}{(16s^4 + 80s^3 + 180s^2 + 210s + 105)(16s^4 - 80s^3 + 180s^2 - 210s + 105)}$$

$$= \frac{16(s^4 + 4.29924s^3 + 7.99175s^2 + 6.75185s + 1.31251) \times 16(s^4 - 4.29924s^3 + \dots)}{(16s^4 + 80s^3 + 180s^2 + 210s + 105)(16s^4 - 80s^3 + 180s^2 - 210s + 105)}$$

$$\rho(s) = \frac{s^4 + 4.29924s^3 + 7.99175s^2 + 6.75185s + 1.31251}{s^4 + 5s^3 + 11.25s^2 + 13.125s + 6.5625}$$

$$Z_{in}(s) = \frac{1 + \rho(s)}{1 - \rho(s)} = \frac{2s^4 + 9.29924s^3 + 19.24175s^2 + 20.00185s + 7.87501}{0.70076s^3 + 3.25825s^2 + 6.37315s + 5.24999}$$

$Z_{in}(0) = 1.5 = R_e$

$$\frac{2.85404s}{0.70076s^3 + 3.25825s^2 + 6.37315s + 5.24999} \Big/ \frac{2s^4 + 9.29924s^3 + 19.24175s^2 + 20.00185s + 7.87501}{2s^4 + 9.29919s^3 + 18.18423s^2 + 14.98368s}$$


$$\frac{0.66579s}{0.70076s^3 + 3.25825s^2 + 6.37315s + 5.24999}$$

$$\frac{0.93141s}{1.13003s + 5.24999} \Big/ \frac{1.05252s^2 + 5.01817s + 7.87501}{1.05252s^2 + 4.88990s}$$


$$\frac{0.14350s}{1.13003s + 5.24999}$$

$$\frac{1.5}{5.24999} \Big/ \frac{7.87501}{7.87501}$$

$$0$$

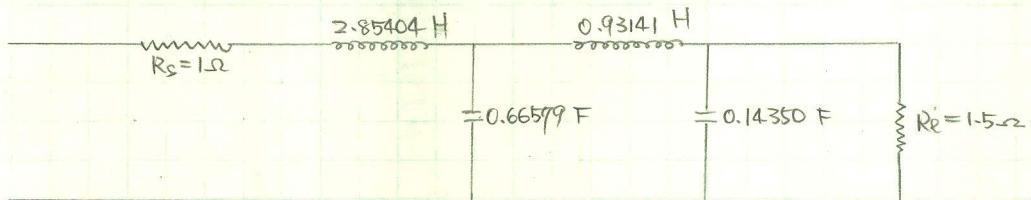

BUTTERWORTH FILTER:

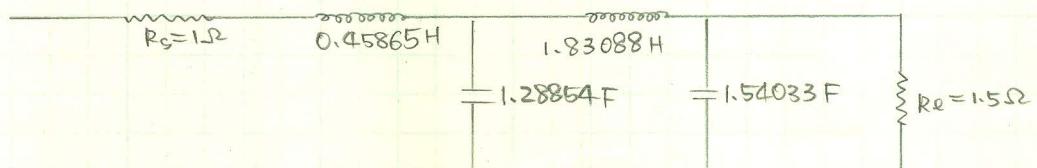

TRANSITIONAL FILTER:

$$H(s) = \frac{k}{s^4 + 3.80563s^3 + 6.75900s^2 + 6.48618s + 2.80502}$$

$$H(0) = \frac{k}{2.80502} = \frac{1.5}{1+1.5} \Rightarrow k = 1.68301$$

$$p(s)p(-s) = 1 - \frac{4}{1.5} \cdot \frac{2.83253}{(s^4 + 3.80563s^3 + 6.75900s^2 + 6.48618s + 2.80502)(s^4 - 3.80563s^3 + 6.759s^2 - 6.48618s + 2.80502)}$$

$$= \frac{s^8 - 0.96482s^6 + 1.92734s^4 - 4.15227s^2 + 0.31473}{(s^4 + 3.80563s^3 + 6.75900s^2 + 6.48618s + 2.80502)(s^4 - 3.80563s^3 + 6.759s^2 - 6.48618s + 2.80502)}$$

$$= \frac{(s^4 + 3.14080s^3 + 4.44991s^2 + 3.02414s + 0.56103)(s^4 - 3.14080s^3 + 4.44991s^2 - \dots)}{(s^4 + 3.80563s^3 + 6.75900s^2 + 6.48618s + 2.80502)(s^4 - 3.80563s^3 + 6.75900s^2 - \dots)}$$


$$p(s) = \frac{s^4 + 3.14080s^3 + 4.44991s^2 + 3.02414s + 0.56103}{s^4 + 3.80563s^3 + 6.75900s^2 + 6.48618s + 2.80502}$$

$$Z_{in}(s) = \frac{1+p(s)}{1-p(s)} = \frac{2s^4 + 6.94643s^3 + 11.20891s^2 + 9.51032s + 3.36605}{0.66483s^3 + 2.30909s^2 + 3.46204s + 2.24399}$$

$$Z_{in}(0) = 1.50003 \approx 1.5 \Omega = R_e$$

$$\frac{0.66483s^3 + 2.30909s^2 + 3.46204s + 2.24399}{2s^4 + 6.94643s^3 + 11.20891s^2 + 9.51032s + 3.36605} \cdot \frac{3.00829s}{2s^4 + 6.94643s^3 + 10.41481s^2 + 6.75057s} = \frac{0.83721s}{0.66483s^3 + 2.30909s^2 + 3.46204s + 2.24399} - \frac{0.66483s^3 + 2.31050s^2 + 2.81811s}{0.64393s + 2.24399}$$
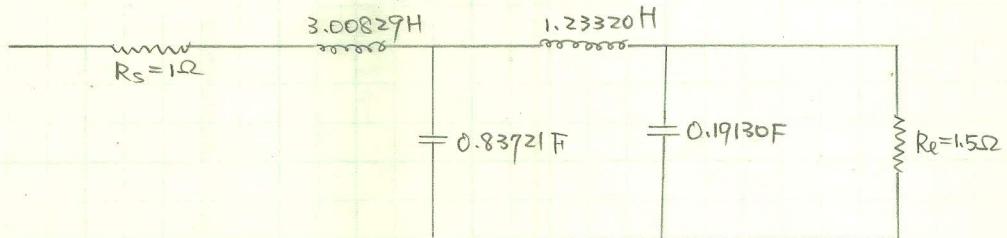
$$\frac{0.64393s + 2.24399}{0.79410s^2 + 2.76730s} \cdot \frac{1.23320s}{0.79410s^2 + 2.76730s} = \frac{0.19130s}{0.64393s + 2.24399} - \frac{0.64393s}{2.24399} + \frac{1.50003}{3.36605} - \frac{3.36605}{3.36605} = 0$$



42.384 50 SHEETS SQUARE
 42.384 100 SHEETS SQUARE
 42.384 200 SHEETS SQUARE
 NATIONAL

d) FROM THE GRAPHICS WE GOT, IT IS EASY TO SEE THAT :

THE FREQUENCY RESPONSE OF BESSEL FILTER DECREASE MORE SLOWLY THAN THE OTHER TWO FILTERS . AT $f = 1 \text{ Hz}$

$$\text{BESSEL} = |H(\omega)|_{\text{dB}} \doteq -53 \text{ dB}$$

$$\text{TRANSITIONAL} = |H(\omega)|_{\text{dB}} \doteq -59 \text{ dB}$$

$$\text{BUTTERWORTH} = |H(\omega)|_{\text{dB}} \doteq -64 \text{ dB}$$

BUT , IN PHASE RESPONSE , BESSEL FILTER HAS A MOST-WIDE-LINEAR-PHASE-BAND.

LINEAR PHASE BAND :

$$\text{BESSEL} = |f| < 0.225 \text{ Hz}$$

$$\text{TRANSITIONAL} = |f| < 0.200 \text{ Hz}$$

$$\text{BUTTERWORTH} = |f| < 0.179 \text{ Hz}$$

SO , IN MAGNITUDE CASE , BUTTERWORTH FILTER IS THE BEST .

BESSEL FILTER IS THE WORST .


TRANSITIONAL FILTER IS BETWEEN THOSE TWO .

IN PHASE CASE , THEY ARE OPPOSITE .

BESSEL 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\Omega$

Date/Time run: 12/ 8/86 22:07:08


Temperature: 27.0

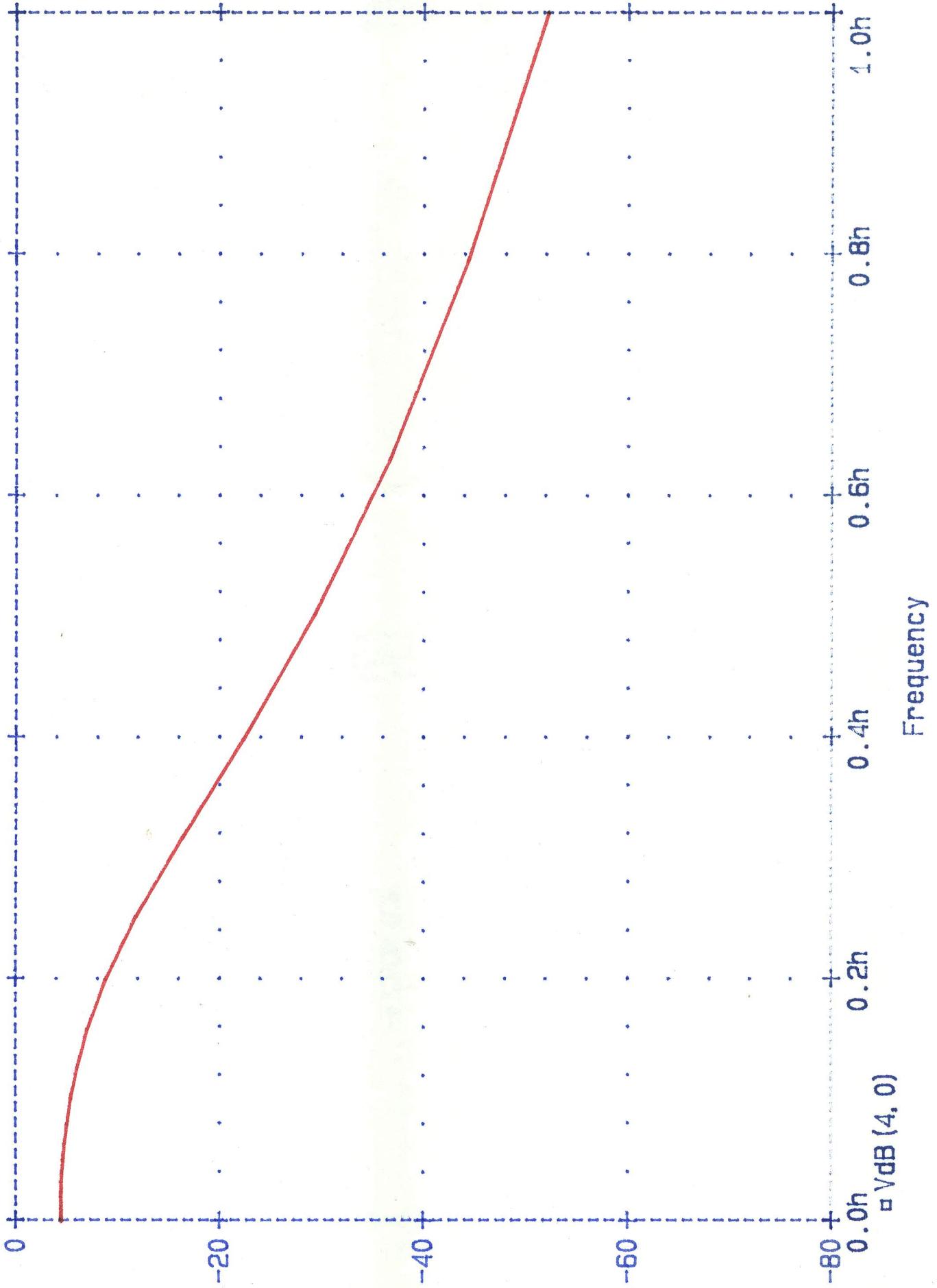

BUTTERWORTH 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\Omega$

Date/Time run: 12/ 8/86 21: 42: 54


Temperature: 27.0

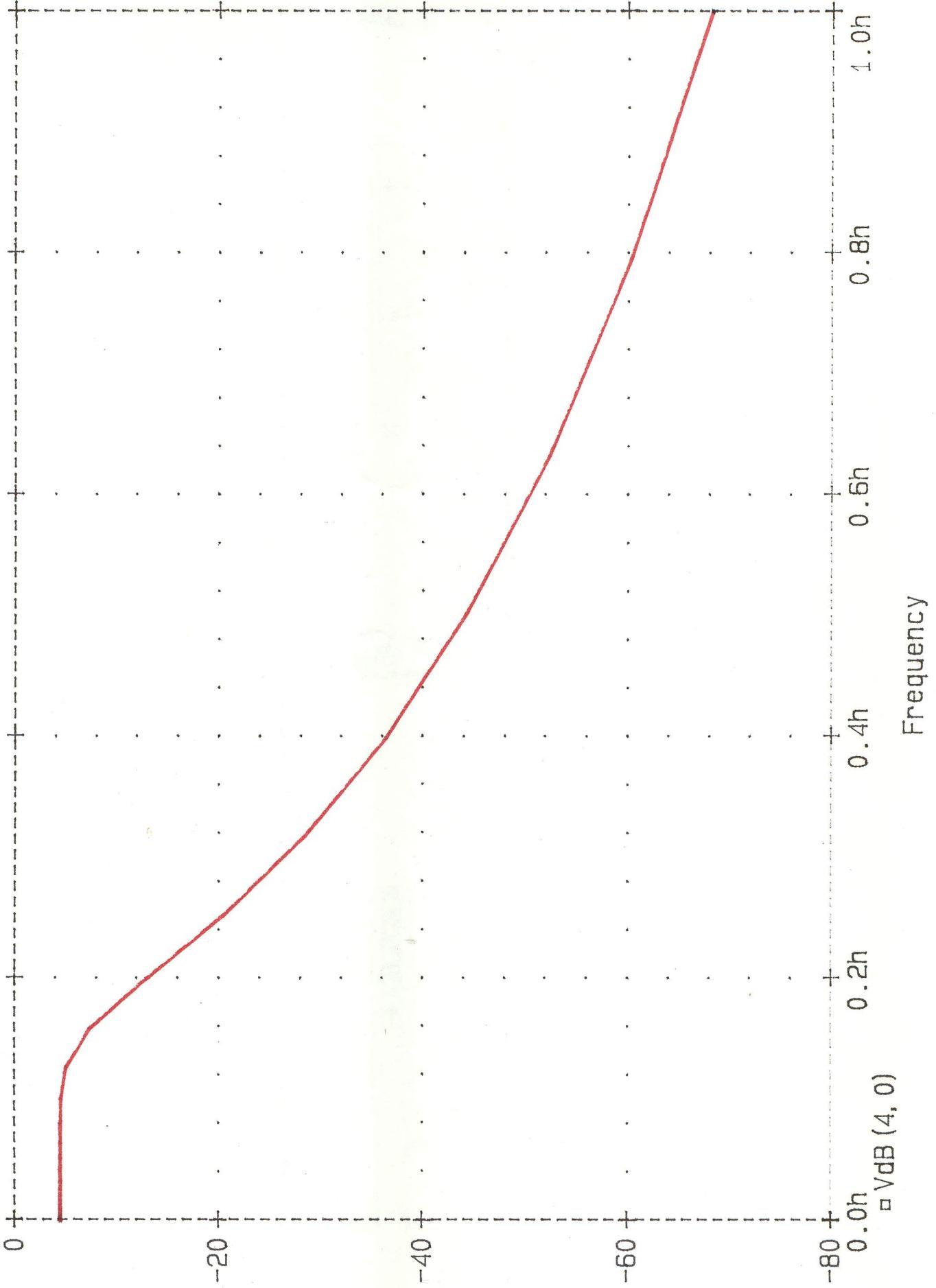

TRANSITIONAL 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\Omega$

Date/Time run: 12/ 8/86 22: 26: 32


Temperature: 27.0

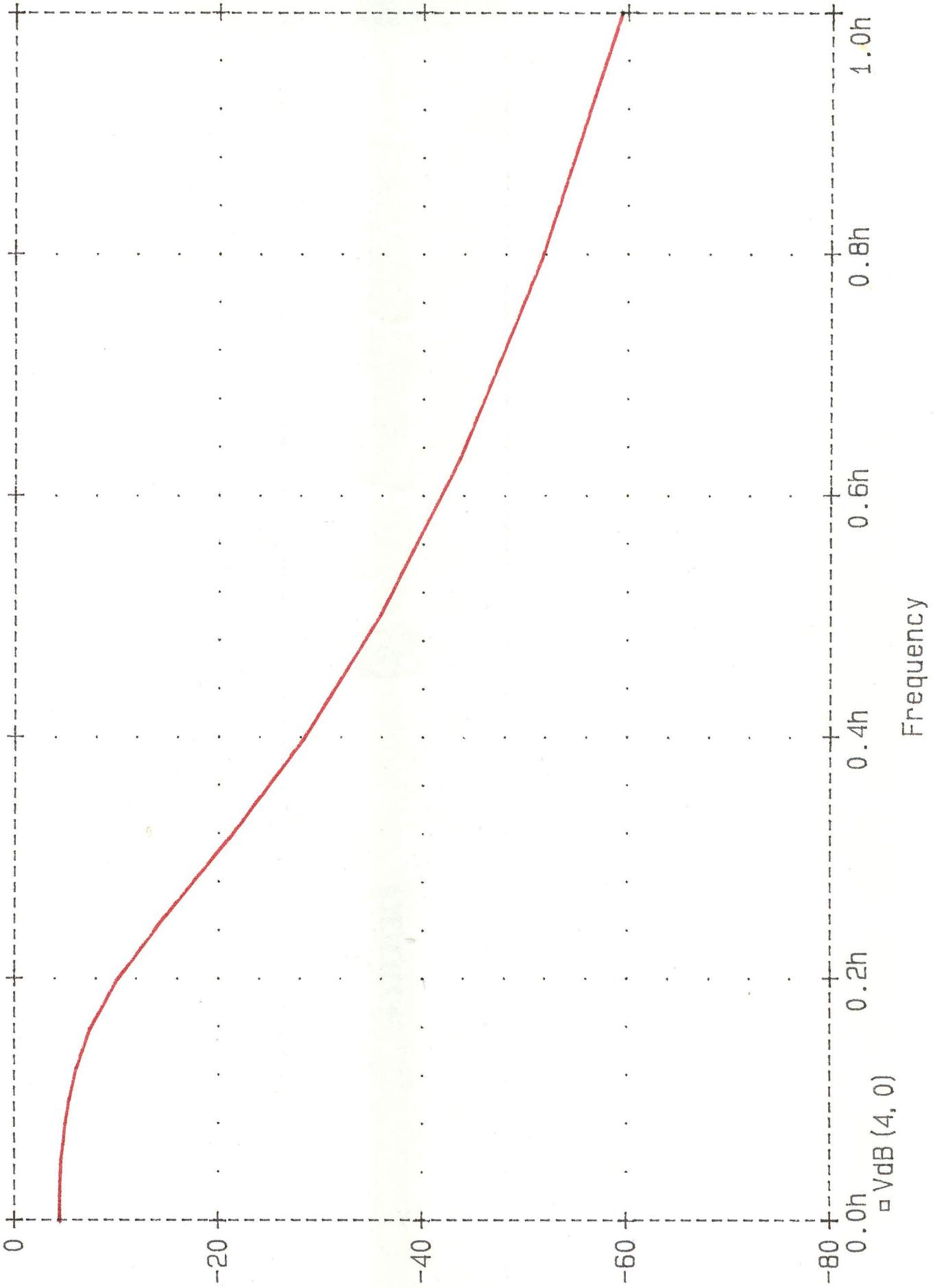


BESSEL 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\text{ohm}$

Date/Time run: 12/ 8/86 22: 07: 08

Temperature: 27.0

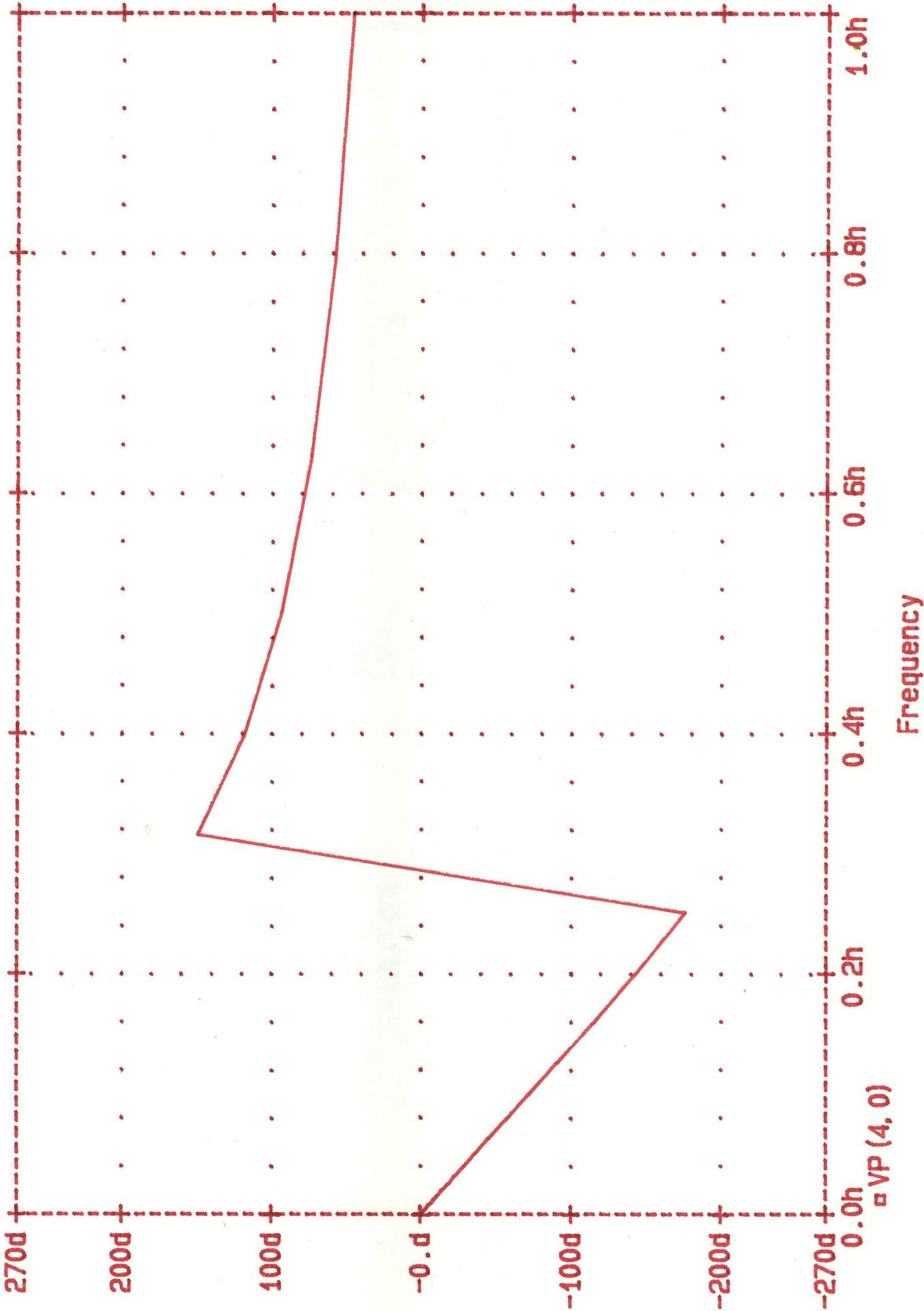

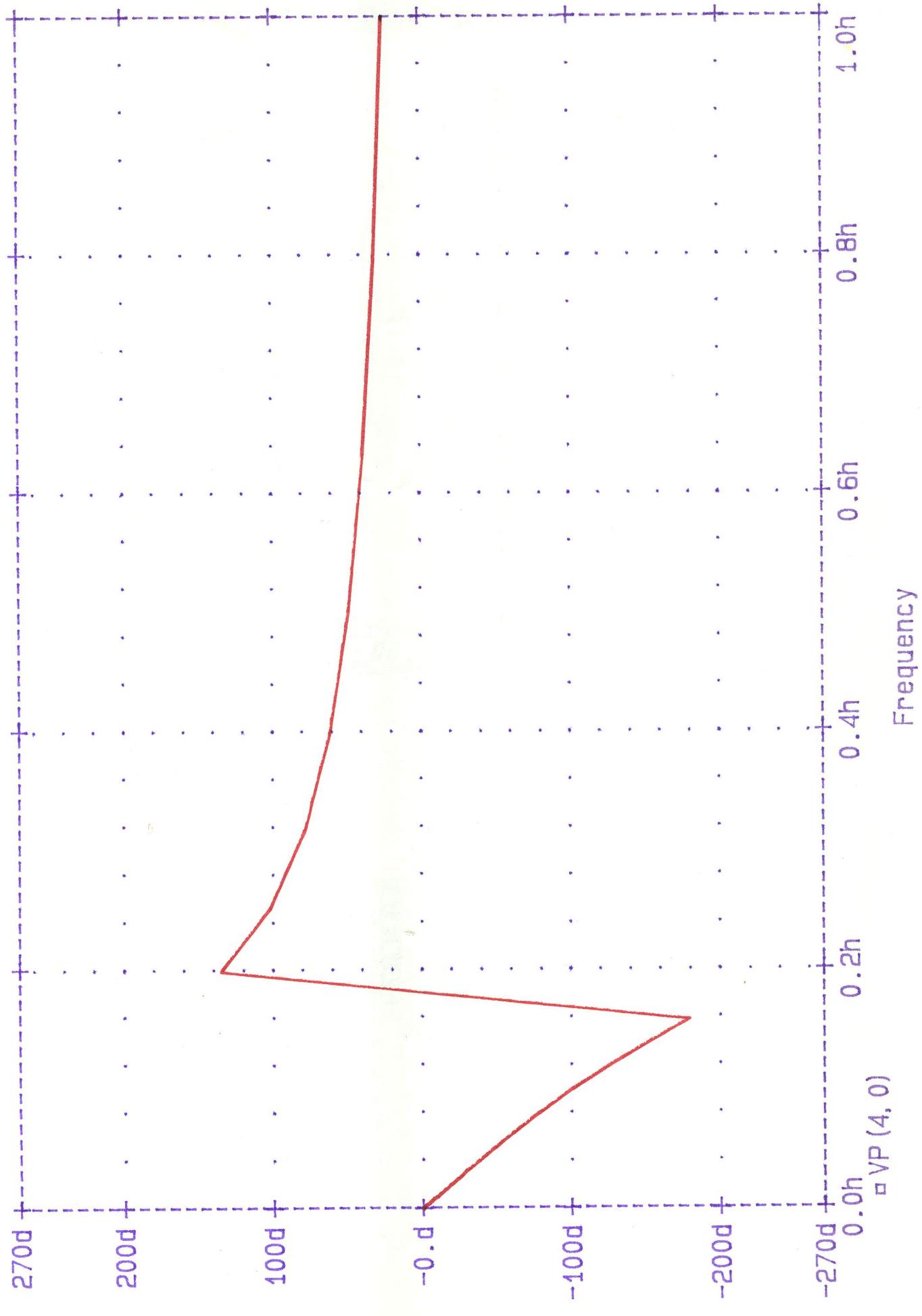BUTTERWORTH 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\text{ohm}$ Temperature: 27.0
Date/Time run: 12/ 8/86 21: 42: 54



TRANSITIONAL 4th-ORDER LOWPASS FILTER WITH $R_0=1.5\text{ohm}$ Temperature: 27.0
Date/Time run: 12/ 8/86 22: 26: 32

