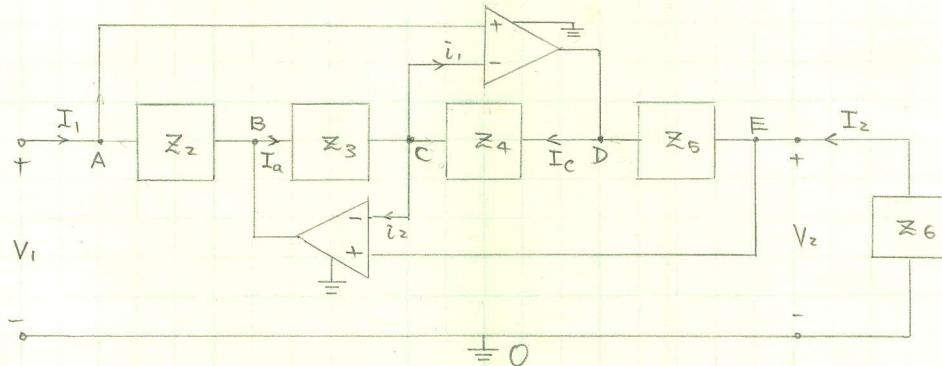


For networks (a) and (b) on p.22, derive $f(s) = I_2/I_1$ and $k = V_1/V_2$, use your derivations to obtain equations (51) and (52)

$\frac{20}{20}$

(a) Antoniou's GIC Circuit



$$V_{AB} = I_1 Z_2, \quad V_{ED} = I_2 Z_5, \quad V_{CO} = V_{AO} = V_1, \quad V_{CO} = V_{EO} = V_2$$

$$V_{BC} = V_{BO} - V_{OC} = V_{BA} - V_{AO} - V_{OC} = V_{BA}$$

$$V_{DC} = V_{DO} - V_{OC} = V_{DE} - V_{EO} - V_{OC} = V_{DE}$$

$$I_a = V_{BC} / Z_3 = V_{BA} / Z_3 = -V_{AB} / Z_3 = -I_1 Z_2 / Z_3$$

$$I_c = V_{DC} / Z_4 = V_{DE} / Z_4 = -V_{ED} / Z_4 = -I_2 Z_5 / Z_4$$

$$I_a = -I_c \quad (\text{Because } i_1 = i_2 = 0) \quad \text{so,}$$


$$-I_1 Z_2 / Z_3 = +I_2 Z_5 / Z_4$$

$$f(s) = \frac{I_2}{I_1} = \frac{-Z_2 \cdot Z_4}{Z_3 \cdot Z_5}, \quad k = \frac{V_2}{V_1} = \frac{V_{CO}}{V_{CO}} = 1$$

FROM THE EQUATION (50) ON P.21, WE HAVE

$$Z_{in} = k f(s) \cdot \frac{V_2}{I_2} = -\frac{Z_2 \cdot Z_4}{Z_3 \cdot Z_5} \cdot 1 \cdot (-Z_6) = \frac{Z_2 \cdot Z_4 \cdot Z_6}{Z_3 \cdot Z_5} \quad \text{QED}$$

(b) Riordan's GIC Circuit

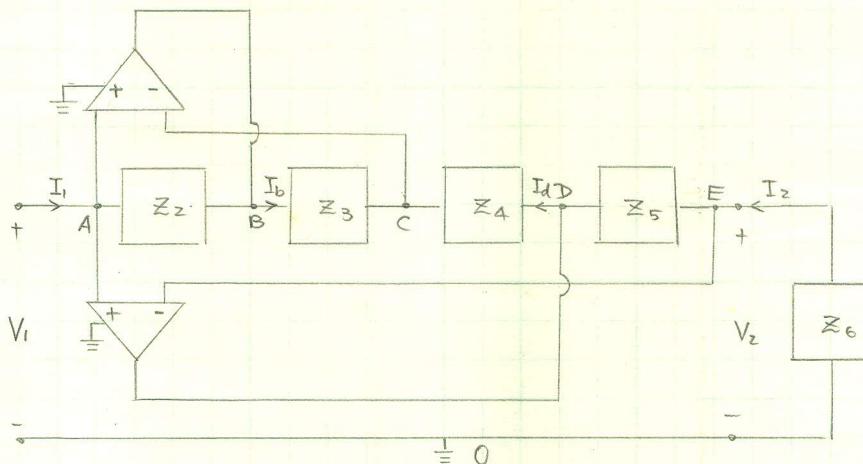

Apply the principle of virtual short circuit for both operational amplifiers.

$$V_{AO} = V_{CO} = V_{EO} = V_1 = V_2$$

$$I_d = V_{DC} / Z_4 = (V_{DO} - V_{OC}) / Z_4 = (V_{DE} - V_{EO} - V_{OC}) / Z_4$$

$$= (-V_{ED} - V_{EO} + V_{CO}) / Z_4 = -\frac{V_{ED}}{Z_4} = -\frac{Z_5 \cdot I_2}{Z_4}$$

$$I_b = V_{BC} / Z_3 = (V_{BO} - V_{OC}) / Z_3 = (V_{BA} - V_{AO} - V_{OC}) / Z_3$$

$$= (-V_{AB} - V_{AO} + V_{CO}) / Z_3 = -\frac{V_{AB}}{Z_3} = -\frac{Z_2}{Z_3} \cdot I_1$$

$$I_d = -I_b$$

$$-\frac{Z_5}{Z_4} I_2 = \frac{Z_2}{Z_3} \cdot I_1$$

$$f(s) = \frac{I_2}{I_1} = \frac{-Z_2 \cdot Z_4}{Z_3 \cdot Z_5}$$


$$K = V_1 / V_2 = 1$$

$$\text{SO, } Z_{in} = R f(s) \cdot \frac{V_2}{I_1} = -\frac{Z_2 \cdot Z_4}{Z_3 \cdot Z_5} \cdot (-Z_6)$$


$$= \frac{Z_2 \cdot Z_4}{Z_3 \cdot Z_5} \cdot Z_6 \quad \text{QED}$$

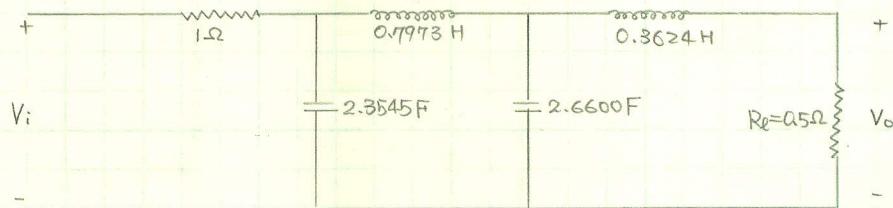10-2. Find an active ladder circuit realization of an n th-order low-pass Chebyshev filter with 0.1 dB ripples, ripple bandwidth $f_r = 3.4$ kHz, and a terminating load resistor $R_e = 600\Omega$, where $n=4$ and use GIC. 20/20


Solution: * From the circuit of Fig. 8-17 on page 261 and Table 8-2 on page 262 in text, we have the normalized Chebyshev low-pass filter with 0.1 dB ripple and ripple bandwidth $\omega_r = 1$ rad/s as well as $R_e = 0.5\Omega$:



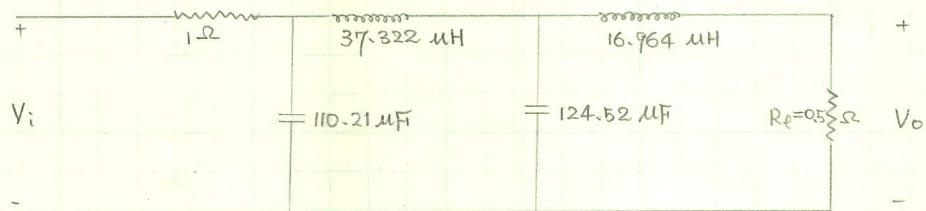* Scaling to the ripple bandwidth $f_r = 3.4$ kHz, $\omega_r = 2\pi f_r = 21362.83$ rad/s



* Impedance scaling by $600/0.5 = 1200$

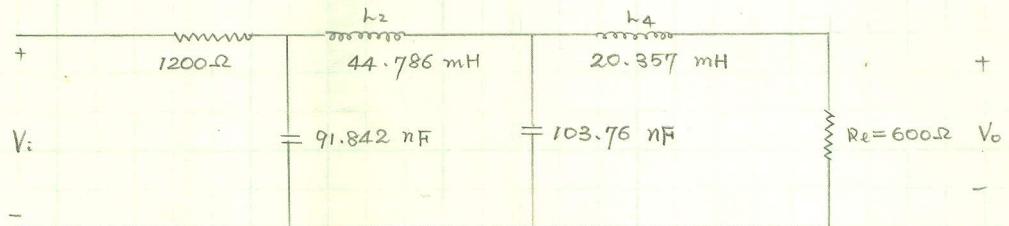


* Replace the inductors in the circuit with GIC


$$\text{LET } R_2 = R_3 = R_4 = 1\text{ k}\Omega \text{ and } C_5 = 1\text{ }\mu\text{F}$$

$$\text{THUS FOR } L_2 = 44.786\text{ mH}, \quad R'_6 = 44.786\text{ }\Omega$$
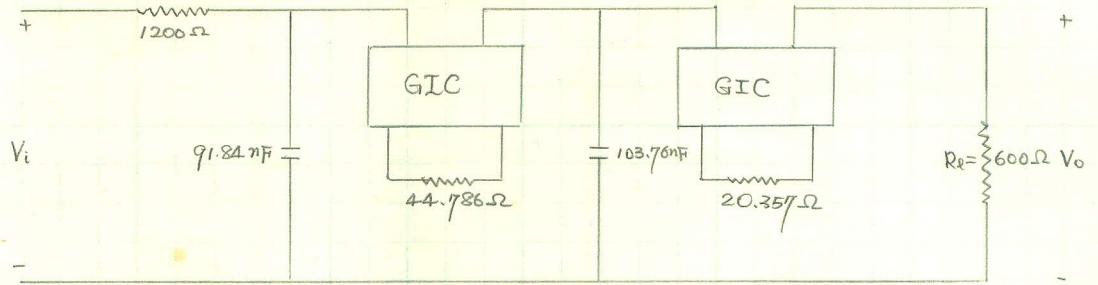
$$\text{FOR } L_4 = 20.357\text{ mH}, \quad R''_6 = 20.357\text{ }\Omega$$




OR:

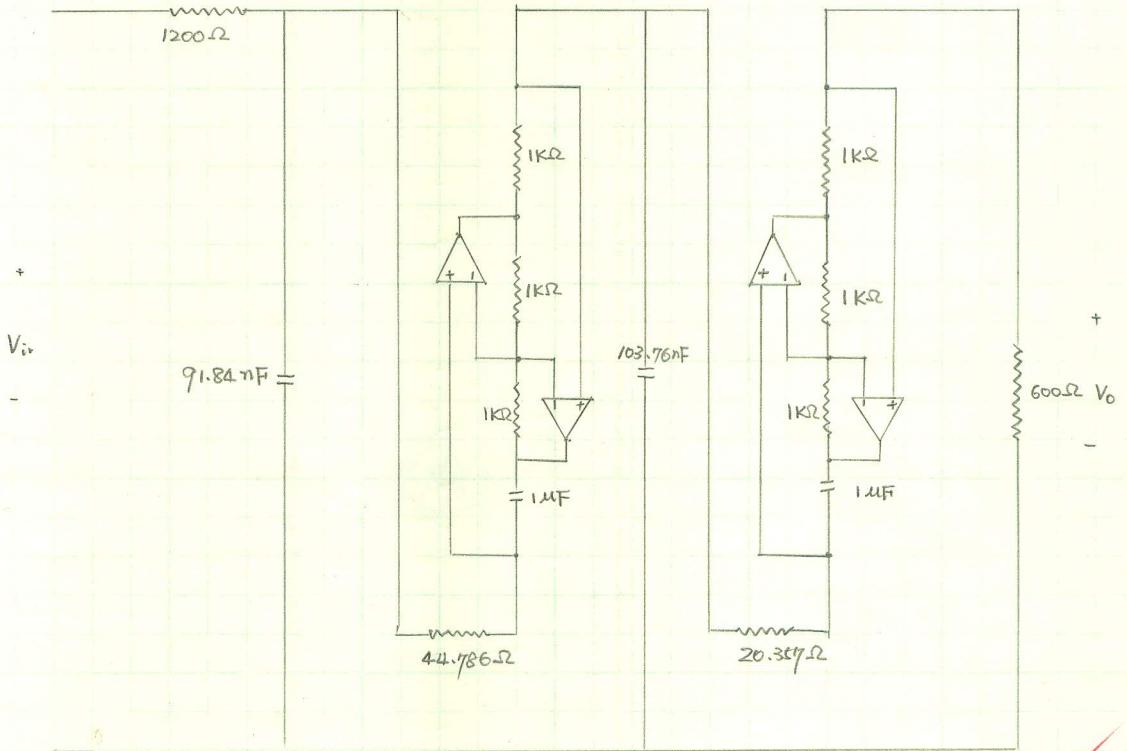


42-381 50 SHEETS 5 SQUARE
 42-382 100 SHEETS 5 SQUARE
 42-383 200 SHEETS 5 SQUARE
 42-384 300 SHEETS 5 SQUARE
 NATIONAL
 MADE IN U.S.A.

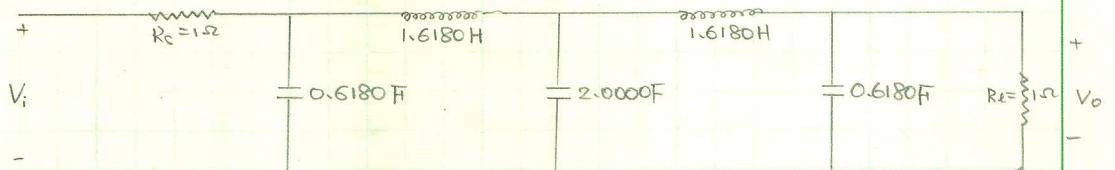10-3 Find an active ladder circuit realization of an n th-order high-pass Butterworth filter with the 3 dB cutoff frequency $f_c = 10$ KHz, and the terminating resistor $R_t = 600\Omega$, where $n=5$ and use FDNR.


Solution: From the circuit at part c of Fig. 8-9 on page 237 and the Table 8-1 on page 238 in text, we can have the normalized Butterworth low-pass filter with the 3 dB cutoff freq. $\omega_c = 1$ rad/s and the terminating resistors $R_t = R_s = 1\Omega$.



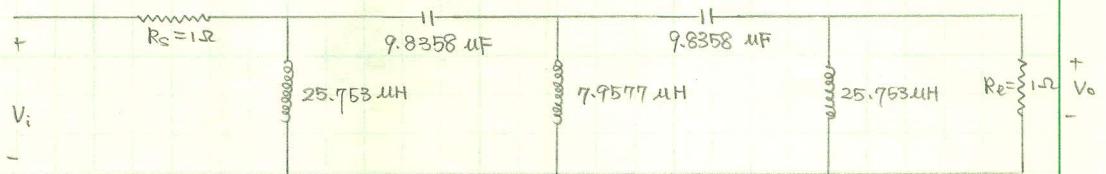
THEN THE HIGH-PASS FILTER WITH CUTOFF FREQ. $\omega_c = 2\pi f_c = 62832$ rad/s



Divide all of elements by s , we have

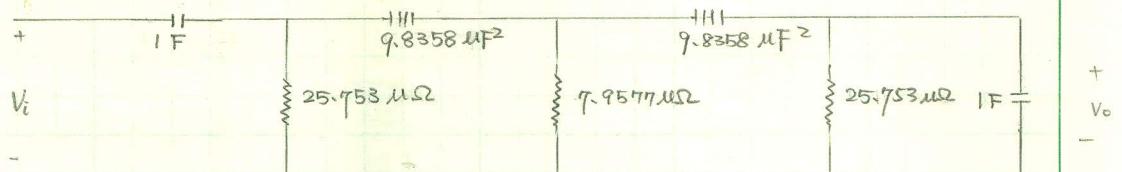

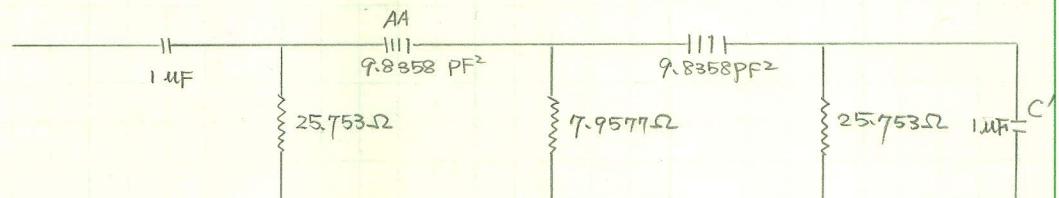To obtain more reasonable values for the elements, we will scale impedance by 10^6




Using FDNR. with $R_2 = R_3 = R_4 = 1K\Omega$, $C_5 = 1\mu F$


FOR $AA = 9.8358 PF^2 \rightarrow C_1 = 9.8358 nF$

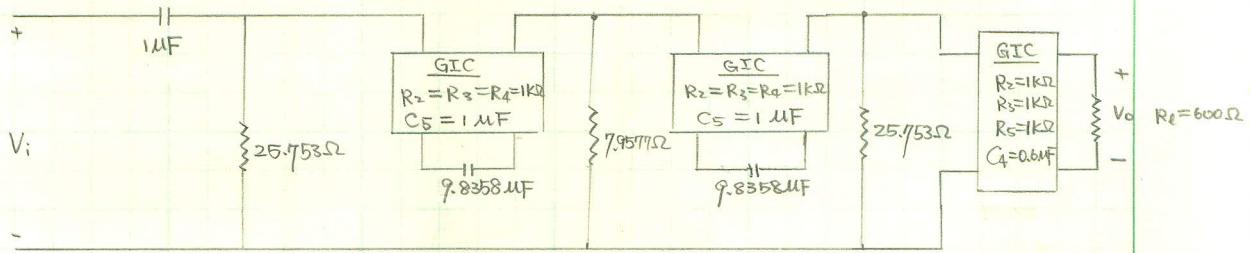And using the other FDNR with $R_2 = R_3 = R_5 = 1K\Omega$, $C_4 = 0.6\mu F$, $C'_1 = 1\mu F \rightarrow R_6 = 600\Omega$





OR:

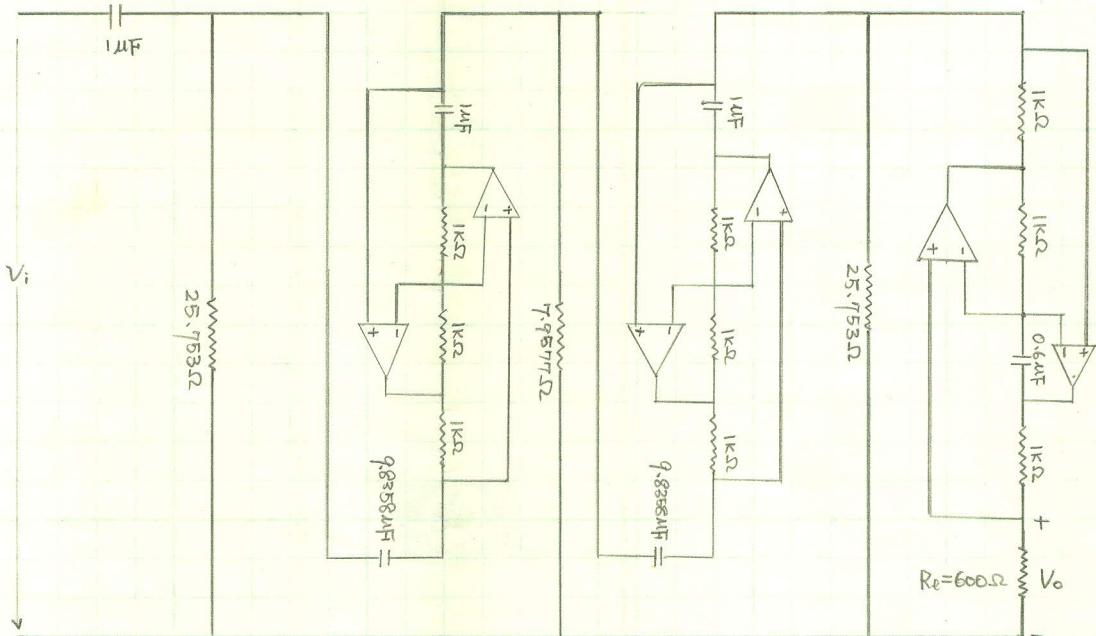

42,381 50 SHEETS 5 SQUARE
 42,382 100 SHEETS 5 SQUARE
 42,383 200 SHEETS 5 SQUARE
 NATIONAL
 Made in U.S.A.



10-6. Realize the following filters with Kuh's configuration:

$\frac{10}{10}$

- (c) A fourth-order bandpass Butterworth filter with center frequency $\omega_0 = 8 \text{ K rad/sec}$, bandwidth $B = 2 \text{ K rad/sec}$, and a midband gain 1.

Solution: From chapter 8 in the text, we know a fourth-order bandpass can be obtained by transforming a normalized second-order low-pass. Look up TABLE A 8-1 from the text on page 301, we have the transfer function of normalized 2-nd order low-pass Butterworth filter:

$$H'(s) = \frac{1}{s^2 + 1.41421356s + 1}$$

Then, from TABLE 8-5, we have the bandpass transfer function.

$$H(s) = H'(s) \Big|_{s \Rightarrow \frac{s^2 + \omega_0^2}{Bs}}$$

where, $\omega_0 = 8000 \text{ rad/sec}$. $B = 2000 \text{ rad/s}$

$$\begin{aligned} H(s) &= H'(s) \Big|_{s \Rightarrow \frac{s^2 + 64 \times 10^6}{4 \times 10^6 s}} \\ &= \frac{1}{\left(\frac{s^2 + 64 \times 10^6}{2000s}\right)^2 + 1.41421356 \cdot \left(\frac{s^2 + 64 \times 10^6}{2000s}\right) + 1} \\ &= \frac{4 \times 10^6 s^2}{s^4 + 2828.427124 s^3 + 132 \times 10^6 s^2 + 1.8101933 \times 10^{11} s + 4096 \times 10^{12}} \end{aligned}$$

Now, we are going to realize $H(s)$ by Kuh's configuration.

$$B(s) = s^4 + 2828.427124 s^3 + 1.32 \times 10^8 s^2 + 1.8101933 \times 10^{11} s + 4096 \times 10^{12}$$

$$\text{LET } D(s) = (s+1000)(s+2000)(s+3000)$$

$$\text{THEN } Y_{21} = -\frac{A(s)}{D(s)} = -\frac{4 \times 10^6 s^2}{D(s)}$$

AND

$$Y_{22} + Y_1 - \alpha Y_2 = \frac{B(s)}{D(s)} = \frac{s^4 + 2828.427124 s^3 + 1.32 \times 10^8 s^2 + 1.8101933 \times 10^{11} s + 4096 \times 10^{12}}{(s+1000)(s+2000)(s+3000)}$$

$$\frac{B(s)}{SD(s)} = \frac{s^4 + 2828.427124 s^3 + 1.32 \times 10^8 s^2 + 1.8101933 \times 10^{11} s + 4096 \times 10^{12}}{s^4 + 6000 s^3 + 11 \times 10^6 s^2 + 6 \times 10^9 s}$$

$$\frac{B(s)}{SD(s)} = 1 - 3171.517288x \cdot \frac{S^3 - 38151.41716S^2 - 55183764.21S - 1.29147 \times 10^{12}}{S(S+1000)(S+2000)(S+3000)}$$

$$= 1 + \frac{682665.2047}{S} - \frac{2022571.735}{S+1000} + \frac{2127662.575}{S+2000} - \frac{790927.6175}{S+3000}$$

SO, $y_{22} + Y_1 - \alpha Y_2 = 682665.2047 + S - \frac{2022571.735S}{S+1000} + \frac{2127662.575S}{S+2000} - \frac{790927.6175S}{S+3000}$

LET $y_{22} = 682665.2047 + S + \frac{1000000S}{S+1000} + \frac{2127662.575S}{S+2000} + \frac{600000S}{S+3000}$

$$= \frac{S^4 + 3.91633 \times 10^6 S^3 + 1.79176 \times 10^{10} S^2 + 2.00983 \times 10^{13} S + 4.09599 \times 10^{15}}{S^3 + 6000 S^2 + 11 \times 10^6 S + 6 \times 10^9}$$

$$S^3 + 6000S^2 + 11 \times 10^6 S + 6 \times 10^9 \sqrt{\frac{S^4 + 3.91633 \times 10^6 S^3 + 1.79176 \times 10^{10} S^2 + 2.00983 \times 10^{13} S + 4.09599 \times 10^{15}}{S^3 + 6000 S^2 + 11 \times 10^6 S + 6 \times 10^9}}$$

$$\frac{3.91033 \times 10^6 S^3 + 1.79066 \times 10^{10} S^2 + 2.00923 \times 10^{13} S + 4.09599 \times 10^{15}}{3.91033 \times 10^6 S^3 + 1.79066 \times 10^{10} S^2 + 2.00923 \times 10^{13} S + 4.09599 \times 10^{15}}$$

$$\frac{2.55733 \times 10^{-7}}{3.91033 \times 10^6 S^3 + 1.79066 \times 10^{10} S^2 + 2.00923 \times 10^{13} S + 4.09599 \times 10^{15}}$$

$$\frac{S^3 + 6000 S^2 + 11 \times 10^6 S + 6 \times 10^9}{S^3 + 4579.31 S^2 + 5.13826 \times 10^6 S + 1.04748 \times 10^9}$$

$$\frac{1.42069 \times 10^3 S^2 + 5.86174 \times 10^6 S + 4.95252 \times 10^9}{1.42069 \times 10^3 S^2 + 5.86174 \times 10^6 S + 4.95252 \times 10^9}$$

$$\frac{2.68203 \times 10^3 S}{3.91033 \times 10^6 S^3 + 1.79066 \times 10^{10} S^2 + 2.00923 \times 10^{13} S + 4.09599 \times 10^{15}}$$

$$\frac{3.91033 \times 10^6 S^3 + 1.57213 \times 10^{10} S^2 + 1.32828 \times 10^{13} S}{2.18525 \times 10^9 S^2 + 6.80950 \times 10^{12} S + 4.09599 \times 10^{15}}$$

SO THAT,

$$y_{22} = S + \frac{1}{2.55733 \times 10^{-7} + \frac{1}{2.68203 \times 10^3 S + \frac{1}{1.42069 \times 10^3 S^2 + 5.86174 \times 10^6 S + 4.95252 \times 10^9}}}$$

$$\frac{8.27052 \times 10^5}{4.95252 \times 10^9 + 5.86174 \times 10^6 S + 1.42069 \times 10^3 S^2} \sqrt{\frac{4.09599 \times 10^{15} + 6.80950 \times 10^{12} S + 2.18525 \times 10^9 S^2}{4.09599 \times 10^{15} + 4.84796 \times 10^{12} S + 1.17498 \times 10^9 S^2}}$$

$$\frac{2.52481 \times 10^{-3} / S}{1.96154 \times 10^{12} S + 1.01027 \times 10^9 S^2} \sqrt{\frac{4.95252 \times 10^9 + 5.86174 \times 10^6 S + 1.42069 \times 10^3 S^2}{4.95252 \times 10^9 + 2.55074 \times 10^6 S}}$$


$$\frac{5.92432 \times 10^5}{3.31100 \times 10^6 + 1.42069 \times 10^3 S} \sqrt{\frac{1.96154 \times 10^{12} + 1.01027 \times 10^9 S}{1.96154 \times 10^{12} + 8.41662 \times 10^8 S}}$$

$$\frac{1.96373 \times 10^{-2} / S}{1.68608 \times 10^8 S} \sqrt{\frac{3.31100 \times 10^6 + 1.42069 \times 10^3 S}{3.31100 \times 10^6}}$$

$$\frac{1.18164 \times 10^5}{1.68608 \times 10^8} \sqrt{\frac{1.68608 \times 10^8}{1.68608 \times 10^8}}$$

0

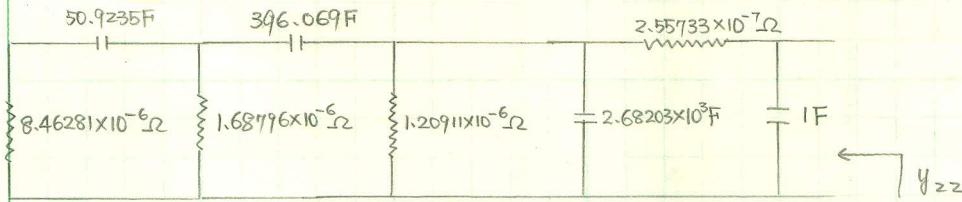SO, WE HAVE THE CIRCUIT REALIZATION FOR Y_{22}




$$\alpha Y_2 - Y_1 = Y_{22} - \frac{b(s)}{a(s)} = \frac{1022571.735 S}{s + 1000} + \frac{190927.6495 S}{s + 3000}$$


$$= \frac{1}{9.77927 \times 10^{-7} + 1/1022.571735 S} + \frac{1}{5.23759 \times 10^{-6} + 1/63.6425 S}$$

LET $Y_1 = 0$, $\alpha = 1$

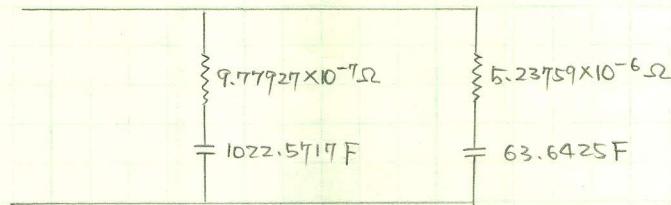
$$Y_2 = \frac{1}{9.77927 \times 10^{-7} + 1/1022.5717 S} + \frac{1}{5.23759 \times 10^{-6} + 1/63.6425 S}$$



SO, THE Kuh's configuration is:

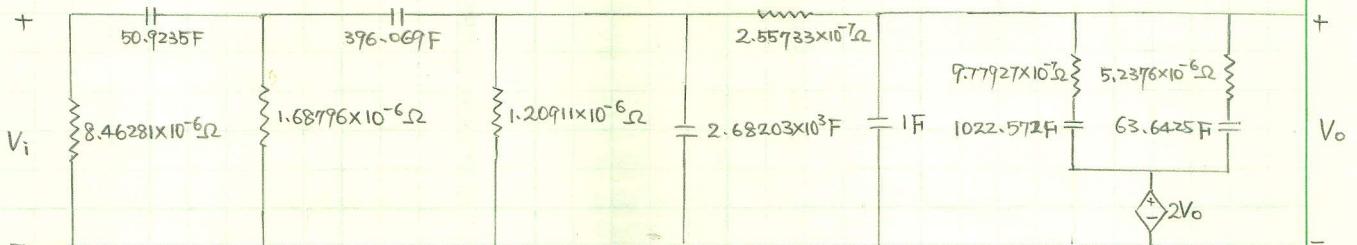

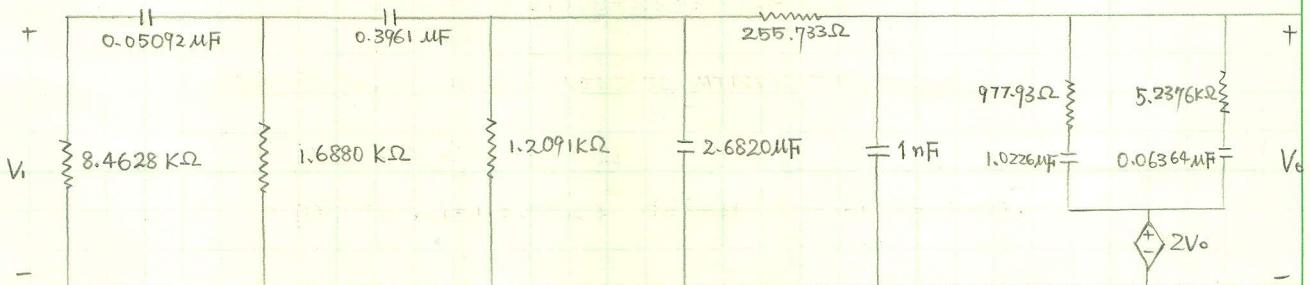IMPEDANCE SCALING BY 10^9 , WE HAVE THE CIRCUIT REALIZATION:




42 SHEETS SQUARE 50 SHEETS SQUARE 200 SHEETS SQUARE 42,389 42,389 200,000 NATIONAL Made in U.S.A.

10-8. Realize the following transfer function by Yanagisawa's method:

$$H(s) = 1 / (\hat{s}+1)(\hat{s}^2+1) \quad \text{where } \hat{s}=s/1000$$

50/50

SOLUTION:

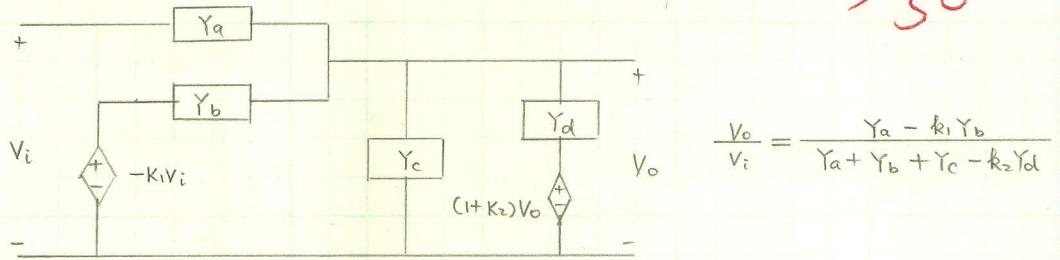

Now, the transfer function has a $\max(n_c, n_D) = 3$, so, we let $D(s) = (\hat{s}+1)(\hat{s}+2)$

$$H(s) = \frac{1}{(\hat{s}+1)(\hat{s}^2+1)}$$

$$= \frac{1}{(\hat{s}+1)(\hat{s}+2) \frac{(\hat{s}^2+1)}{\hat{s}+2}}$$

SO, $\frac{A(s)}{D(s)} = \frac{1}{(s+1)(\hat{s}+2)}$; $\frac{B(s)}{D(s)} = \frac{\hat{s}^2+1}{\hat{s}+2}$

(i) $\frac{A(s)}{D(s)} = \frac{1}{\hat{s}(\hat{s}+1)(\hat{s}+2)} = \frac{1/2}{\hat{s}} + \frac{1/2}{\hat{s}+2} - \frac{1}{\hat{s}+1}$

$$\frac{A(s)}{D(s)} = \frac{1}{2} + \frac{1}{2 + 1/4\hat{s}} - \frac{1}{1 + 1/2\hat{s}}$$

(ii) $\frac{B(s)}{D(s)} = \frac{(\hat{s}^2+1)}{\hat{s}(\hat{s}+2)} = \frac{\hat{s}^2+2\hat{s}-2\hat{s}+1}{\hat{s}^2+2\hat{s}} = 1 - \frac{2\hat{s}-1}{\hat{s}(\hat{s}+2)} = 1 + \frac{1/2}{\hat{s}} - \frac{5/2}{\hat{s}+2}$


$$\frac{B(s)}{D(s)} = \hat{s} + \frac{1}{2} - \frac{1}{2/5 + 1/4\hat{s}}$$

SO, WE HAVE $Y_{RC}^{(1)} = \frac{1}{2} + \frac{1}{2 + 1/4\hat{s}}$; $Y_{RC}^{(2)} = \frac{1}{1 + 1/2\hat{s}}$


$$Y_{RC}^{(3)} = \hat{s} + \frac{1}{2} ; Y_{RC}^{(4)} = \frac{1}{2/5 + 1/4\hat{s}}$$

AND LET $k_1=k_2=1$, WE HAVE ($\hat{s} = s/1000$)

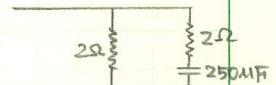
$$Y_a = Y_{RC}^{(1)} = \frac{1}{2} + \frac{1}{2 + 1/4\hat{s}} = \frac{1}{2} + \frac{1}{2 + 1/4000 s} \Rightarrow$$



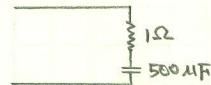
$$Y_b = Y_{RC}^{(2)} = \frac{1}{1 + 1/2\hat{s}} = \frac{1}{1 + 1/2000 s} \Rightarrow$$



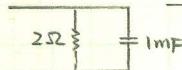
$$Y_c = Y_{RC}^{(3)} = \hat{s} + \frac{1}{2} = \frac{s}{1000} + \frac{1}{2} \Rightarrow$$


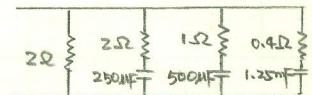
$$Y_d = Y_{RC}^{(1)} + Y_{RC}^{(2)} + Y_{RC}^{(4)} \Rightarrow$$




The overall realization is as follows:

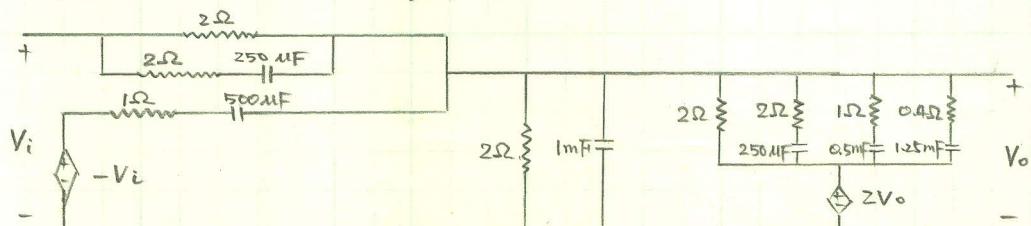

10-9. Realize the following transfer function by Mathews-Seifert's

METHOD: $H(s) = (s+1)^2 / (s+2)(s^2+3)$

SOLUTION:

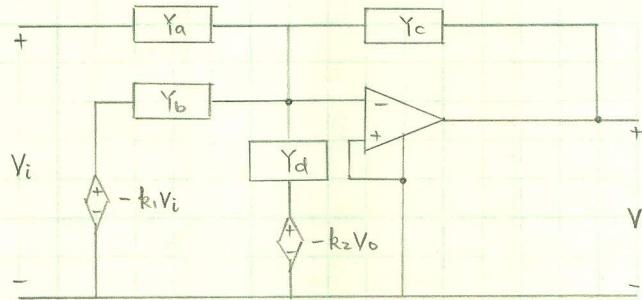

$$H(s) = \frac{V_o}{V_i} = \frac{k_1 Y_b - Y_a}{Y_c - k_2 Y_d}$$

LET $D(s) = (s+1)(s+2)$

∴ (i) $\frac{A(s)}{D(s)} = \frac{s+1}{s+2}$

$$\frac{A(s)}{sD(s)} = \frac{s+1}{s(s+2)} = \frac{1/2}{s} + \frac{1/2}{s+2}$$

$$\frac{A(s)}{D(s)} = \frac{1}{2} + \frac{1}{2 + 1/s} = Y_a - k_1 Y_b$$


(ii) $\frac{B(s)}{D(s)} = \frac{s^2+3}{s+1}$

$$\frac{B(s)}{sD(s)} = \frac{s^2+3}{s^2+s} = 1 + \frac{2}{s(s+1)} = 1 + \frac{2}{s} - \frac{2}{s+1}$$

$$\frac{B(s)}{D(s)} = s+2 - \frac{1}{0.5 + 1/2s} = k_2 Y_d - Y_c$$

LET $k_1 = 0, k_2 = 1$, AND
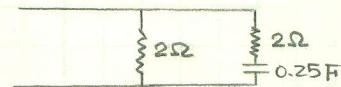
$$Y_a = \frac{1}{2} + \frac{1}{2 + 1/s} \Rightarrow$$




$$Y_b = 0$$


$$Y_c = \frac{1}{0.5 + 1/2s} \Rightarrow$$



$$Y_d = s+2 \Rightarrow$$

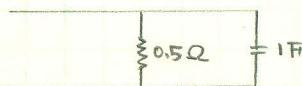

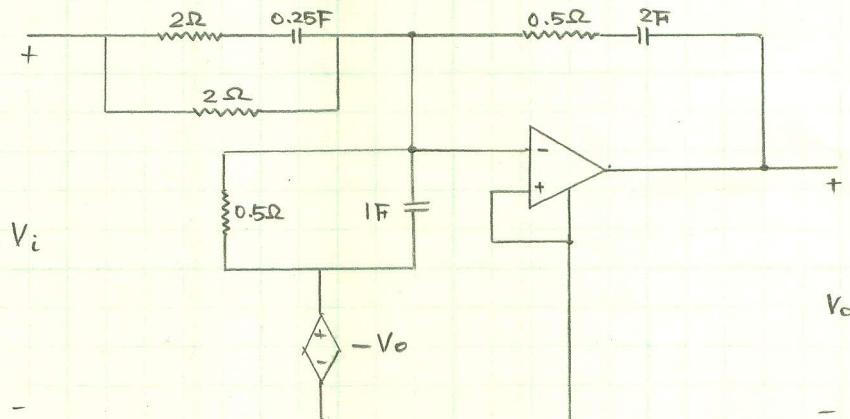
The following is the Mathews-Seifert's realization:



10-10. Realize the transfer function below by Lovering's method:

$$H(s) = (\hat{s}^2 + 1) / ((\hat{s} + 1)(\hat{s}^2 + 3\hat{s} + 3)) \text{ where } \hat{s} = s/4000$$

SOLUTION:

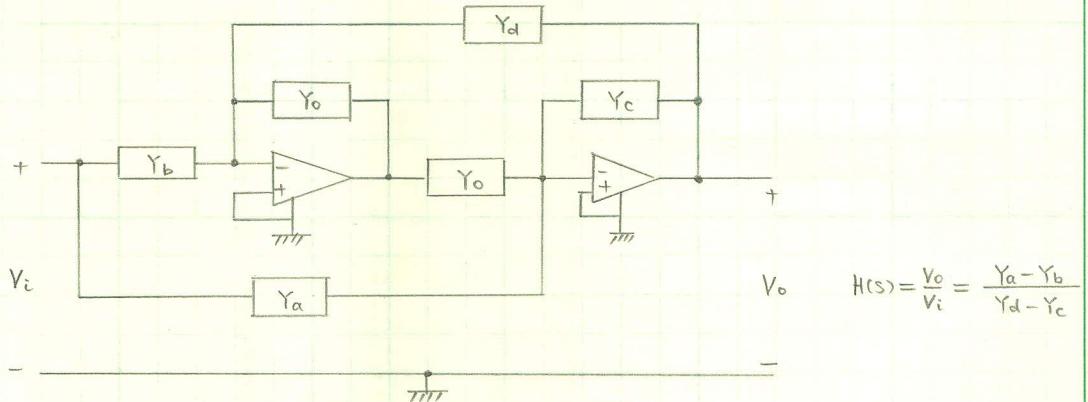

LET $D(s) = (\hat{s} + 1)(\hat{s} + 2)$

(i) $\frac{A(s)}{D(s) \cdot \hat{s}} = \frac{\hat{s}^2 + 1}{\hat{s}(\hat{s} + 1)(\hat{s} + 2)} = \frac{1/2}{\hat{s}} + \frac{5/2}{\hat{s} + 2} - \frac{2}{\hat{s} + 1}$


$\frac{A(s)}{D(s)} = \frac{1}{2} + \frac{1}{\frac{2}{5} + 1/\frac{5}{4}\hat{s}} - \frac{1}{\frac{1}{2} + 1/2\hat{s}} = Y_a - Y_b$

(ii) $\frac{B(s)}{\hat{s} \cdot D(s)} = \frac{\hat{s}^2 + 3\hat{s} + 3}{\hat{s}^2 + 2\hat{s}} = 1 + \frac{\hat{s} + 3}{\hat{s}(\hat{s} + 2)} = 1 + \frac{3/2}{\hat{s}} - \frac{1/2}{\hat{s} + 2}$

$\frac{B(s)}{D(s)} = \hat{s} + \frac{3}{2} - \frac{1}{2 + 1/\frac{1}{4}\hat{s}} = Y_d - Y_c$

THEN, LET

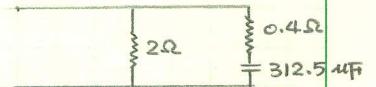$Y_a = \frac{1}{2} + \frac{1}{\frac{2}{5} + 1/\frac{5}{4}\hat{s}} = \frac{1}{2} + \frac{1}{\frac{2}{5} + 1/\frac{5}{4000 \times 4} s} \Rightarrow$




$Y_b = \frac{1}{\frac{1}{2} + 1/2\hat{s}} = \frac{1}{0.5 + 1/\frac{1}{2000} s} \Rightarrow$




$Y_c = \frac{1}{2 + 1/\frac{1}{4}\hat{s}} = \frac{1}{2 + 1/\frac{1}{16000} s}$



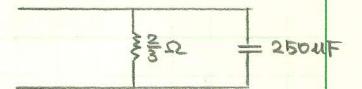$Y_d = \hat{s} + \frac{3}{2} = \frac{1}{4000} s + \frac{3}{2} \Rightarrow$



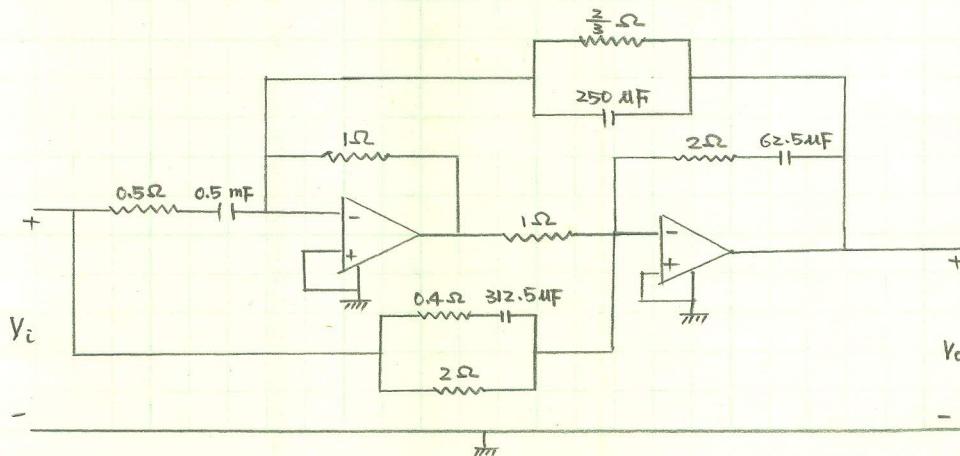
The overall realization is as follows: Choose $Y_0 = 1 \Omega$



10-11. Realize the following function by Mitra's method:

$$H(s) = \frac{-s^3 + 2s^2 - 2s + 4}{(s^3 + 2s^2 + 2s + 4)}$$

SOLUTION:

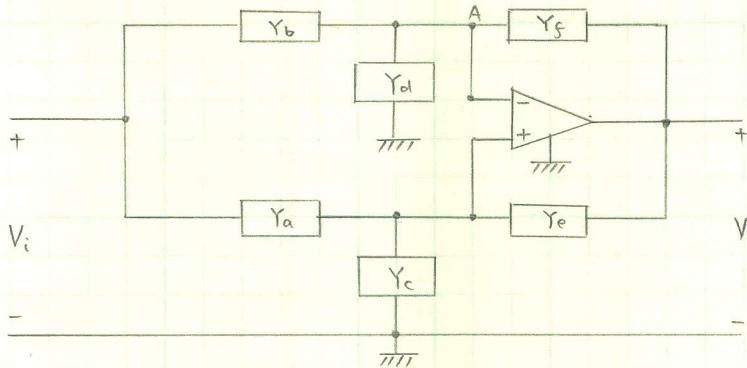

$$H(s) = \frac{Y_a(Y_b + Y_d + Y_f) - Y_b(Y_a + Y_c + Y_e)}{Y_f(Y_a + Y_c + Y_e) - Y_e(Y_b + Y_d + Y_f)}$$

$$H(s) = \frac{-s^3 + 2s^2 - 2s + 4}{s^3 + 2s^2 + 2s + 4} = \frac{-(s-2)(s^2+2)}{(s+2)(s^2+2)} = \frac{-s+2}{s+2}$$

LET $D(s) = 1$


(i) $\frac{A(s)}{s D(s)} = \frac{-s+2}{s} = -1 + \frac{2}{s}$

$\frac{A(s)}{D(s)} = 2 - s$


(ii) $\frac{B(s)}{s D(s)} = \frac{s+2}{s} = 1 + \frac{2}{s}$

$\frac{B(s)}{D(s)} = s + 2$


LET $Y_b = Y_{RC}^{(1)} = 2 \implies$

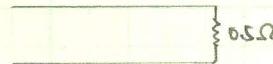

$Y_a = Y_{RC}^{(2)} = s$

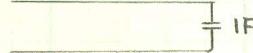

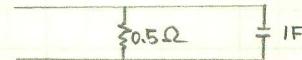$Y_f = 0 ; Y_e = Y_{RC}^{(3)} = s+2 \implies$




so, $Y_c - Y_d = Y_f + Y_b - Y_e - Y_a$

$= 2 - s - 2 - s = -2s$

$Y_c = 0 ; Y_d = 2s \implies$



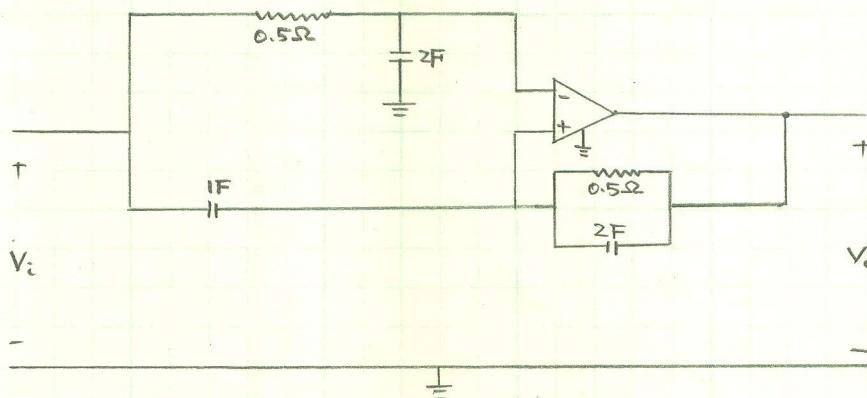The following is the Mitra's realization:



10-13. Realize the following transfer function via the state-variable technique: $H(s) = 2\hat{s}^2 / ((\hat{s}+2)(\hat{s}^2+1))$ where $\hat{s} = s/10000$.

SOLUTION:

$$\begin{aligned} H(s) &= \frac{z\hat{s}^2}{(\hat{s}+2)(\hat{s}^2+1)} \\ &= \frac{z\hat{s}^2}{\hat{s}^3 + 2\hat{s}^2 + \hat{s} + 2} \\ &= \frac{z(s/10000)^2}{(s/10000)^3 + 2(s/10000)^2 + (s/10000) + 2} \\ &= \frac{2 \times 10^4 s^2}{s^3 + 2 \times 10^4 s^2 + 10^8 s + 2 \times 10^{12}} \quad \dots \dots (1) \end{aligned}$$

From the equation (7) on page 105 in notes, we have the state-variable realization given as

$$H(s) = \frac{G_0 (RC)^{-1} s^2}{s^3 + \frac{G_1}{RC} s^2 + \frac{G_2}{(RC)^2} s + \frac{G_3}{(RC)^3}} = \frac{V_1}{V_2} \quad \dots \dots (2)$$

Compare the equations (1) and (2) above, we have

- (i) $G_0 = 2 \times 10^4 RC$
- (ii) $G_1 = 2 \times 10^4 RC$
- (iii) $G_2 = 10^8 (RC)^2$
- (iv) $G_3 = 2 \times 10^{12} (RC)^3$

We let all the G 's within the range of $10^{-6} < G < 10^{-1} \Omega$

Range of RC :


- (i) $5 \times 10^{-11} \times 0 \quad 5 \times 10^{-6}$
- (ii) $5 \times 10^{-11} \times 0 \quad 5 \times 10^{-6}$
- (iii) $1 \times 10^{-7} \times 0 \quad 3.1623 \times 10^{-5}$
- (iv) $7.937 \times 10^{-7} \times 0 \quad 3.684 \times 10^{-5}$

SO, LET $RC = 7.937 \times 10^{-7}$; $C = 1 \text{ nF}$ and $R = 793.7 \Omega$

$$G_0 = 1.5874 \times 10^{-2} \Rightarrow R_0 = 62.996 \Omega; \quad G_1 = 1.5874 \times 10^{-2} \Rightarrow R_1 = 62.996 \Omega$$

$$G_2 = 6.2996 \times 10^{-5} \Rightarrow R_2 = 15.874 \text{ k}\Omega; \quad G_3 = 10^{-6} \Rightarrow R_3 = 1 \text{ M}\Omega$$

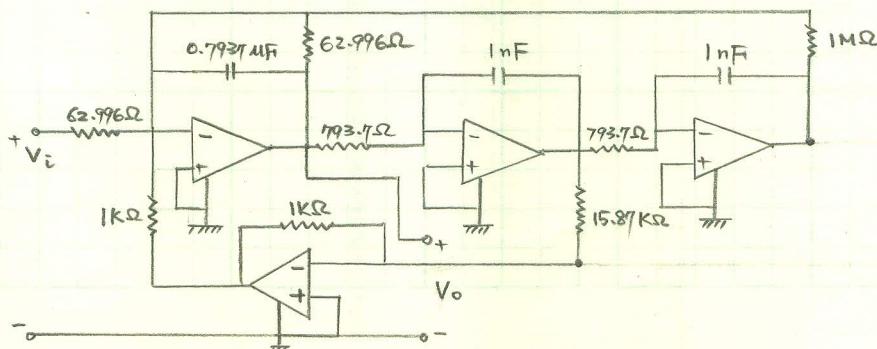The state-variable realization is as follows:




10-14. Realize the following second-order transfer functions via Table 10-1.

(e) $H(s) = \frac{\hat{s}^2 + 1}{\hat{s}^2 + 0.1\hat{s} + 1}$ where $\hat{s} = s/10^4$

50
50

According to the Table 10-1, A4 (b)

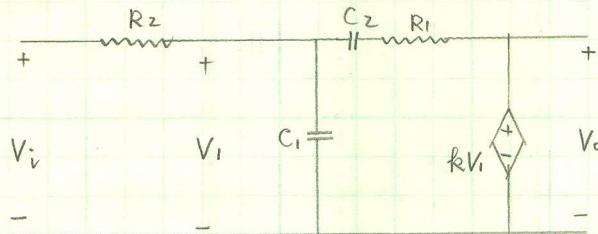

And the equations

$R_1 C_1 R_2 C_2 = 1$ (1)

$R_2 C_2 = 1/a = 1$ (2)

$R_1 C_1 + R_2 C_2 + R_1 C_2 (1-k) = 0.1$ (3)

$k R_2 C_2 = G_1 = 1$ (4)

$R_1 C_1 = 1$

$R_2 C_2 = 1$

$R_1 C_2 (1-k) = -1.9$

$G_1 = k R_2 C_2$

LET $R_1 = R_2 = 1 \Omega$; $C_1 = C_2 = 1 F$.


$k = 2.9$; $\therefore G_1 = 2.9$; $\beta = 0.34483$

$H(s) = 0.34483 \cdot \frac{2.9(\hat{s}^2 + 1)}{\hat{s}^2 + 0.1\hat{s} + 1} = \beta H_1(s)$

SCALING FREQUENCY BY 10^4

$R_1 = R_2 = 10 K\Omega$; $C_1 = C_2 = 0.1 \mu F$

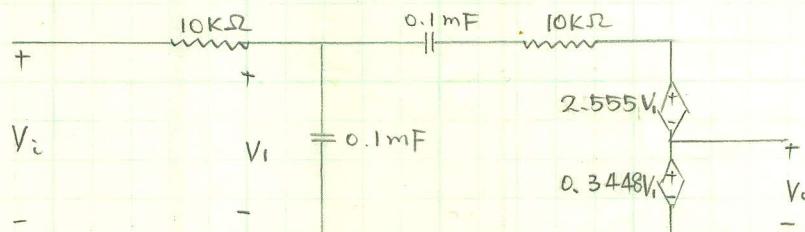THE FOLLOWING IS THE CIRCUIT REALIZATION:



10.-19. Realize the following transfer functions by Friend's circuit configuration of Fig. 10-26:

$$(b) \quad H(s) = \frac{s^2 - 100s + 10^6}{s^2 + 100s + 10^6}$$

$$= \frac{\left(\frac{s}{1000}\right)^2 - 0.1 \times \left(\frac{s}{1000}\right) + 1}{\left(\frac{s}{1000}\right)^2 + 0.1 \times \left(\frac{s}{1000}\right) + 1}$$

$$\underline{A} \quad \frac{\hat{s}^2 - 0.1 \hat{s} + 1}{\hat{s}^2 + 0.1 \hat{s} + 1} \quad \text{WHERE } \hat{s} = s/10^3$$

WITH $a_2 = 1$, $a_1 = -0.1$, $a_0 = 1$, $b_1 = 0.1$, $b_0 = 1$

$$G_1 = \frac{C_2 G_a}{2 G_b} \left[-0.1 + \sqrt{0.01 + 4 \left(1 + \frac{C_1}{C_2}\right) \frac{G_b}{G_a}} \right]$$

$$G_4 = \frac{G_1 G_a}{G_a + G_b} \left[1 + \left(1 + \frac{C_1}{C_2}\right) \cdot \frac{C_2}{G_1^2} + \frac{0.1 C_2}{G_1} \right]$$

CHOOSE $C_1 = C_2 = 1 \text{ F}$, $G_a = G_b = 1 \text{ mho}$.

WE HAVE $G_1 = 0.95125$ $G_4 = 1.576817$

LET $\beta = G_1 / G_4 = 0.6$


$$\therefore \beta H(s) = \frac{0.6 \hat{s}^2 - 0.06 \hat{s} + 0.6}{\hat{s}^2 + 0.1 \hat{s} + 1}$$

LET $C_1 = C_2 = 1 \text{ F}$, $G_a = G_b = 1 \text{ V}$, $\alpha = 0$

WE HAVE

$$\left\{ \begin{aligned} G_1 &= 0.95125 = \frac{1}{1.05125} \\ G_4 &= 0.88612 = 1/1.12852 \\ G_3 &= 0 \\ G_2 &= 1.05125 = 1/0.95125 \\ G_5 &= 0.06513 = 1/15.3539 \\ G_6 &= G_7 = 0 \\ G_c &= 0.6 = 1/1.66667 \\ G_d &= 0.4 = 1/2.5 \end{aligned} \right.$$

SCALED BY FREQ. 10^3 :

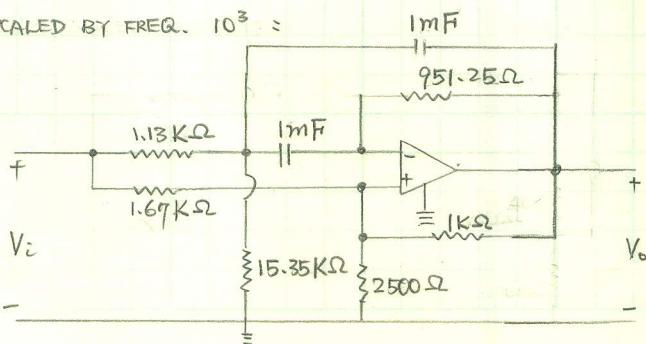

$$H(s) = \frac{0.6(s^2 - 100s + 10^6)}{s^2 + 100s + 10^6}$$

10-20. (a) Realize the transfer function by Friend's circuit configuration.

$$H(s) = \frac{s^2 + 10^4}{s^2 + 100s + 10^6}$$

SOLUTION: $H(s) = \frac{(s/1000)^2 + 0.01}{(s/1000)^2 + 0.1(s/1000) + 1} \cdot \frac{\Delta}{\hat{s}^2 + 0.1\hat{s} + 1} ; \hat{s} = s/10^3$

$a_2 = 1, a_1 = 0, a_0 = 0.01, b_1 = 0.1, b_0 = 1$

LET $C_1 = C_2 = 1F ; G_a = G_b = 1\Omega ; \alpha = 1, \beta = 0.9$

$G_1 = 0.95125 = 1/1.05125 ; G_4 = 0.43662 = 1/2.29032$


$G_3 = 4.68332 = 1/0.21352 ; G_2 = 5.73457 = 1/0.17438$

$G_5 = 0.51463 = 1/1.94315 ; G_6 = 4.21499 = 1/0.23725$


$G_7 = 0.46833 = 1/2.13524 ; G_c = 0.9 = 1/1.11111$

$G_d = 0.1 = 1/10$

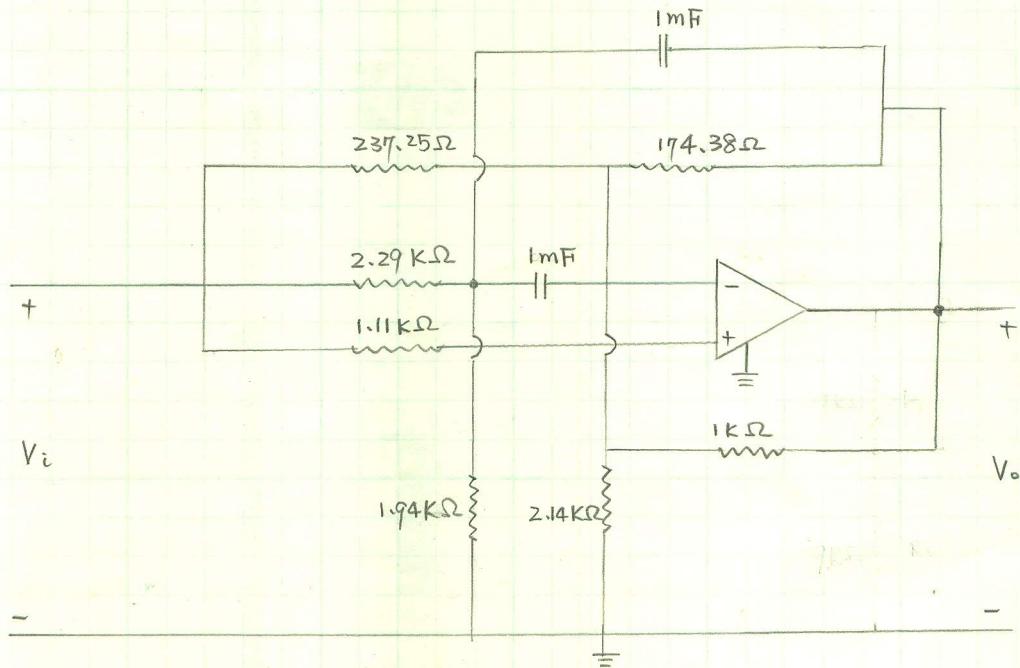THE FOLLOWING IS THE FRIEND'S CIRCUIT CONFIGURATION: (SCALED FREQ. BY 10^3)


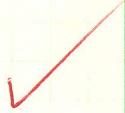
$$H(s) = 0.9 \frac{s^2 + 10^4}{s^2 + 100s + 10^6}$$



10-21. Realize the following transfer functions via the multiple amplifier biguads of Fig. 10-29.

$$(b) \quad H(s) = \frac{1}{s^2 + \sqrt{2}s + 1}, \quad \text{WHERE } \hat{s} = s/10^4$$

FROM EQ. (10-133a) IN TEXT,

$$\frac{V_3}{V_i} = \frac{R_2(R+R_3)}{R_3(R_1+R_2)} \cdot \frac{1}{C_1 C_2 R_8 R_9 s^2 + \frac{R_1(R+R_3)}{(R_1+R_2)R_3} R_9 C_2 s + \frac{R}{R_3}}$$

$$\text{LET } C_1 = C_2 = 1 \text{ F} \quad R_1 = R_2 = R_3 = 1 \Omega$$

$$\therefore R = R_3 = 1 \Omega \quad \text{and}$$


$$\frac{2}{2} \cdot R_9 \cdot 1 = \sqrt{2} \Rightarrow R_9 = \sqrt{2} \Omega$$

$$R_8 = \sqrt{2}/2 \Omega \quad \text{and} \quad R = 1$$

FREQ. SCALING BY 10^4 , WE HAVE

$$C_1 = C_2 = 0.1 \text{ mF}, \quad R_1 = R_2 = R_3 = R = 10 \text{ k}\Omega, \quad R_8 = 7.07 \text{ k}\Omega, \quad R_9 = 14.14 \text{ k}\Omega$$

THEN CIRCUIT GIVEN BELOW:

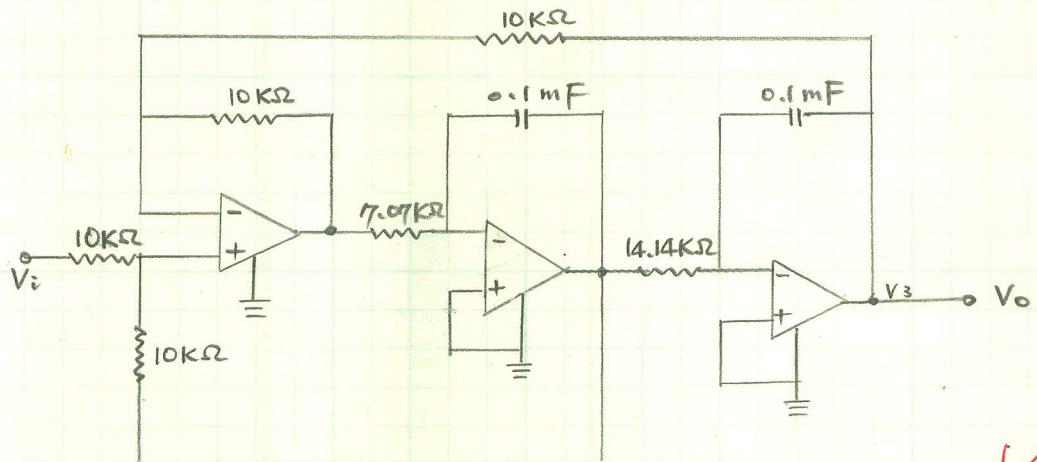

$$(j) \quad H(s) = \frac{s^2 + \sqrt{2}s + 1}{s^2 + 3s + 3}$$

Solution: $a_1 = \sqrt{2}$, $a_0 = 1$; $b_1 = 3$, $b_0 = 3$

$$\frac{R_6(R_4 + R_5)}{C_1 R_8 R_5 (R_6 + R_7)} = a_1 = \sqrt{2}$$

$$\frac{R_4}{C_1 R_8 C_2 R_9 R_5} = a_0 = 1$$

$$\frac{R_1(R_2 + R_3)}{C_1 R_8 R_3 (R_1 + R_2)} = b_1 = 3$$

$$\frac{R}{C_1 R_8 C_2 R_9 R_3} = b_0 = 3$$

$$\beta = \frac{R_2 R_5 (R_2 + R_3)(R_6 + R_7)}{R_3 R_7 (R_1 + R_2)(R_4 + R_5)} = 1$$

LET $R_1 = R_2 = R_3 = R_4 = R_5 = 1\Omega$; $C_1 = C_2 = 1F$

$$\therefore \left\{ \begin{array}{l} 2 \frac{R_6}{R_8 (R_6 + R_7)} = \sqrt{2} \\ \frac{1}{R_8 R_9} = 1 \\ \frac{R+1}{2R_8} = 3 \\ \frac{(R+1)(R_6 + R_7)}{4R_7} = 1 \end{array} \right. \quad \text{and} \quad \frac{R}{R_8 R_9} = 3$$

$\therefore R = 3\Omega$; $R_8 = 0.667\Omega$; $R_9 = 1.5\Omega$; $R_6 = 0$, $R_7 = 2.121\Omega$

